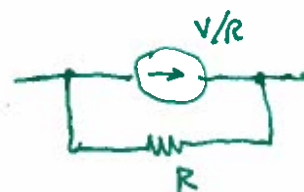


Thevenin and Norton equivalents related by a source transformation.

Thursday, February 25, 2016




voltage source, V
series resistance, R




Current source, V/R
parallel resistance, R .

Example 2, revisited

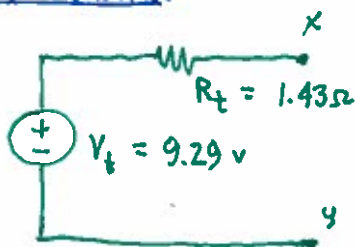

THEVENIN


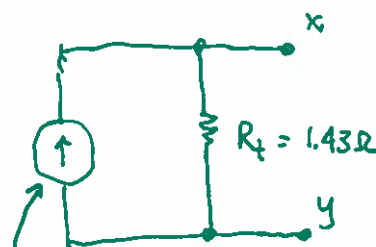


$$I_n = V_t / R_t \\ = 6.5 \text{ A}$$


The source transformation as a handy simplification

Circuits can often be simplified by source transformations.


Example:

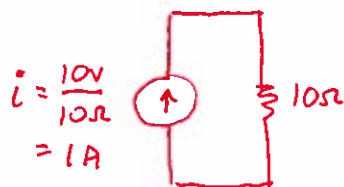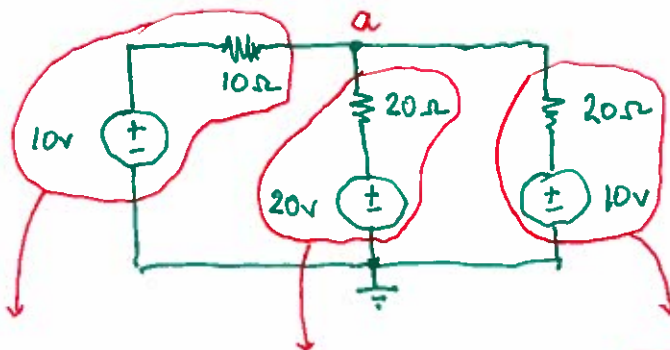

We now have

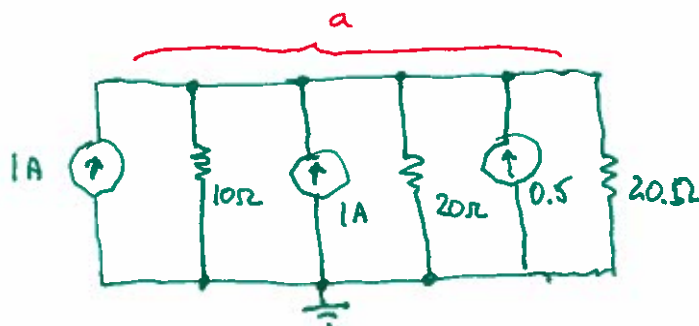

Rearranged:

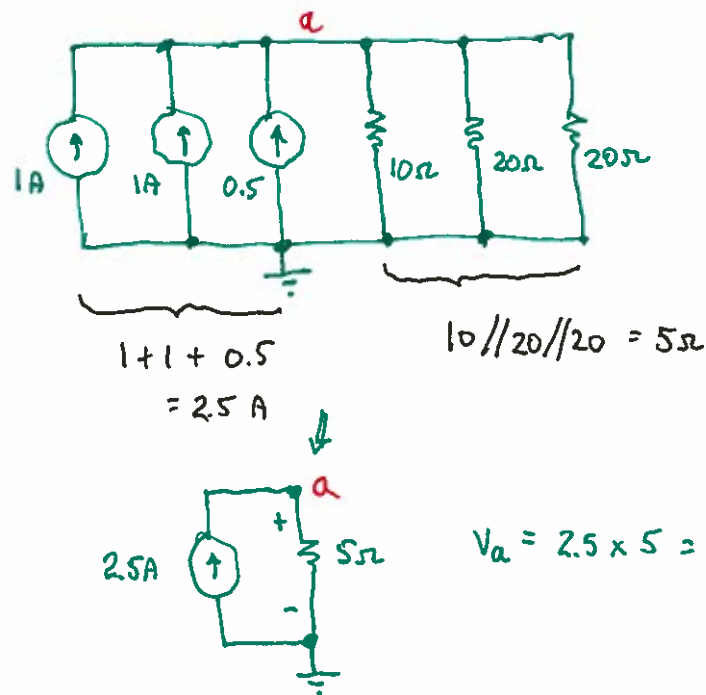

Principle of superposition

A fundamentally important concept, and often a required method in AC circuit analysis. We first present for DC circuits.

Method:

1. Let only one independent source be active.
2. Zero all other independent sources.
3. Determine the response (voltage or current) r' at desired location in the circuit.


Repeat one at a time for all other independent sources in circuit; find r'' , r''' , etc.

Superposition:

The total response (voltage or current) r is the sum of the individual responses


$$r = r' + r'' + r''' + \dots$$

Example 1: Find i_x by superposition

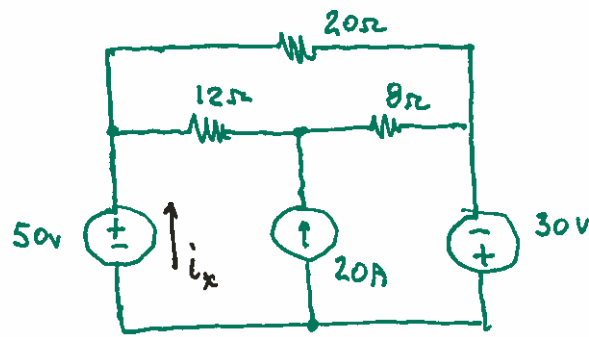

We have three independent sources. Activate one source at a time, zero the other two.

(a) 50 v source by itself

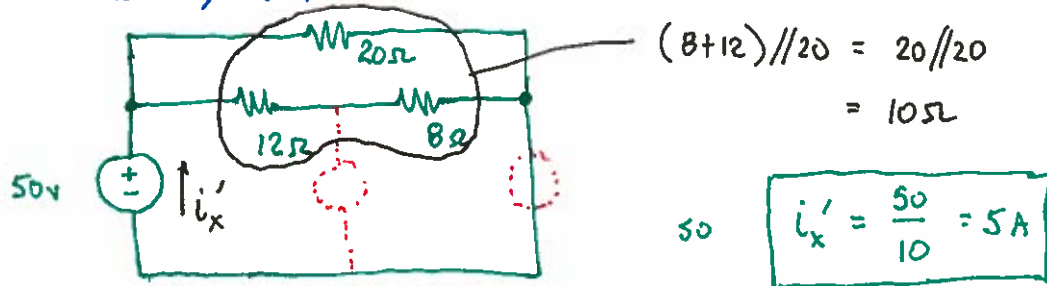

(b) 20 A source by itself

