

Monday, March 7, 2016

$$V_D = \frac{10K}{10K + 20K} \times 5 = \frac{5}{3}V$$

$$[\text{or node equation: } \frac{V_D - 5}{20K} + \frac{V_D}{10K} + i_{A1} = 0]$$

This must also be the voltage at A: $V_A = \frac{5}{3}V$.

Also, we know $V_C = 0V$. We have two unknown voltages: V_B, V_O

Op-amp's input terminals always most important. Write an equation at node A, where we know $V_A = \frac{5}{3}V$.

$$\frac{V_A - 1}{20K} + i_{n1} + \frac{V_A - V_B}{10K} = 0$$

$$V_A - 1 + 2V_A - 2V_B = 0$$

$$3V_A - 2V_B = 1$$

$$\text{But } V_A = \frac{5}{3}V, \text{ so } \left(\frac{5}{3}\right)3 - 2V_B = 1$$

$$5 - 2V_B = 1$$

$$\therefore V_B = 2V$$

One more node of interest: V_C !

$$\frac{V_C - V_O}{100K} + \frac{V_C - V_B}{40K} + i_{n2} = 0$$

With $V_B = 2, V_C = 0$


$$\frac{-V_O}{100K} - \frac{2}{40K} = 0$$

$$V_O = \frac{-2(100K)}{40K}$$

$$\boxed{V_O = -5V}$$

Input resistance of op-amp circuits

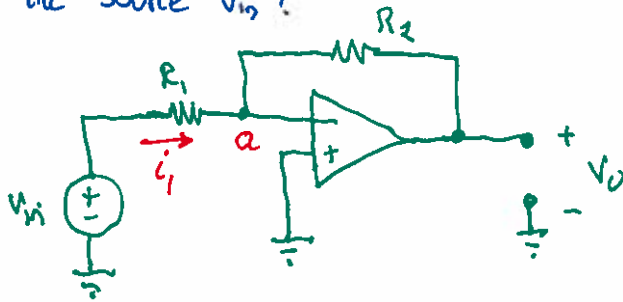
Consider an inverting amplifier. What is the resistance "seen" by the source V_{in} ?




Recall that $V_a = 0$ due to the virtual short circuit

$$\text{We have } i_1 = \frac{V_{in}}{R_1}$$

so the source "sees" a resistance of R_1

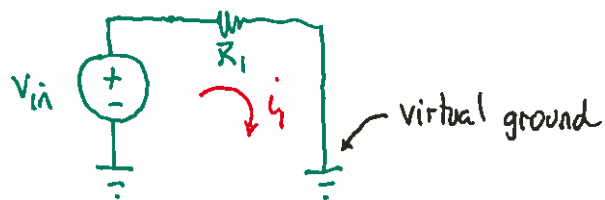

Now how about non-inverting

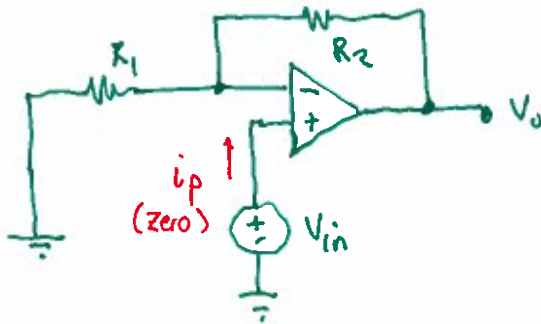


$$i_p = 0$$

$$\text{so } R_{in} = \frac{V_{in}}{i_p} = \infty$$

open-circuit!

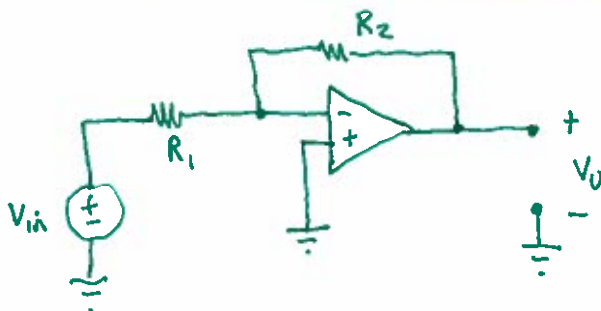Another application of op-amps - comparators



We showed


$$V_o = -\frac{R_2}{R_1} V_{in}$$

$$\text{closed-loop gain } A_v = -\frac{R_2}{R_1}$$

Resistor R_2 is a critical component here

- provides the required "negative feedback" to allow this circuit to operate.

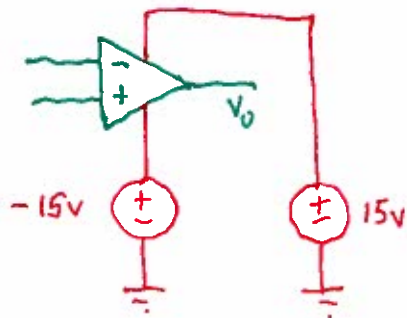
Also recall that the op-amp itself requires an external power source to operate.




— with external power sources as shown, V_o is allowed to be any voltage in range

$$-15 \leq V_o \leq 15.$$

Now suppose that R_2 is not there.

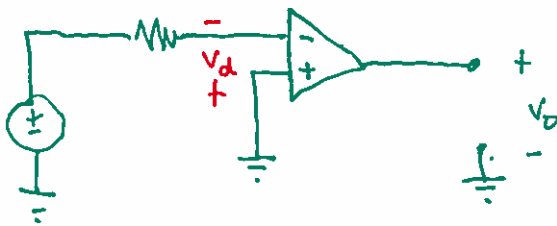

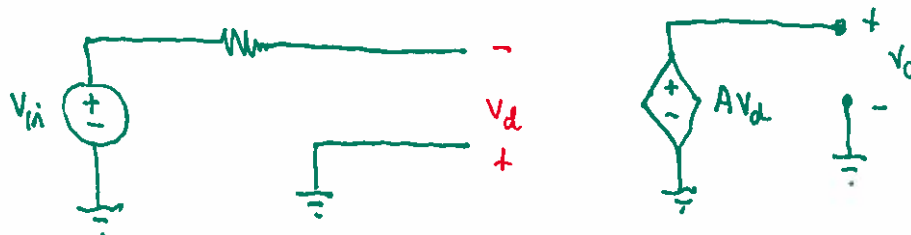This now means that we are running the op-amp "open-loop".
Using the ideal model,



We have

$$V_d = -V_{in}, \quad \text{so}$$

$$V_o = -A V_{in}$$

↑ "open-loop" gain
→ big number! (ideally ∞)

$$\text{If } V_{in} < 0, \quad V_o = + [\text{huge number}]$$

$$V_{in} > 0, \quad V_o = - [\text{huge number}]$$

Here, [huge number] is limited by the external power sources, so

$$\begin{array}{ll} \text{If } V_{in} < 0, & V_o = +15 \text{ V} \\ V_{in} > 0, & V_o = -15 \text{ V} \end{array} \quad \left. \vphantom{\begin{array}{l} \\ \\ \end{array}} \right\} \begin{array}{l} \text{only operates} \\ \text{at extremes.} \end{array}$$

This behaviour makes the op-amp very useful as a voltage comparator.