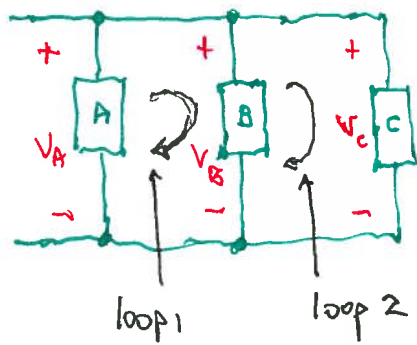


Parallel circuits:



KVL around loop 1

$$-V_A + V_B = 0, \text{ so } V_A = V_B$$

KVL around loop 2


$$-V_B + V_C = 0, \text{ so } V_B = V_C$$

$$\text{Therefore } V_A = V_B = V_C$$

Circuit elements in parallel have the same voltage.

KVL/KCL examples

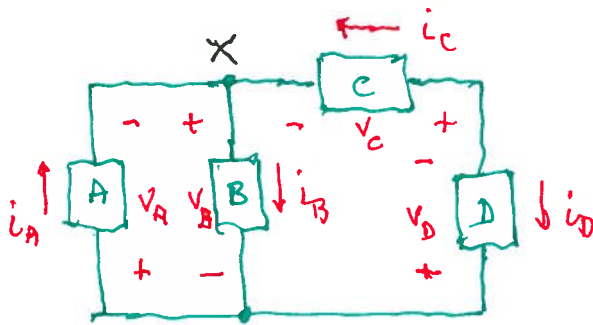Example 1: Consider the circuit below, labeled as shown.





(a) what's in series, what's in parallel?

(b) what's i_C in terms of i_D ?



(c) $i_A = 3$, $i_C = 1$. Find i_B , i_D .

Solution

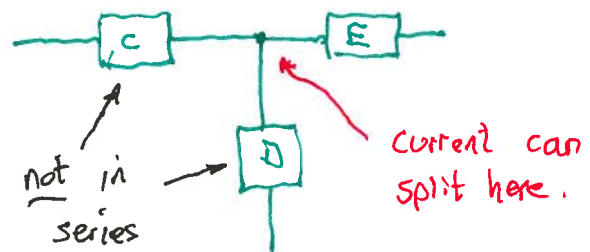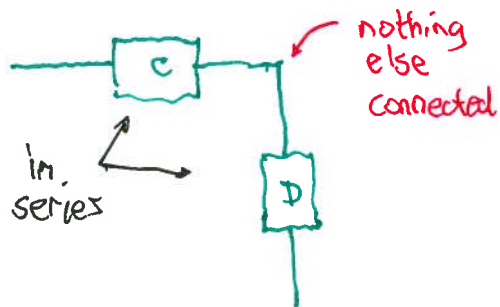(a) In series: only C and D (where they join, nothing else joins).



In parallel: Only A and B

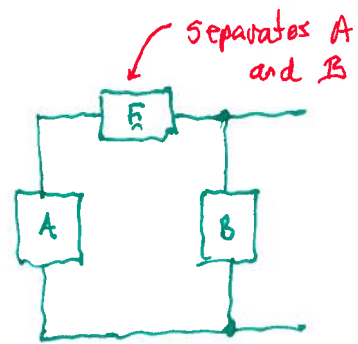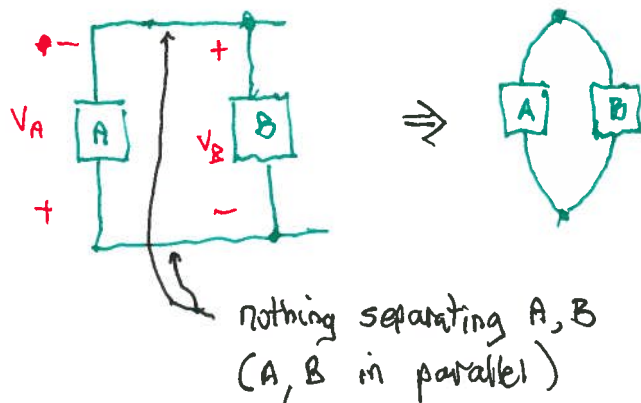

A, B not in parallel
(because A and B are separated at the top by E).

(b) Since C and D in series, they must have identical currents.

$$i_C = -i_D$$

(c) KCL at node X: $i_A + i_C - i_B = 0$

$$i_B = i_A + i_C = 3 + 1 = 4 \text{ A}$$

$$\text{and } i_D = -i_C, \text{ so } i_D = -1 \text{ A.}$$