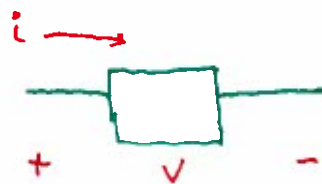



Circuit elements (continued)

Thursday,
January 14, 2015


All circuit elements are characterized by their voltage-current relationship.



Conductors (wires)

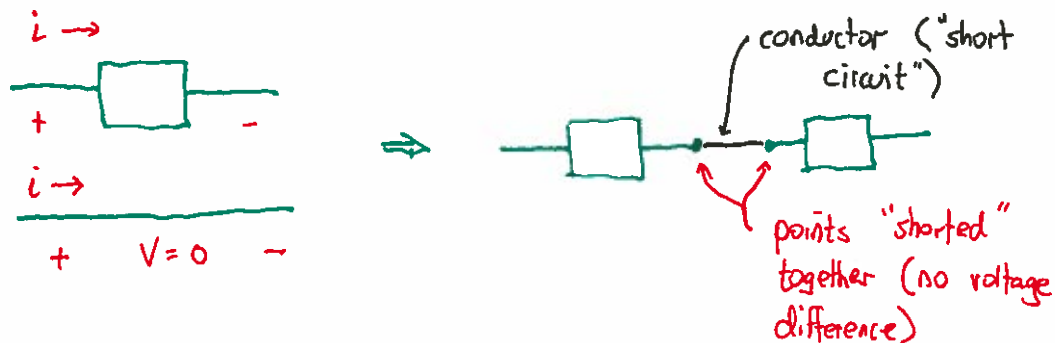

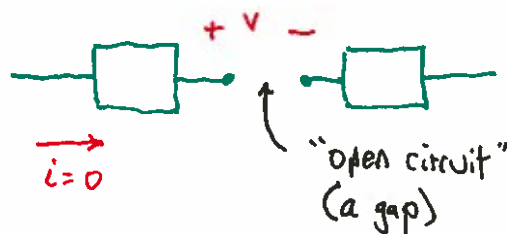
The absence of a conductor between other circuit elements is an open circuit.




Sources

Independent voltage sources:

Symbol:

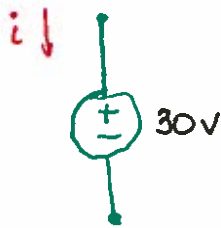

DC source

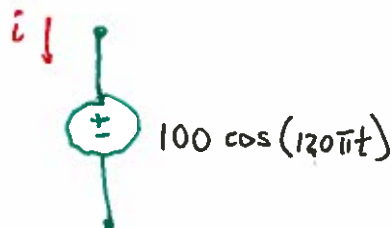

AC source


Properties:

- voltage is specified explicitly — not dependent on any other factor
- voltage unchanged by whatever it's connected to (i.e., voltage is independent of the current through it).


Dependent voltage sources:

- Have the same properties as independent voltage sources, except the value of the voltage depends on either a voltage or current elsewhere in the circuit.

VCVS
(voltage-controlled VS)

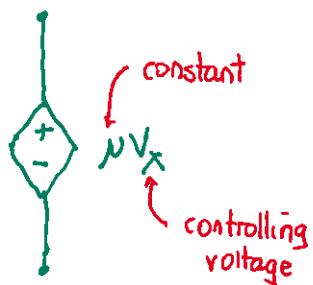


CCVS
(current-controlled VS)

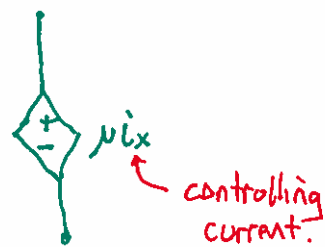


There can be DC or AC dependent sources as well.

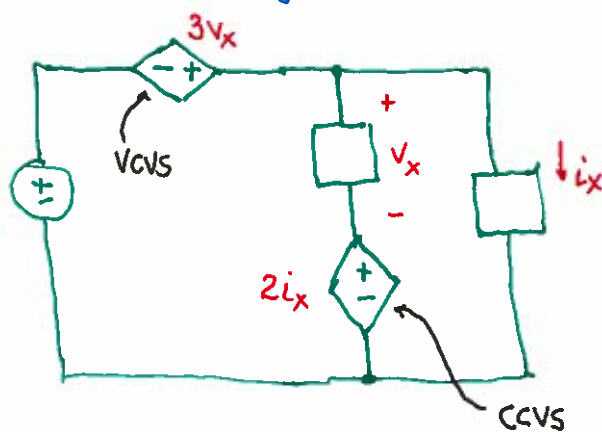A circuit using dependent voltage sources ...




Independent current sources:

Symbol:

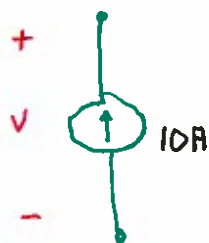

DC source

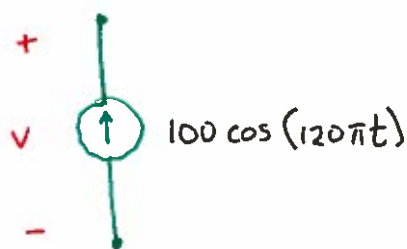

AC source


Properties:

- current specified explicitly — not dependent on any other factor
- current unchanged by whatever it is connected to (i.e., current is independent of the voltage across it).


Dependent current sources:

- Same properties as independent, except current depends on voltage or current elsewhere.

VCCS
(voltage-controlled CS)

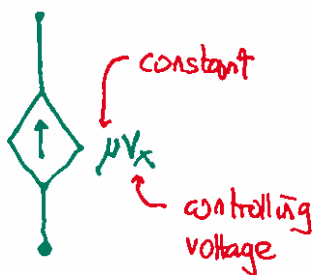


CCCS
(current-controlled CS)

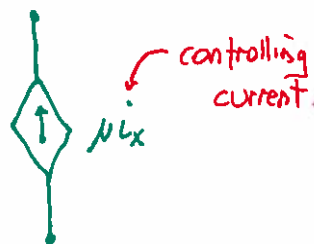

Resistors

Circuit symbol:

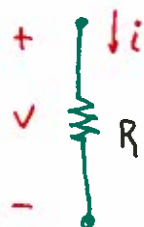


resistance in Ohms (Ω),
 R is a constant

Important: direction of i , polarity of v , defined as shown for Ohm's Law — resistor is always absorbing energy.

$$V = iR$$

Ohm's Law

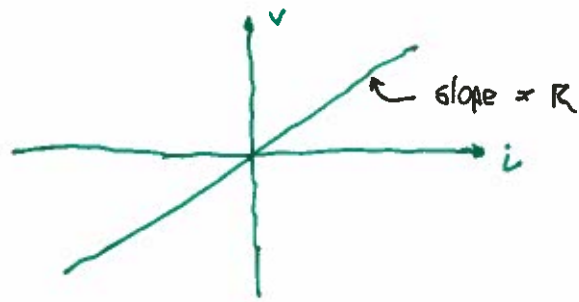

Suppose we have labelled a resistor this way:



Ohm's Law then
states $V = -iR$