


Monday, January 25, 2016

Circuit Analysis using series-parallel equivalents

Circuit analysis: this is a procedure for determining all voltages and currents in every circuit element.


We may employ the above simple resistor equivalents to analyze a circuit.

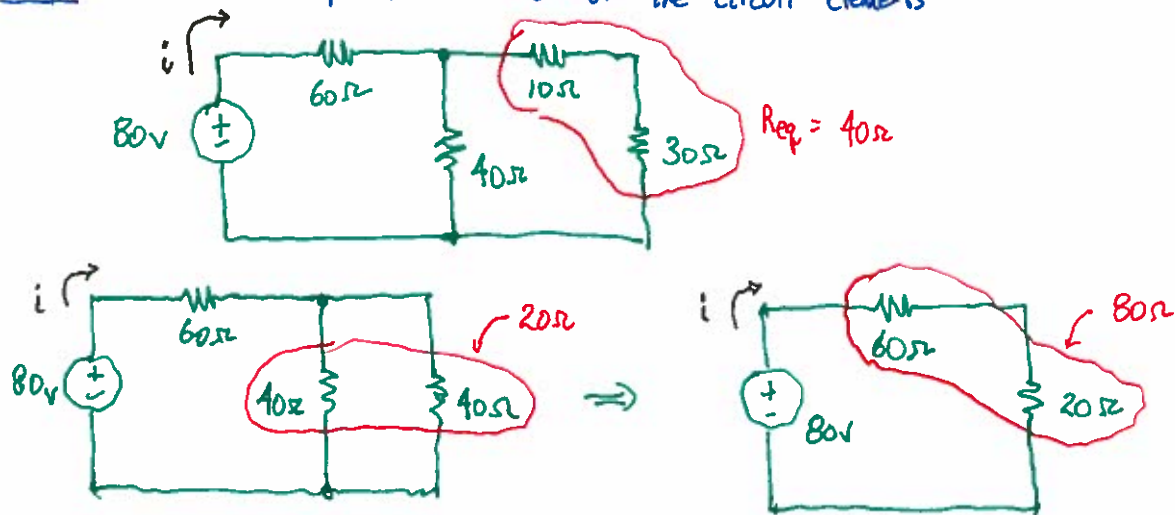Example: Find the power in each of the circuit elements



We may now determine $i = \frac{80\text{ V}}{80\Omega} = 1\text{ A}$

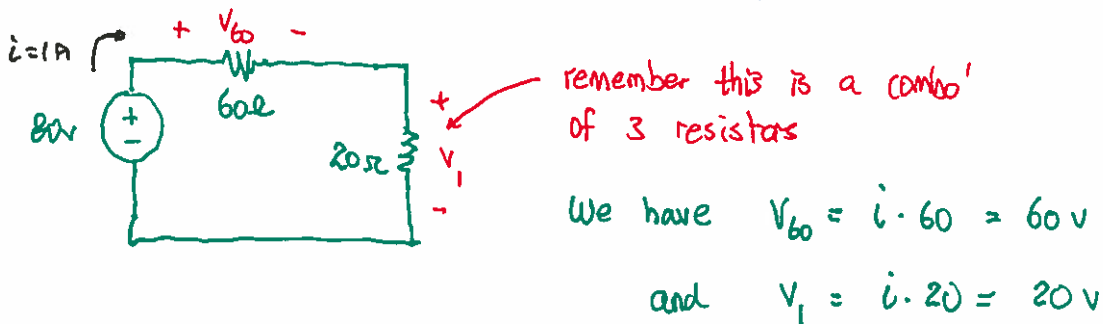Now reconstruct the original circuit, step-by-step. Let's define V_{60} and V_1



KVL check: $-80 + V_{60} + V_1 = 0$
 $-80 + 60 + 20 = 0 \checkmark$

Now reconstruct the rest




We have $i_1 = \frac{V_1}{40} = 0.5$

and $i_2 = \frac{V_1}{30+10} = 0.5$

KCL check at node A: $i - i_1 - i_2 = 0$

$1 - 0.5 - 0.5 = 0$ ✓

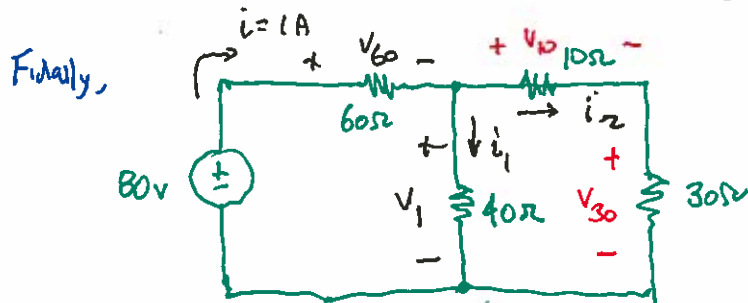

Finally,

$V_{10} = i_2 \cdot 10 = 5V$

$V_{30} = i_2 \cdot 30 = 15V$

Now power:

element

power

80V

$P_{80} = -vi = -80 \times 1 = -80W$

60Ω

$P_{60} = i^2(60) = 60W$

40Ω

$P_{40} = i_1^2(40) = 10W$

10Ω

$P_{10} = i_2^2(10) = 2.5W$

30Ω

$P_{30} = i_2^2(30) = 7.5W$

Energy balance: $-80 + 60 + 10 + 2.5 + 7.5 = 0$


Later, we will use well-established systemic methods to do analysis:

- node-voltage method
- mesh-current method
- Thevenin equivalents
- superposition

Other simple resistor circuits - voltage and current dividers

Voltage dividers:

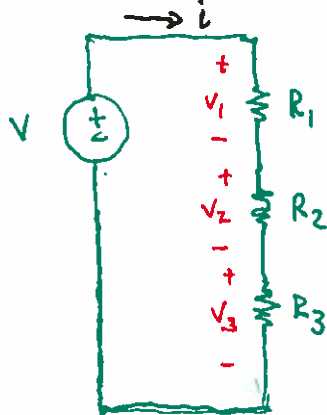In a series connection of resistors, the total applied voltage divides among them.



We have

$$R_{eq} = R_1 + R_2 + R_3$$

$$\text{so } i = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2 + R_3}$$

Individual voltages

$$V_1 = iR_1$$

$$V_2 = iR_2$$

$$V_3 = iR_3$$


$$\text{so, for } R_1: V_1 = \left(\frac{R_1}{R_1 + R_2 + R_3} \right) V$$

Similarly for R_2, R_3

R_1 's portion of total resistance is same as V_1 's portion of total voltage.

Current dividers:

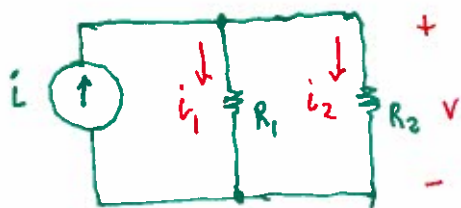In a parallel connection of resistors, total applied current divides among them.



We have

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{so } V = i \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$