

Question 1

Solving using the mesh-current method:

$$\begin{aligned} \text{mesh } \bar{I}_1: \quad & -30 \angle 20^\circ + (3+j4)\bar{I}_1 + (2+j)(\bar{I}_1 - \bar{I}_2) = 0 \\ & -30 \angle 20^\circ + 3\bar{I}_1 + j4\bar{I}_1 + 2\bar{I}_1 + j\bar{I}_1 - 2\bar{I}_2 - j\bar{I}_2 = 0 \\ & (5+j5)\bar{I}_1 + (-2-j)\bar{I}_2 = 30 \angle 20^\circ \quad (1) \end{aligned}$$

$$\begin{aligned} \text{mesh } \bar{I}_2: \quad & (2+j)(\bar{I}_2 - \bar{I}_1) + (3+j2-j6)\bar{I}_2 = 0 \\ & 2\bar{I}_2 - 2\bar{I}_1 + j\bar{I}_2 - j\bar{I}_1 + 3\bar{I}_2 - j4\bar{I}_2 = 0 \\ & (5-j3)\bar{I}_2 + (-2-j)\bar{I}_1 = 0 \quad (2) \end{aligned}$$

$$\text{From equation (2), } \bar{I}_2 = \frac{(2+j)}{5-j3} \bar{I}_1$$

$$\begin{aligned} \text{so } \bar{I}_2 &= \frac{(2+j)}{(5-j3)} \cdot \frac{(5+j3)}{(5+j2)} \times \bar{I}_1 \\ &= \frac{7+j11}{34} \times \bar{I}_1 = (0.2059 + j0.3235) \bar{I}_1 \quad (3) \end{aligned}$$

Substitute into equation (1),

$$(5+j5)\bar{I}_1 + (-2-j)(0.2059 + j0.3235)\bar{I}_1 = 30 \angle 20^\circ$$

$$(5+j5)\bar{I}_1 + (-0.08824 - j0.0529)\bar{I}_1 = 30 \angle 20^\circ$$

$$(4.9118 + j4.1471)\bar{I}_1 = 30 \angle 20^\circ$$

$$\bar{I}_1 = \frac{28.191 + j10.261}{4.9118 + j4.1471} = \frac{30 \angle 20^\circ}{6.4284 \angle 40.175^\circ}$$

$$\boxed{\bar{I}_1 = 4.667 \angle -20.174^\circ}$$

From equation (3),


$$\bar{I}_2 = (0.2059 + j0.3235)\bar{I}_1 = (0.3835 \angle 57.529^\circ)\bar{I}_1$$

$$\bar{I}_2 = (4.667 \angle -20.174^\circ)(0.3835 \angle 57.529^\circ)$$

$$\boxed{\bar{I}_2 = 1.790 \angle 37.355^\circ}$$

Question 2

In phasor form using complex impedances

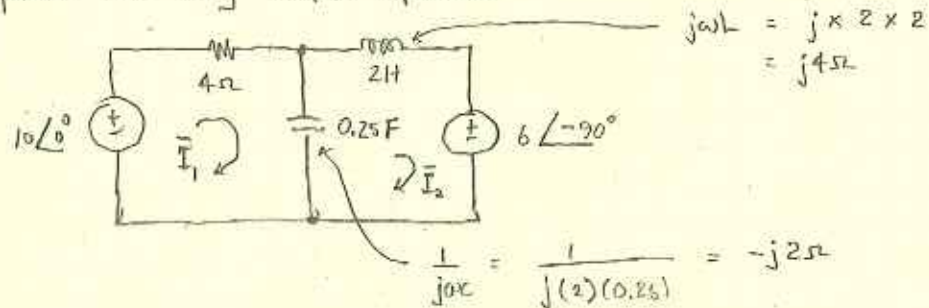

$$\text{Mesh } \bar{I}_1: -10\angle 0^\circ + 4\bar{I}_1 + (-j2)(\bar{I}_1 - \bar{I}_2) = 0$$

$$-10 + 4\bar{I}_1 - j2\bar{I}_1 + j2\bar{I}_2 = 0$$

$$(4 - j2)\bar{I}_1 + j2\bar{I}_2 = 10 \quad (1)$$

$$\text{Mesh } \bar{I}_2: (-j2)(\bar{I}_2 - \bar{I}_1) + (j4)\bar{I}_2 + 6\angle -90^\circ = 0$$

$$-j2\bar{I}_2 + j2\bar{I}_1 + j4\bar{I}_2 - j6 = 0$$

$$j2\bar{I}_2 + j2\bar{I}_1 = j6$$

$$\text{Divide by } j: 2\bar{I}_2 + 2\bar{I}_1 = 6 \quad (2)$$

$$\text{From equation (2), } \bar{I}_2 + \bar{I}_1 = 3, \text{ so } \bar{I}_2 = 3 - \bar{I}_1 \quad (3)$$

Substitute into (1)

$$(4 - j2)\bar{I}_1 + j2(3 - \bar{I}_1) = 10$$

$$4\bar{I}_1 - j2\bar{I}_1 + j6 - j2\bar{I}_1 = 10$$

$$(4 - j4)\bar{I}_1 = 10 - j6$$

$$\bar{I}_1 = \frac{10 - j6}{4 - j4} = \frac{10 - j6}{4 - j4} \times \frac{4 + j4}{4 + j4} = \frac{40 + j40 - j24 + 24}{16 - j16 + j16 + 16} = \frac{64 + j16}{32}$$

$$\bar{I}_1 = 2 + j0.5$$


$$\text{From (3), } \bar{I}_2 = 3 - \bar{I}_1 = 3 - 2 - j0.5 = 1 - j0.5$$

$$\text{And } \bar{I}_0 = \bar{I}_1 - \bar{I}_2 = 2 + j0.5 - (1 - j0.5) = 1 + j$$

$$\bar{I}_0 = 1 + j = 1.414 \angle 45^\circ$$

Question 3

From above, $\theta = 14.036^\circ$

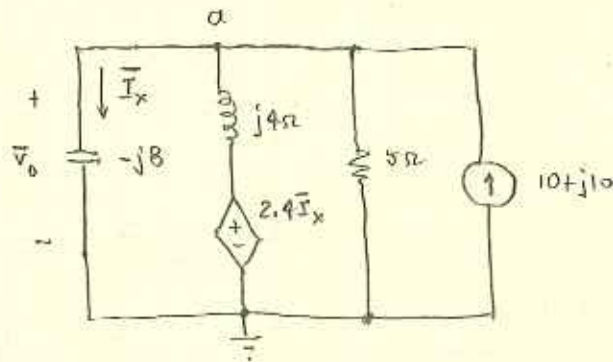Question 4

Note that $\bar{V}_o = \bar{V}_a$

Using the node-voltage method,

$$\frac{\bar{V}_o}{-j8} + \frac{\bar{V}_o - 2.4\bar{I}_x}{j4} + \frac{\bar{V}_o}{5} - (10 + j10) = 0$$

$$(\times j40) \quad -5\bar{V}_o + 10\bar{V}_o - 24\bar{I}_x + j8\bar{V}_o = -400 + j400$$

$$\bar{V}_o(5 + j8) - 24\bar{I}_x = -400 + j400 \quad (1)$$

The controlling current $\bar{I}_x = \frac{\bar{V}_o}{-j8}$, so equation (1) becomes

$$(5 + j8)\bar{V}_o - j3\bar{V}_o = -400 + j400$$

$$(5 + j5)\bar{V}_o = -400 + j400$$


$$\text{so } \bar{V}_o = \frac{-400 + j400}{5 + j5} = \frac{-80 + j80}{1 + j1}$$

$$\text{and } \bar{V}_o = \frac{-80 + j80}{1 + j} \cdot \frac{1 - j}{1 - j} = \frac{-80 + j80 + j80 + 80}{1 + j - j + 1}$$

$$= \frac{j160}{2} = \boxed{j80}$$

Question 5

From above, $\bar{V}_o = j80 \text{ V}$, so $\theta = 90^\circ$

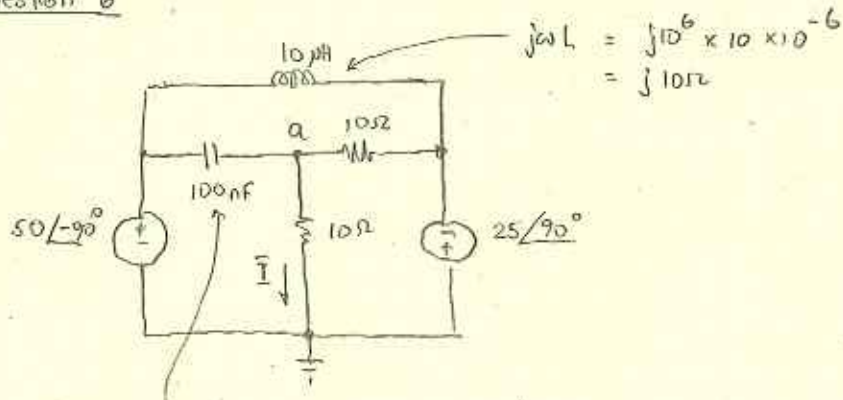Question 6

$$\frac{1}{j\omega C} = \frac{1}{j(10^6 \times 100 \times 10^{-9})} = -j10 \Omega$$

$$\text{Node a: } \frac{\bar{V}_a - 50\angle-90^\circ}{-j10} + \frac{\bar{V}_a}{10} + \frac{\bar{V}_a - (-25\angle90^\circ)}{10} = 0$$

$$\text{or } \frac{\bar{V}_a + j50}{-j10} + \frac{\bar{V}_a}{10} + \frac{\bar{V}_a + j25}{10} = 0$$

(x 10)

$$j(\bar{V}_a + j50) + \bar{V}_a + \bar{V}_a + j25 = 0$$

$$j\bar{V}_a - 50 + 2\bar{V}_a + j25 = 0$$

$$\bar{V}_a(2 + j) = 50 - j25$$


$$\bar{V}_a = \frac{50 - j25}{2 + j} \times \frac{2 - j}{2 - j} = \frac{50 - j50 - j50 + 25}{4 + 2j - 2j + 1}$$

$$= \frac{75 - j100}{5} = 15 - j20$$

The phasor current \bar{I} is simply $\bar{I} = \frac{\bar{V}_a}{10}$

$$\text{so } \bar{I} = 1.5 - j2$$

$$\bar{I} = 2.5 \angle -53.13^\circ$$

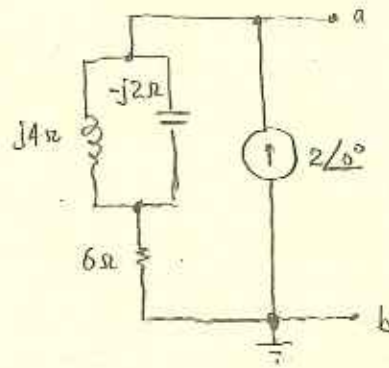
Question 7

We may solve for the Thevenin impedance first. Zeroing the current source, we get

$$Z_T = (j4 \parallel -j2) + 6 \, \Omega$$

$$= \frac{j4 \times -j2}{j4 + -j2} + 6 = \frac{8}{j2} + 6 = 6 - j4 \, \Omega$$

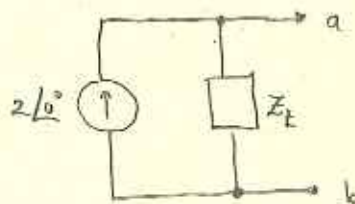This will give us Norton equivalent circuit



$$\text{so } \bar{V}_T = 2 \angle 0^\circ \times Z_T$$

$$= 2 \times (6 - j4)$$

$$= 12 - j8 \, \text{V}$$

$$= 14.422 \angle -33.69^\circ$$

Question 8

From above, the Thevenin impedance is $Z_T = 6 - j4$

$$= 7.211 \angle -33.69^\circ$$