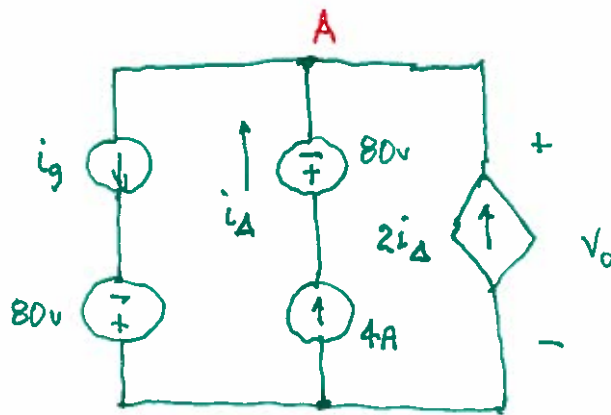


Example 2: For the following circuit, let $V_0 = 100\text{ V}$, and find the total power in the circuit using KVL, KCL.



Solution: We need all voltages and currents


Apply KCL at node A: $i_A + 2i_A - i_g = 0$

We know $i_A = 4\text{ A}$

so $4 + 2 \times 4 - i_g = 0$

$\therefore i_g = 12\text{ A}$

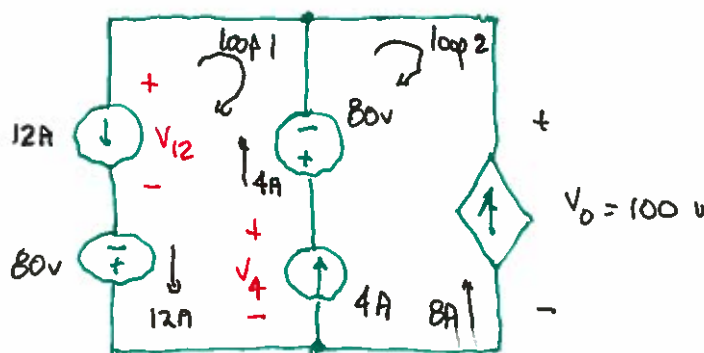Redraw and add our own labels for loops and unknown voltages



We know all the currents; have two unknown voltages V_{12} , V_4 .

KVL around loop 2: $-V_4 + 80 + 100 = 0$

$\therefore V_4 = 180\text{ V}$

KVL around loop 1: $80 - V_{12} - 80 + V_4 = 0$

$\therefore V_{12} = V_4 = 180\text{ V}$

Now find power (using passive reference convention)


<u>element</u>	<u>power</u>
12 A	$p = v_i = V_{12} \times 12 = 2160 \text{ W}$
left 80v	$p = -v_i = -80 \times 12 = -960 \text{ W}$
middle 80v	$p = v_i = 80 \times 4 = 320 \text{ W}$
4A	$p = -v_i = -V_4 \times 4 = -720 \text{ W}$
dependent	$p = -v_i = -100 \times 8 = -800 \text{ W}$
<hr/>	
0 W (energy balance!)	

RESISTIVE CIRCUITS

KVL, KCL, and Ohm's Law give us all the tools we need to begin circuit analysis.

Resistances in series and parallel

Series resistances:

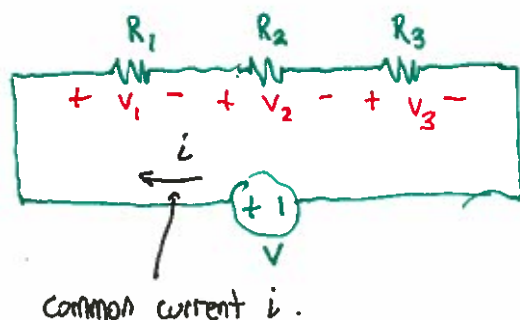

Ohm's Law


$$V = iR$$

By KVL, we have $-V + V_1 + V_2 + V_3 = 0$

$$-V + iR_1 + iR_2 + iR_3 = 0$$


$$\text{so } V = i(R_1 + R_2 + R_3)$$

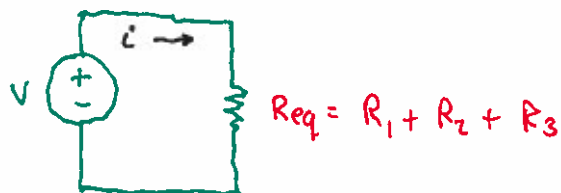Can replace with a single equivalent resistance R_{eq}



→ Resistances in series add

Parallel resistances:

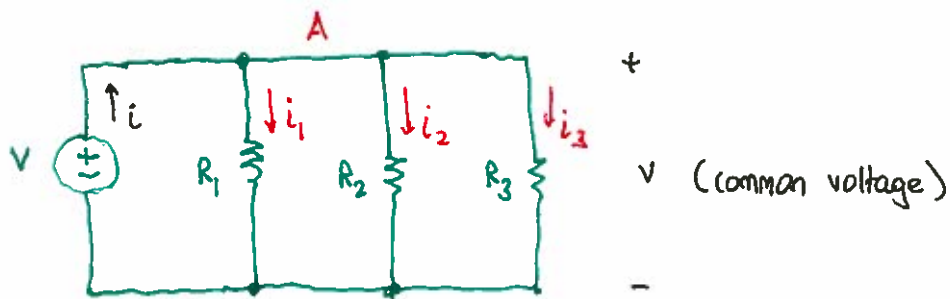

By KCL at node A, $i - i_1 - i_2 - i_3 = 0$

and Ohm's Law,

$$i - \frac{V}{R_1} - \frac{V}{R_2} - \frac{V}{R_3} = 0$$

$$\text{so } i = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = V (G_1 + G_2 + G_3)$$


→ Conductances in parallel add

$$\text{or } V = i \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

Very common resistor configuration:

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$

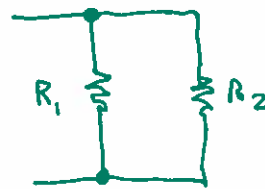

Example: Find a single equivalent resistance for

