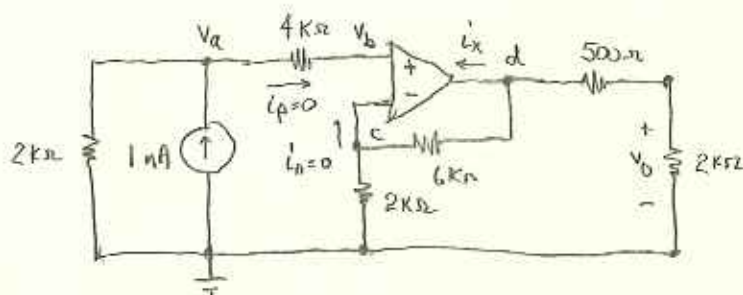


Question 1



At node a: $\frac{V_a}{2k} - 0.001 + i_p^o = 0$
 so $V_a = 2v$

This is also the voltage V_b and V_c : $V_a = V_b = V_c = 2$

At node c: $\frac{V_c}{2k} + \frac{V_c - V_d}{6k} + i_n^o = 0$
 ($\times 6k$) $3V_c + V_c - V_d = 0$

so $V_d = 4V_c = 4(2) = 8v$

At V_o , we have a simple voltage divider

$V_o = \frac{2k}{2k + 500} \times V_d = 0.8 \times 8$

$V_o = 6.4v$

Question 2


At node d in the diagram above,

$\frac{V_d - V_c}{6k} + i_x + \frac{V_d - V_o}{500} = 0$, where $V_d = 8v$,
 $V_c = 2v$,
 $V_o = 6.4v$
 $\times (6k)$ $V_d - V_c + 6000i_x + 12V_d - 12V_o = 0$
 $8 - 2 + 6000i_x + 96 - 76.8 = 0$
 $6000i_x = -25.2$

$i_x = -4.2mA$

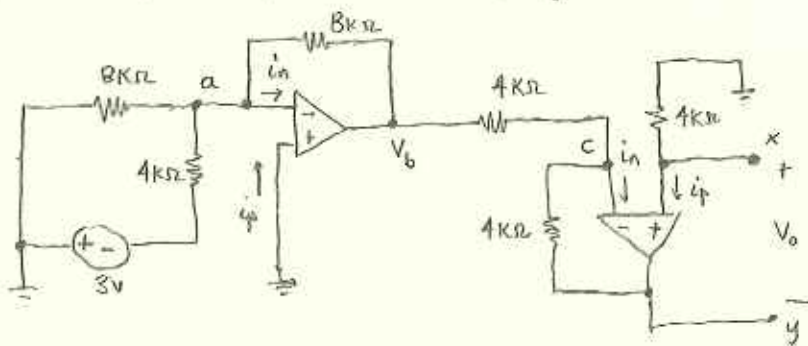Question 3

Zeroing all sources except the 3v source gives



We see that the voltage at node $V_a = 0$. Applying the node-voltage method, we may find V_b

$$\frac{V_a}{8k} + \frac{V_a - (-3)}{4k} + \cancel{I_0} + \frac{V_a - V_b}{8k} = 0$$

$$\begin{aligned} \text{With } V_a &= 0, & \frac{3}{4k} - \frac{V_b}{8k} &= 0 \\ (\times 8k) & & 6 - V_b &= 0 \end{aligned}$$

$$V_b = 6.$$

In the second op-amp, we see that $V_C = 0$ as well. Writing a node equation there will give us V_y

$$\frac{V_c - V_D}{4k} + \frac{V_c - V_y}{4k} + i_n = 0$$

$$\text{or } -\frac{V_d}{4k} - \frac{V_y}{4k} = 0$$


giving $V_g = -V_b = -6\text{V}$.

With V_x also at zero volts

$$V_o' = V_x - V_y = 0 - (-6)$$


$$V_0' = 6 \text{ V}$$

Question 4

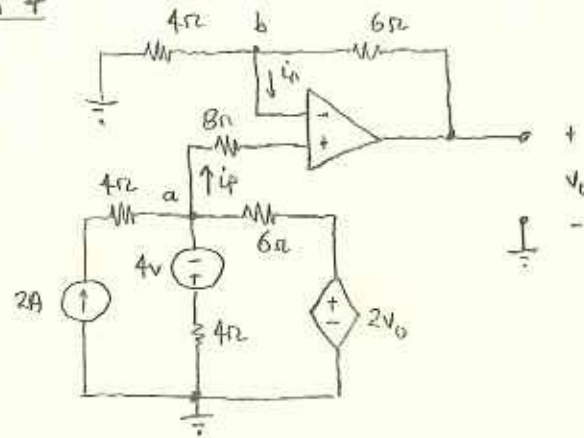

Two node equations, one at a , the other at b , should do it.

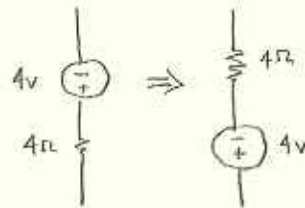Node a : Notice the middle branch. We could make a supernode there, but we could also make a slight modification



$$-2 + \frac{V_a - (-4)}{4} + \frac{V_a - 2V_o}{6} + i_p^0 = 0$$

$$\begin{aligned} (\times 12) \quad -24 + 3V_a + 12 + 2V_a - 4V_o &= 0 \\ 5V_a - 4V_o &= 12 \end{aligned}$$

$$\text{so } V_a = \frac{12 + 4V_o}{5} \quad (1)$$

$$\text{Node } b: \quad \frac{V_b}{4} + \frac{V_b - V_o}{6} = 0$$

$$\begin{aligned} (\times 12) \quad 3V_b + 2V_b - 2V_o &= 0 \\ 5V_b &= 2V_o \end{aligned}$$

Substituting equation (1) for V_o , and with $V_a = V_b$,


$$\begin{aligned} 5V_a &= 2V_o \\ 5 \left(\frac{12 + 4V_o}{5} \right) &= 2V_o \end{aligned}$$

$$12 + 4V_0 = 2V_0$$

$$-2V_0 = 12$$

$$V_0 = -6 \text{ V}$$

Question 5

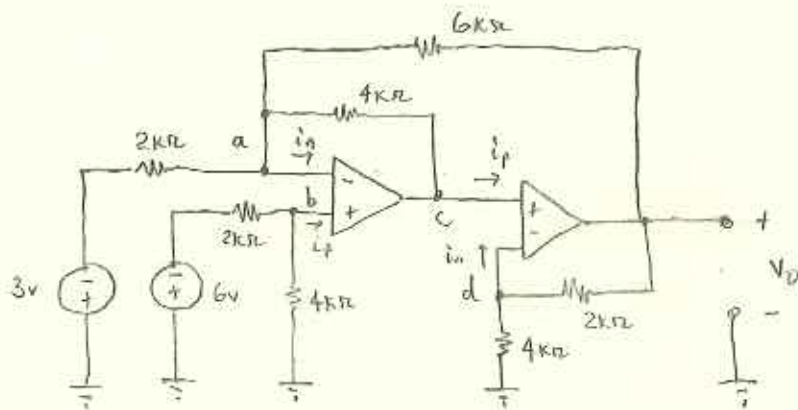

Remember: op-amp input nodes are perfect for writing node-voltage equations.

$$\text{Node } a: \frac{V_a - (-3)}{2\text{k}} + \frac{V_a - V_c}{4\text{k}} + i_n^0 + \frac{V_a - V_0}{6\text{k}} = 0$$

$$(\times 12) \quad 6V_a + 18 + 3V_a - 3V_c + 2V_a - 2V_0 = 0$$

$$11V_a - 3V_c - 2V_0 = -18 \quad (1)$$

$$\text{Node } b: \frac{V_b - (-6)}{2\text{k}} + \frac{V_b}{4\text{k}} + i_p^0 = 0$$

$$(\times 4\text{k}) \quad 2V_b + 12 + V_b = 0$$

$$3V_b = -12$$

$$V_b = -4 \text{ V}$$

And since, $V_a = V_b$, equation (1) becomes

$$11(-4) - 3V_c - 2V_0 = -18$$

$$-3V_c - 2V_0 = 26 \quad (2)$$

$$\text{Node } d: \frac{V_d}{4\text{k}} + \frac{V_d - V_0}{2\text{k}} + i_n^0 = 0$$

$$(\times 4\text{k}) \quad V_d + 2V_d - 2V_0 = 0$$

$$3V_d - 2V_0 = 0 \quad (3)$$

And we see that $V_d = V_c$, so equation (3) becomes

$$3V_c - 2V_o = 0$$

$$\text{or } V_c = \frac{2}{3} V_o$$


Substitute back into (2),

$$-3\left(\frac{2}{3} V_o\right) - 2V_o = 26$$

$$-2V_o - 2V_o = 26$$

$$\boxed{V_o = -6.5 \text{ V}}$$

Question 6

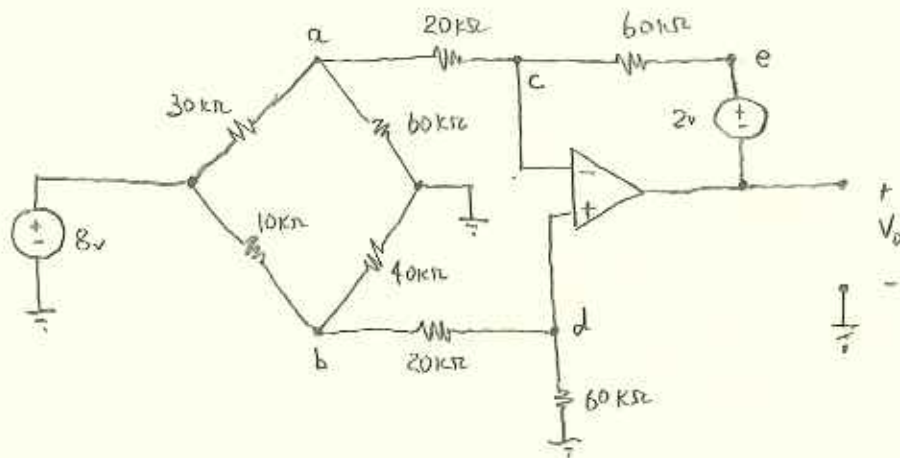

Node-voltage method.

$$\text{Node } a: \frac{V_a - 8}{30K} + \frac{V_a}{60K} + \frac{V_a - V_c}{20K} = 0$$

$$(\times 60K) \quad 2V_a - 16 + V_a + 3V_a - 3V_c = 0$$

$$6V_a - 3V_c = 16 \quad (1)$$

$$\text{Node } b: \frac{V_b - 8}{10K} + \frac{V_b}{40K} + \frac{V_b - V_d}{20K} = 0$$

$$(\times 40K) \quad 4V_b - 32 + V_b + 2V_b - 2V_d = 0$$

$$7V_b - 2V_d = 32 \quad (2)$$

Node d: $\frac{V_d - V_b}{20k} + \frac{V_d}{60k} + \cancel{j_p} = 0$
 (x 60k) $3V_d - 3V_b + V_d = 0$
 $4V_d = 3V_b$

so $V_d = \frac{3}{4}V_b$ (3)

We see that $V_d = V_c$, so $V_c = \frac{3}{4}V_b$

Substitute this into equation (1)

$$6V_a - 3\left(\frac{3}{4}V_b\right) = 16$$

$$6V_a - \frac{9}{4}V_b = 16 \quad (4)$$

Same substitution into equation (2)

$$7V_b - 2\left(\frac{3}{4}V_b\right) = 32$$

$$5.5V_b = 32$$

$$\text{so } V_b = 5.818 \text{ v}$$

From (1), $6V_a - 3V_c = 16$, so $V_a = \frac{16 + 3V_c}{6}$ (5)

With $V_b = 5.818$, then $V_d = \frac{3}{4}V_b = 4.3636$

$$V_c = V_d = 4.3636 \text{ v}$$

and $V_a = \frac{16 + 3V_c}{6} = 4.8485$

One more node!

Node c: $\frac{V_c - V_a}{20k} + \frac{V_c - V_e}{60k} + \cancel{j_n} = 0$
 (x 60k) $3V_c - 3V_a + V_c - V_e = 0$

$$V_e = 4V_c - 3V_a$$

$$= 4(4.3636) - 3(4.8485) = 2.9091$$


Finally, From node e to V_o , there is 2v drop through the voltage source

$$V_o = V_e - 2v = \boxed{0.9091 \text{ v}}$$

Question 7

This is easiest to break into parts.

(a) lower-left part:

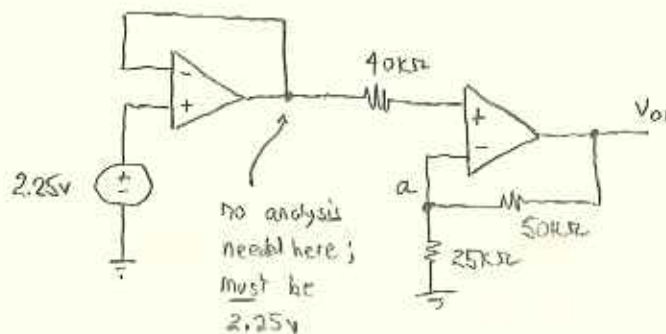


$$\text{Node a: } \frac{V_a}{25k} + \frac{V_a - V_{o1}}{50k} + i_n = 0$$

$$(\times 50k) \quad 2V_a + V_a - V_{o1} = 0$$

$$V_{o1} = 3V_a$$

And we know $V_a = 2.25$, so $V_{o1} = 6.75V$

(b) upper-left part

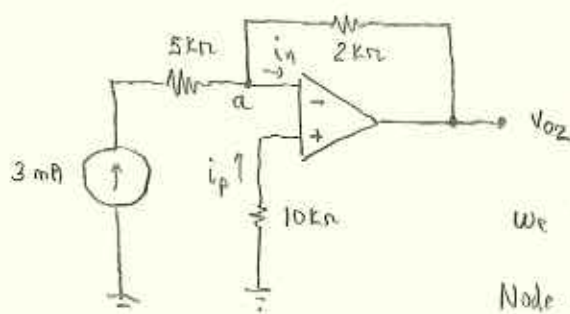


We know $V_a = 0$

$$\text{Node a: } -0.003 + \frac{V_a - V_{o2}}{2k} + i_n = 0$$

$$(\times 2k) \quad -6 - V_{o2} = 0$$

$$V_{o2} = -6V$$

(c) top-right part

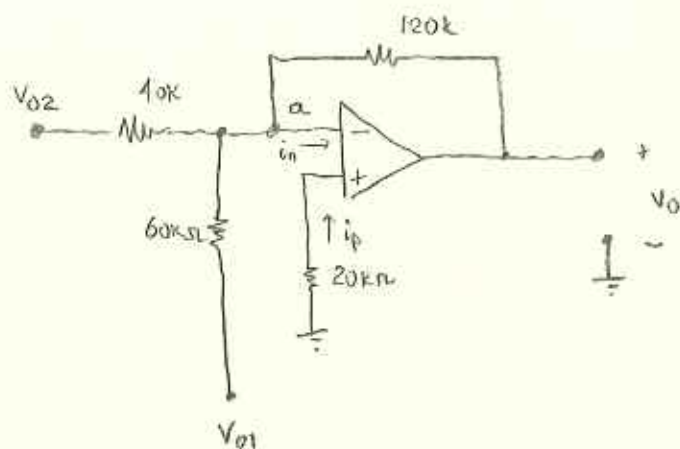

Once again, we see $V_a = 0$

$$\text{Node } a: \frac{V_a - V_{02}}{10k} + \frac{V_a - V_{01}}{60k} + \frac{V_a - V_o}{120k} + i_p = 0$$

$$(\times 120k) \quad 3V_a - 3V_{02} + 2V_a - 2V_{01} + V_a - V_o = 0$$

$$6V_a - 2V_{01} - 3V_{02} = V_o$$

$$V_o = 6 \times 0 - 2(6.75) - 3(-6)$$

$$\boxed{V_o = 4.5v}$$

AMPAD