

Question 1

The average power in a resistor is determined in terms of rms voltage and current.

$$P = \bar{i}_{rms}^2 R \quad \text{or} \quad P = V_{rms} i_{rms} \quad \text{or} \quad P = \frac{V_{rms}^2}{R}$$

We have  $i(t) = 2 \cos(120\pi t)$ , so  $i_{rms} = 2/\sqrt{2}$

$$\text{Therefore } P = (2/\sqrt{2})^2 \times 4 \Omega = \boxed{8 \text{ W}}$$

Question 2

For a capacitor,  $\bar{I}_c \rightarrow \begin{array}{c} Z_c \\ \parallel \\ + \bar{V}_c - \end{array}$  where  $Z_c = \frac{1}{j\omega C}$

Here, the phasor current is  $\bar{I}_c = 2 \angle 0^\circ$

$$\begin{aligned} \text{and } Z_c &= \frac{1}{j\omega C} = \frac{1}{j(120\pi \times 400 \times 10^{-6})} \\ &= -j6.6315 \Omega \end{aligned}$$

$$\begin{aligned} \text{so } \bar{V}_c &= Z_c \bar{I}_c = (-j6.6315)(2) \\ &= -j13.2629 \end{aligned}$$


$$\text{therefore } V_c = |\bar{V}_c| = \boxed{13.2629 \text{ V}}$$

Question 3

A sketch often helps:

- Need to convert the time 0.1875 ms into degrees.
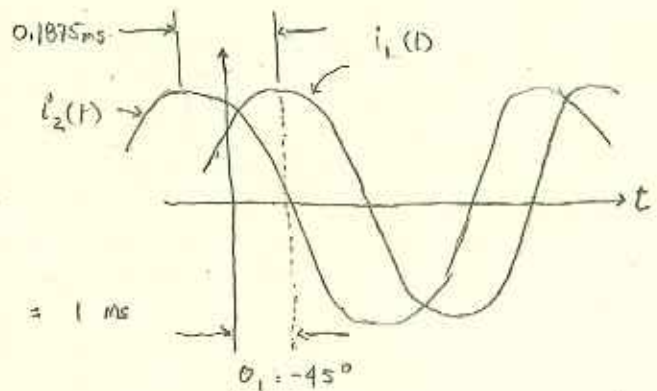
$$\text{One period } T = \frac{1}{f} = \frac{1}{1000} = 1 \text{ ms}$$



Therefore 1 ms of time corresponds to  $360^\circ$  (one complete period)

We have a simple ratio:  $\frac{0.1875 \text{ ms}}{1 \text{ ms}} = \frac{\psi}{360^\circ}$

$$\text{so } \psi = 0.1875 \times 360^\circ = 67.5^\circ$$

So  $i_2(t)$  leads  $i_1(t)$  by  $67.5^\circ$ ,

$$\begin{aligned} \text{Hence } \theta_2 &= \theta_1 + \psi \\ &= -45^\circ + 67.5^\circ \end{aligned}$$

$$\boxed{\theta_2 = 22.5^\circ}$$

#### Question 4

The voltage phasor  $\tilde{V}_1 = 30 \angle 30^\circ$ , so peak amplitude is 30


The current phasor has an RMS amplitude of 10, and leads  $\tilde{V}_1$  by  $40^\circ$ , so  $\tilde{I}_1$ 's phase is  $30^\circ + 40^\circ = 70^\circ$

$$\text{The peak amplitude of } \tilde{I}_1 = \sqrt{2} \times 10 = 14.14 \text{ A}$$

The current phasor is  $14.14 \angle 70^\circ$

Answer is (c)

#### Question 5

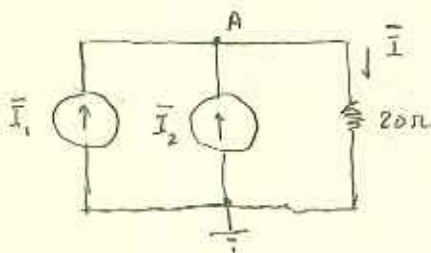

A node-voltage equation at A

$$-\tilde{I}_1 - \tilde{I}_2 + \tilde{I} = 0$$

$$\text{so } \tilde{I}_2 = \tilde{I} - \tilde{I}_1$$

We are given  $\tilde{I}_1 = 10 \angle 45^\circ$  and  $\tilde{I} = 8 \angle 30^\circ$

$$\begin{aligned} \text{so } \tilde{I}_2 &= 8 \angle 30^\circ - 10 \angle 45^\circ \\ &= (6.9282 + j4) - (7.0711 + j7.0711) \\ &= -0.14286 - j3.07107 \end{aligned}$$

$$\tilde{I}_2 = 3.07439 \angle -92.663^\circ, \quad \text{so}$$

$$\boxed{\theta_2 = -92.663^\circ}$$

Question 6

From above, the peak amplitude of  $i_2(t)$  was found to be

$$|I_2| = 3.07439 \text{ A}$$

And its rms value  $|\bar{I}_{2,rms}| = 3.07439/\sqrt{2} = \boxed{2.1739 \text{ A}}$

Question 7

We have  $\bar{V} = 400 \angle 120^\circ$  and  $\bar{I} = 5 \angle 30^\circ$

Therefore, the impedance must be  $Z = \bar{V}/\bar{I}$

$$Z = \frac{400 \angle 120^\circ}{5 \angle 30^\circ} = 80 \angle 90^\circ \Omega$$

or  $Z = j80 \Omega$

Since this purely imaginary and positive, it is inductive impedance

$$Z_L = j\omega L = j80 \Omega$$

We are given  $\omega = 100 \text{ rad/sec}$ , so

$$\omega L = 80$$

$$100L = 80$$

giving  $\boxed{L = 0.8 \text{ H}}$