
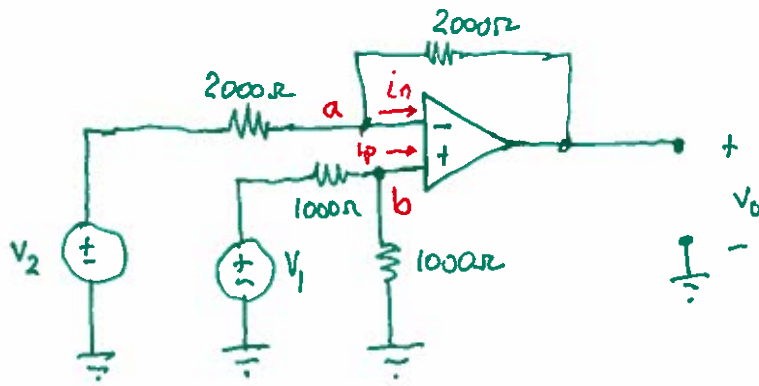


Friday, March 4, 2016

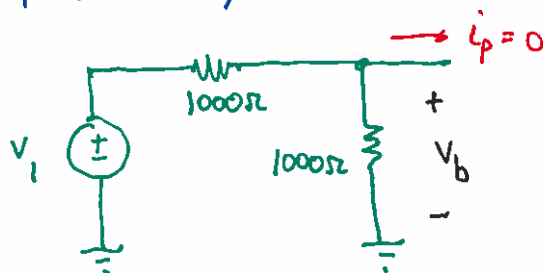Example 2: a differential amplifier - solve for V_o



Start with what we know for sure. At the op-amp's '+' terminal, by our previous analysis.



Since $i_p = 0$, resistors are in series, \rightarrow voltage divider.

This means $V_a = V_b = \frac{1000}{1000 + 1000} V_1 = \frac{1}{2} V_1$ (1)

At node a:

$$\frac{V_a - V_2}{2000} + \frac{V_a - V_o}{2000} + \cancel{i_n} = 0$$

$$(\times 2000) \quad V_a - V_2 + V_a - V_o = 0$$


$$\text{So } V_o = 2V_a - V_2$$

Substitute equation (1)

$$V_o = 2 \left(\frac{1}{2} V_1 \right) - V_2$$

$$V_o = V_1 - V_2$$

Example 3: A more tricky example!

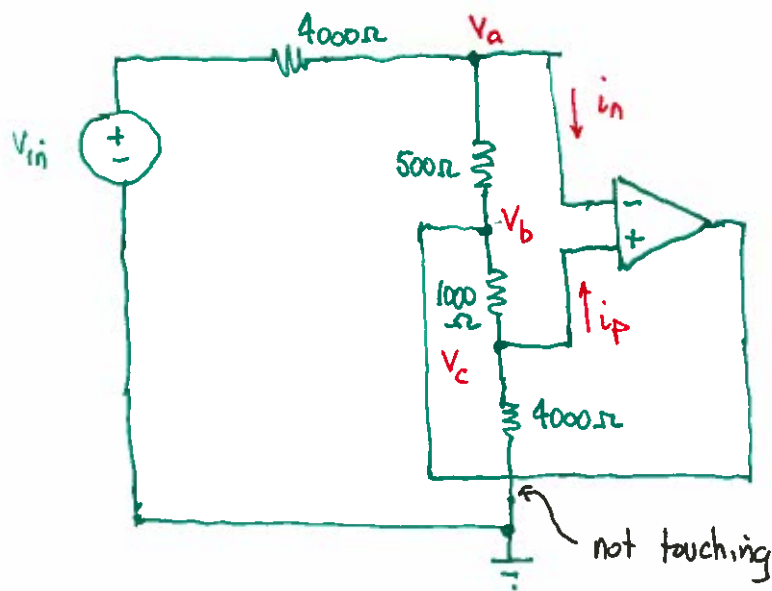

Find V_a .

As always, the most interesting things happen at the op-amp's input terminals.

$$\text{Node a: } \frac{V_a - V_{in}}{4000} + \cancel{i_{in}} + \frac{V_a - V_b}{500} = 0 \quad (1)$$

From the summing-point constraints, we also know $V_a = V_c$.

We have two unknowns: V_a, V_b

$$\text{Node c: } \frac{V_c - V_b}{1000} + \cancel{i_p} + \frac{V_c}{4000} = 0$$

$$\text{so } \frac{V_a - V_b}{1000} + \frac{V_a}{4000} = 0$$

($\times 4000$)

$$4V_a - 4V_b + V_a = 0$$

$$5V_a = 4V_b, \quad \text{so } V_b = \frac{5}{4}V_a \quad (2)$$

Substitute into (1)

$$\frac{V_a - V_{in}}{4000} + \frac{V_a - \frac{5}{4}V_a}{500} = 0$$


$$(\times 4000) \quad V_a - V_{in} + 8V_a - 8\left(\frac{5}{4}V_a\right) = 0$$

$$V_a(1+8-10) = V_{in}$$

$$\therefore V_a = -V_{in}$$

(Notice we didn't need to write an equation at b.)

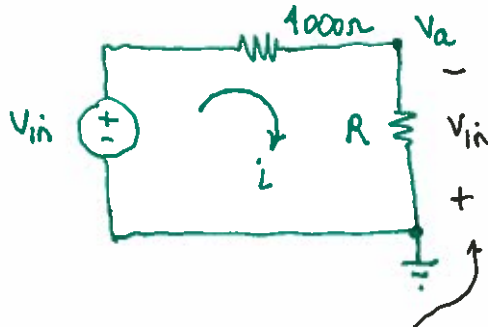The op-amp circuit is emulating a negative resistance!



backwards to
Ohm's law?


$$i = \frac{V_{in} - (-V_{in})}{1000}$$

$$= \frac{2V_{in}}{1000}$$

$$\text{and } R = \frac{V_a}{i} = -\frac{V_{in}}{i}$$

$$= \frac{-V_{in}}{\left(\frac{2V_{in}}{1000}\right)} = -2000\Omega$$

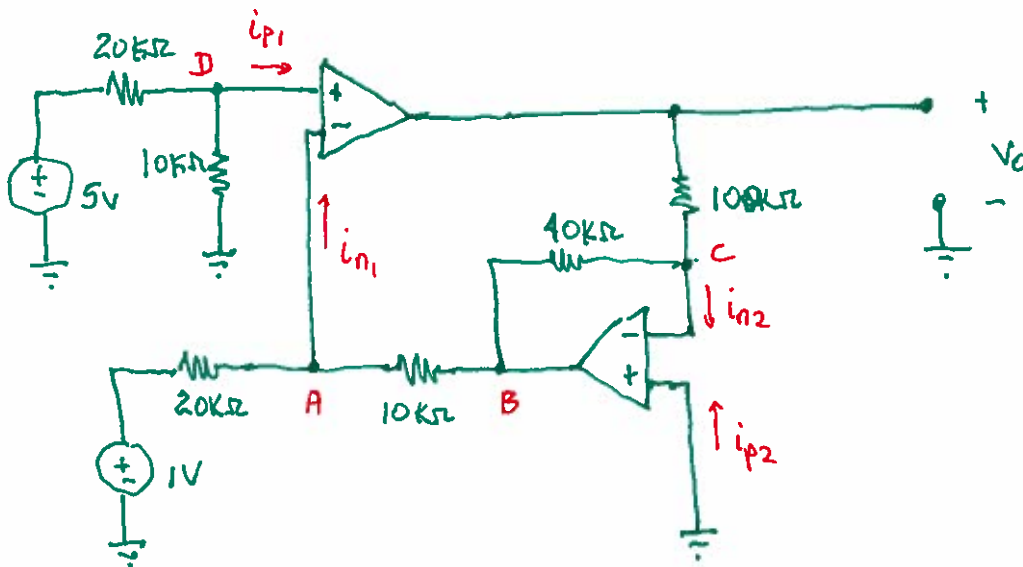Example 4: Trickier still - a two op-amp problem



Find V_o .

What the summing-point constraints give us:

Upper op-amp: $i_{n1} = 0$, so we have a simple voltage divider