

We have $\bar{V} = 10 \angle 0^\circ$. Phasor current is

Wednesday, March 23,
2016

$$\begin{aligned}\bar{I} &= \frac{\bar{V}}{Z_R + Z_C + Z_L} = \frac{10 \angle 0^\circ}{10 - j20 + j10} \\ &= \frac{10}{10 - j10}\end{aligned}$$


Expressing in standard complex form ($a + jb$)

$$\begin{aligned}\bar{I} &= \frac{10}{10 - j10} \times \frac{10 + j10}{10 + j10} = \frac{100 + j100}{100 - j100 + j100 - j^2 100} \\ &= \frac{100 + j100}{200} \\ &= 0.5 + j0.5\end{aligned}$$

Now, we need \bar{V}_L . By the phasor equivalent of Ohm's law

$$\begin{aligned}\bar{V}_L &= Z_L \bar{I} = j10 \times (0.5 + j0.5) \\ &= j5 + j^2 5 \\ &= -5 + j5\end{aligned}$$

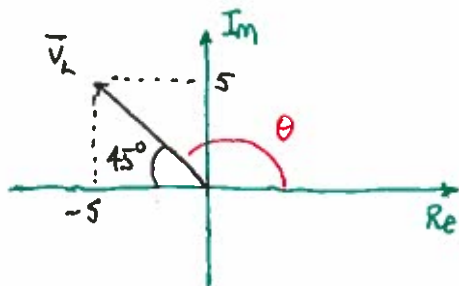
Expressed in polar form $V_L = \sqrt{5^2 + 5^2} = 5\sqrt{2}$




$$\theta = 180^\circ - 45^\circ = 135^\circ$$

$$\text{so } v_L(t) = 5\sqrt{2} \cos(100t + 135^\circ)$$

Phasor diagram:

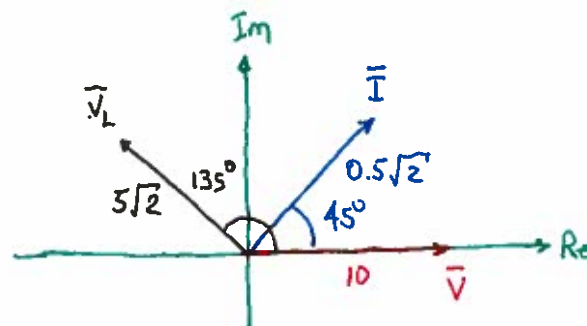

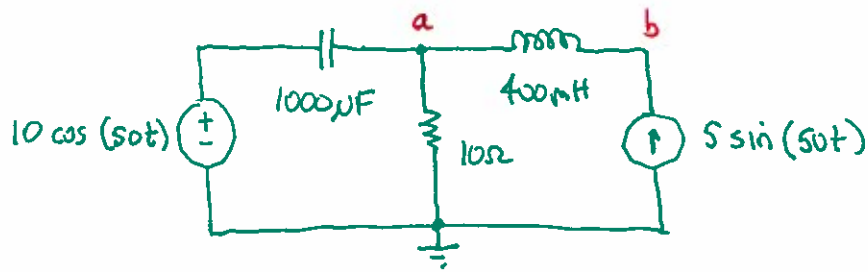
Example 2: Node-voltage method. Find $V_a(t)$ and $V_b(t)$



In terms of complex impedances,

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(50 \times 1000 \times 10^{-6})} = -j20 \Omega$$
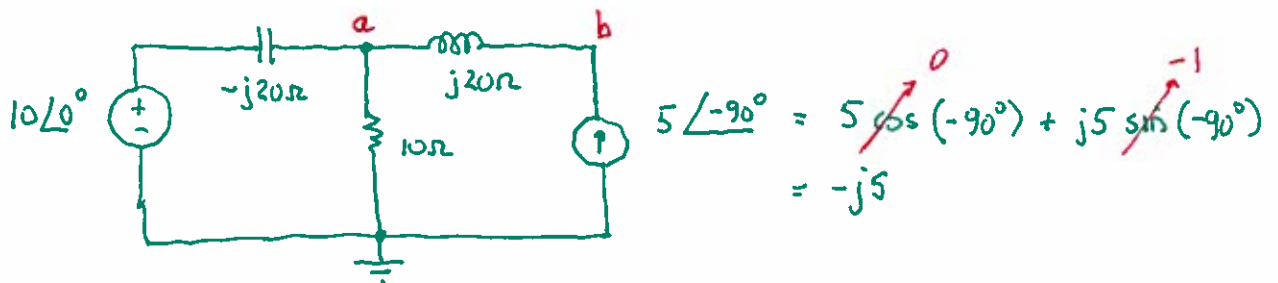
$$Z_L = j\omega L = j(50 \times 400 \times 10^{-3}) = j20 \Omega$$



$$\text{Node } a: \frac{\bar{V}_a - 10}{-j20} + \frac{\bar{V}_a}{10} + \frac{\bar{V}_a - \bar{V}_b}{j20} = 0$$

$$(\times j20) \quad -(\bar{V}_a - 10) + 2j\bar{V}_a + \bar{V}_a - \bar{V}_b = 0$$

$$2j\bar{V}_a - \bar{V}_b = -10$$

(1)

$$\text{Node } b: \frac{\bar{V}_b - \bar{V}_a}{j20} - 5 \angle -90^\circ = 0$$

$$\frac{\bar{V}_b - \bar{V}_a}{j20} + j5 = 0$$

$$(\times j20) \quad \bar{V}_b - \bar{V}_a + j^2 100 = 0$$

$$\bar{V}_b - \bar{V}_a = 100$$

(2)

Add (1) and (2)

$$2j\bar{V}_a - \bar{V}_b = -10$$

$$-\bar{V}_a + \bar{V}_b = 100$$

$$\hline (-1 + j2)\bar{V}_a = 90$$

Therefore, $\bar{V}_a = \frac{90}{-1+j2}$

Put in standard complex form,

$$\bar{V}_a = \frac{90}{-1+j2} \times \frac{-1-j2}{-1-j2} = \frac{-90 - j180}{1 + j2 - j2 - j^2 4}$$


$$= \frac{-90 - j180}{5} = -18 - j36$$

And from (2) $\bar{V}_b - \bar{V}_a = 100$

$$\bar{V}_b + 18 + j36 = 100$$

$$\text{so } \bar{V}_b = 82 - j36$$

Phasor solutions:

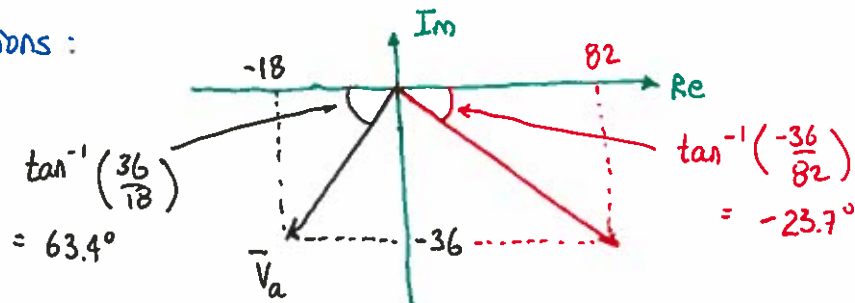

$$\bar{V}_a = -18 - j36 = 40.25 \angle -(180 - 63.4^\circ) = -116.6^\circ$$


$$\bar{V}_b = 82 - j36 = 89.55 \angle -23.7^\circ$$

so back in the time domain

$$V_a(t) = 40.25 \cos(50t - 116.6^\circ)$$

$$V_b(t) = 89.55 \cos(50t - 23.7^\circ)$$

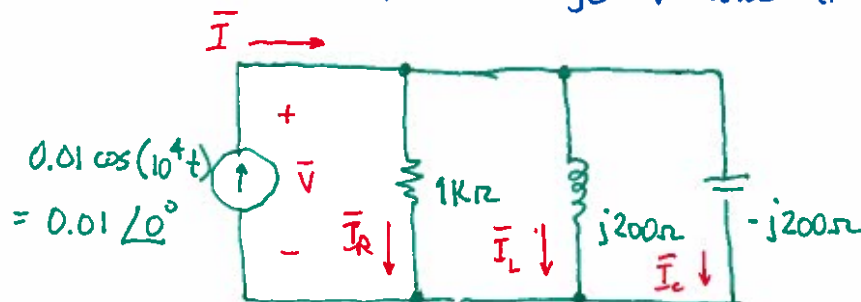Example 3: Find phasor voltage \bar{V} and all phasor currents.



We could find the total impedance Z_{eq} , starting with $Z_C // Z_L$

$$Z_C // Z_L = \frac{j200 \times -j200}{j200 - j200} = \infty$$

- Inductive impedance cancels capacitive impedance! (called resonance)