

## KCL (continued)


Wednesday, January 27, 2016  
(morning)

From our previous example at node A

$$\underbrace{i_1 + i_2}_{\text{entering node A}} - \underbrace{i_3}_{\text{leaving node A}} = 0$$

so  $i_3 = i_1 + i_2$  (common-sense interpretation: what goes in must come out!)


Example: Determine  $i_1$

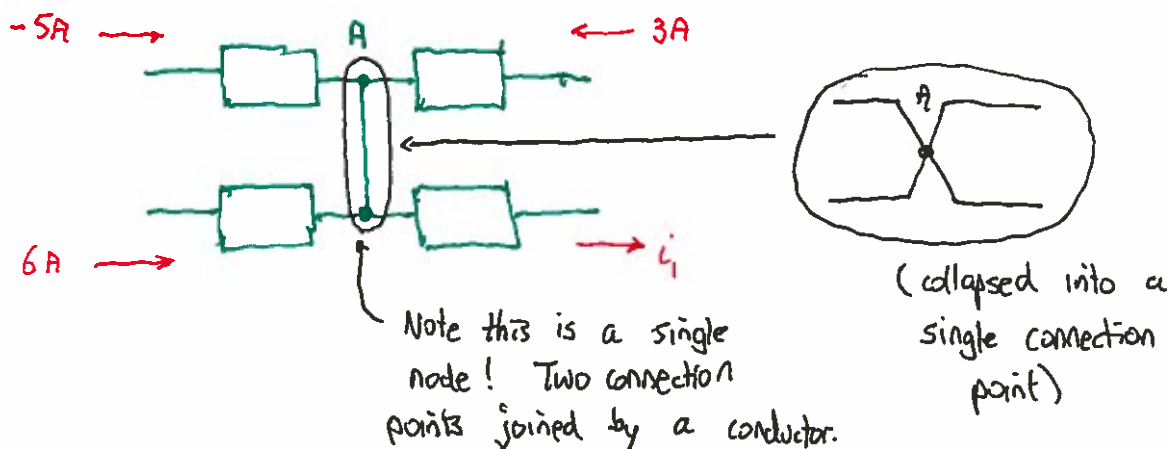

$$\text{KCL at node A: } \underbrace{-5 + 6 + 3}_{\text{entering}} - \underbrace{i_1}_{\text{leaving}} = 0$$

Series circuits:

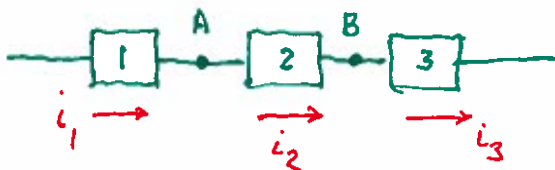This is a very common and important circuit configuration.



nodes A and B each join exactly two circuit elements.


$$\text{KCL at node A: } i_1 - i_2 = 0, \quad i_1 = i_2$$

$$\text{node B: } i_2 - i_3 = 0, \quad i_2 = i_3$$

Circuit elements in series all have the same current

$$i_1 = i_2 = i_3$$


Circuits that violate KCL

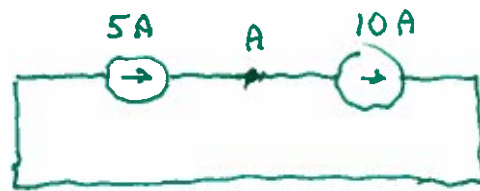

Must have the same current when in series. At Node A:

$$5 - 10 \neq 0$$

Example: What's in series here?

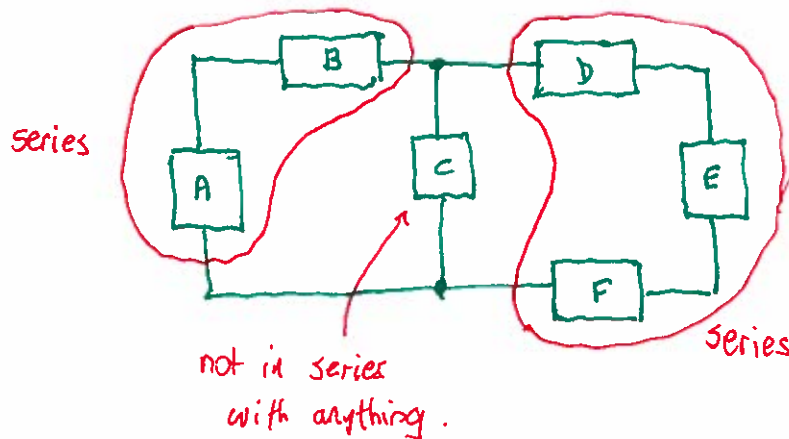


Examine all connection points (nodes), and identify ones at which only two circuit elements are joined.

Kirchoff's voltage Law (KVL)

Derives from conservation of energy.

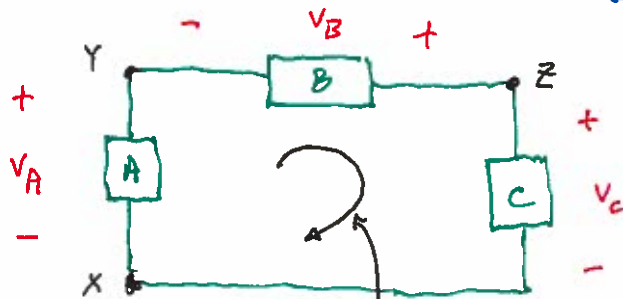Consider circuit elements in a closed loop




loop: a closed path starting at a node and finishing back at the same node.

$$X \rightarrow Y \rightarrow Z \rightarrow X$$

KVL states:

Algebraic sum of all voltages around a loop must be zero

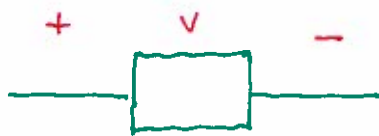Choose a consistent way to sum voltages. By convention:



Add  $V$

direction of travel  
around the loop




Subtract  $V$


Therefore, KVL around our above loop gives

$$-V_A - V_B + V_C = 0$$

Circuits that violate KVL.

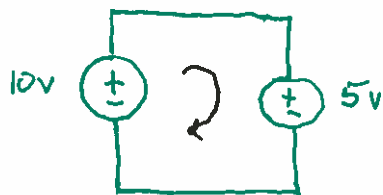


$$-10 + 5 \neq 0$$

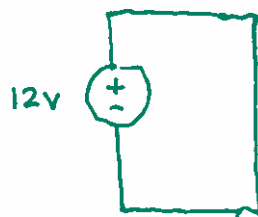

$$-12 \neq 0$$

KVL and power and energy

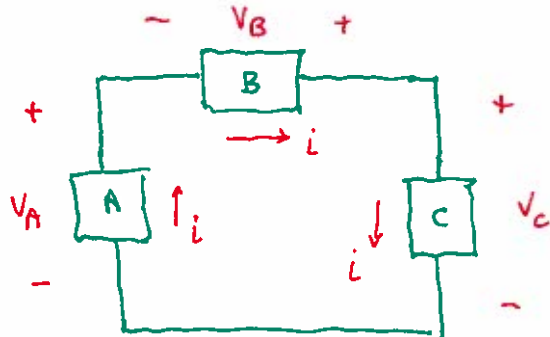

There must be at all times energy balance (generated must equal absorbed). Hence at any time, net power must be zero.

Circuit element

power

A

$-V_A i$

B

$-V_B i$

C

$V_C i$

} Using passive  
reference convention

$$-V_A i - V_B i + V_C i = 0$$

$$\text{or } i(-V_A - V_B + V_C) = 0$$

Assuming  $i \neq 0$ ,

$$\boxed{-V_A - V_B + V_C = 0} \quad \text{KVL}$$