
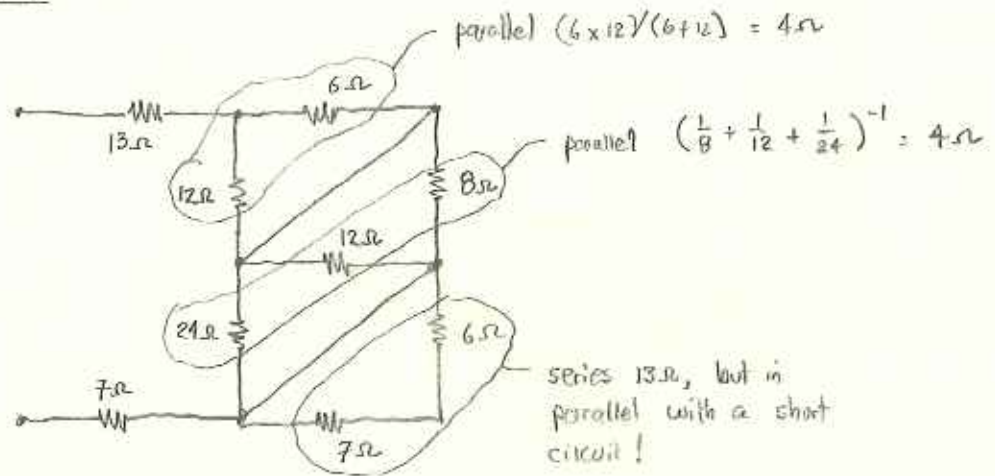



Question 1

Redrawing ...

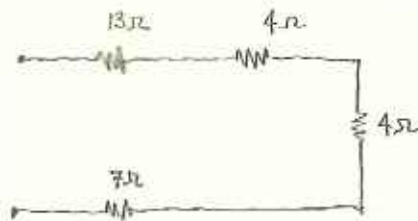

$$R_{eq} = 13 + 4 + 4 + 7$$

$$R_{eq} = 28\Omega$$

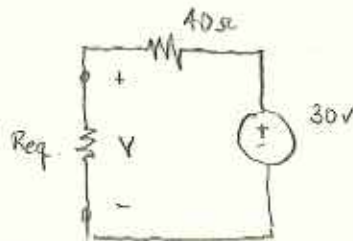Question 2

$$R_{eq} = \left(\frac{1}{60} + \frac{1}{60} + \frac{1}{30} + \frac{1}{90} + \frac{1}{45} \right)^{-1} = 10\Omega$$

By voltage division, $V = \frac{R_{eq}}{R_{eq} + 40} \times 30 = \frac{10}{10 + 40} \times 30$

$$V = 6V$$

Reconstructing the parallel resistor circuit




Then, by Ohm's Law

$$i_1 = -\frac{V}{R} = \frac{-6}{90}$$

$$i_1 = -66.67 \text{ mA}$$

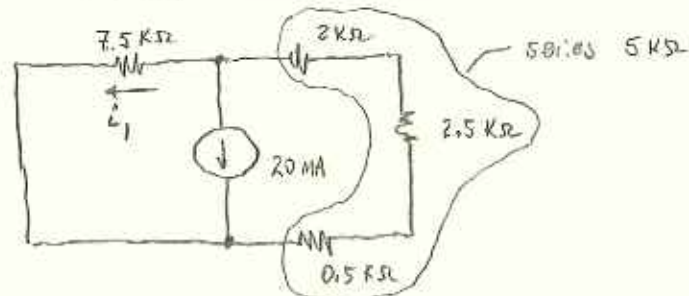Question 3


The two $1\text{ k}\Omega$ resistors at the bottom of the circuit are in parallel, so redrawing ...



Note that i_1 is opposite to the direction of current flow, and then by current division,

$$i_1 = \frac{-5\text{ k}\Omega}{5\text{ k}\Omega + 7.5\text{ k}\Omega} \times 20\text{ mA}$$

$$i_1 = -8\text{ mA}$$

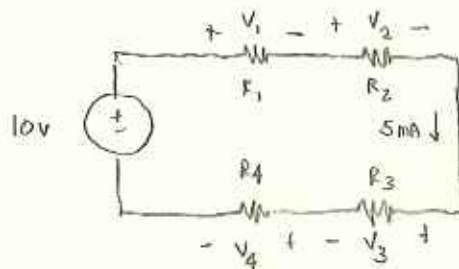Question 4

By KVL, we have $V_1 + V_2 + V_3 + V_4 = 10\text{ V}$.

From the design criteria, we know

$$\begin{aligned} V_3 &= 3V_4 \\ V_2 &= 2V_3 = 6V_4 \\ V_1 &= 5V_2 = 30V_4 \end{aligned}$$

Substituting into the KVL equation,

$$\begin{aligned} 30V_4 + 6V_4 + 3V_4 + V_4 &= 10 \\ 40V_4 &= 10 \end{aligned}$$

$$\text{so } V_4 = 0.25\text{ V}$$

And therefore, $V_1 = 30V_4 = 7.5\text{ V}$




Finally,

$$R_1 = \frac{V_1}{i} = \frac{7.5}{0.005} = 1500 \Omega$$

$$R_1 = 1500 \Omega$$

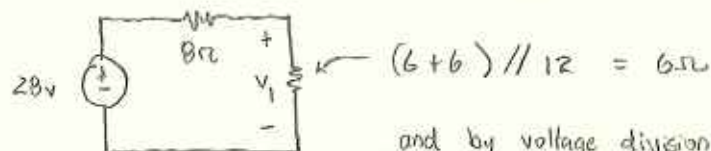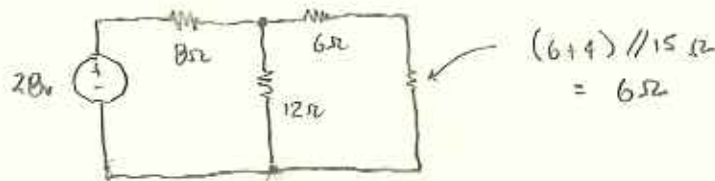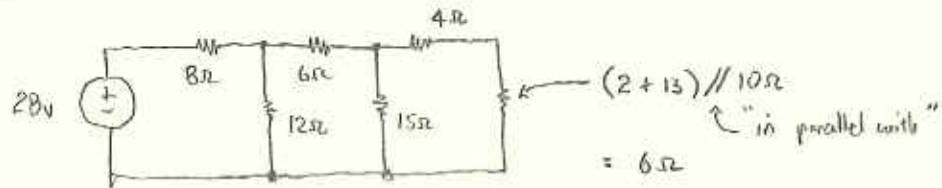Question 5


By combining resistors in series and parallel, we may first simplify the circuit, and then reconstruct it.



and by voltage division $V_1 = \frac{6}{6+8} \times 28$


$$V_1 = 12V$$

Now reconstruct the circuit ...

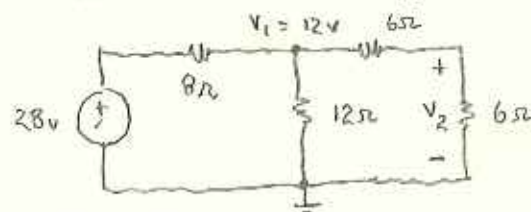


Again by voltage division

$$V_2 = \frac{6}{6+6} \times V_1 = 6V$$

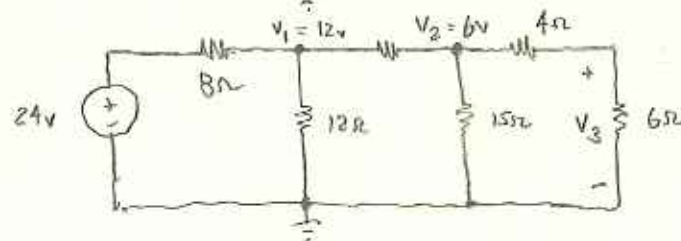

$$V_3 = \frac{6}{6+4} \times V_2 = 3.6V$$


And finally,

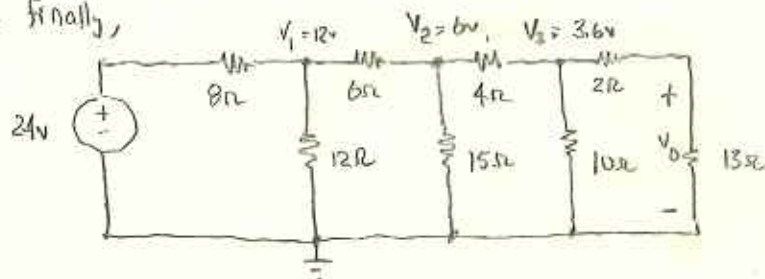

$$V_o = \frac{13}{13+2} \times 3.6$$

$$V_o = 3.12\text{V}$$

Question 6

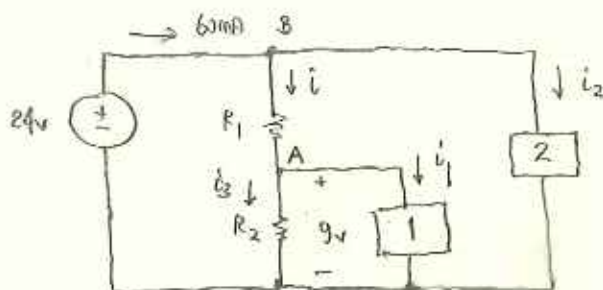

From the specifications given for device 2,

$$p = i_2 V, \text{ where } p = 480 \text{ mW and } V = 24 \text{ V}$$

$$\text{therefore, } i_2 = \frac{480 \text{ mW}}{24 \text{ V}} = 20 \text{ mA}$$

$$\text{By KCL at node B, } i = 60 \text{ mA} - i_2 = 40 \text{ mA.}$$

Then, from the specifications given for device 1,

$$i_1 = \frac{45 \text{ mW}}{9 \text{ V}} = 5 \text{ mA}$$

$$\text{KCL at node A therefore gives } i_3 = i - 5 \text{ mA}$$

$$i_3 = 35 \text{ mA}$$

We now know that R_2 must support 35 mA of current at 9 V.

$$R_2 = \frac{V}{I_3} = \frac{9}{0.035} = 257.14 \Omega$$

$$R_2 = 257.14 \Omega$$

AMPAD