

Similar to the node-voltage method, we can see an important pattern arise when we rearrange this equation:

Monday,  
February 8,  
2016

$$\underbrace{(1200+300)}_{\text{total resistance around mesh a}} i_a - \underbrace{1200}_{\text{resistance shared with mesh b}} i_b - \underbrace{300}_{\text{with } i_c} i_c - \underbrace{15}_{\text{total voltage}} = 0 \quad (1)$$

$$\begin{aligned} \text{Mesh b: } 250(i_b - i_c) + 1200(i_b - i_a) + 1000 i_b &= 0 \\ \text{so } -1200 i_a + 2450 i_b - 250 i_c &= 0 \end{aligned} \quad (2)$$

$$\begin{aligned} \text{Mesh c: } 300(i_c - i_a) + 250(i_c - i_b) + 200 i_c &= 0 \\ \text{so } -300 i_a - 250 i_b + 750 i_c &= 0 \end{aligned} \quad (3)$$

Three equations, 3 unknowns. For power in the  $250\Omega$  resistor,




$$\begin{aligned} P &= i^2 (250) \\ &= (i_c - i_b)^2 \times 250 \end{aligned}$$

### Mesh-current method - special case

As in the node-voltage method, there is one special case we must handle. It is when there is a current source shared by meshes.

Here's one situation:

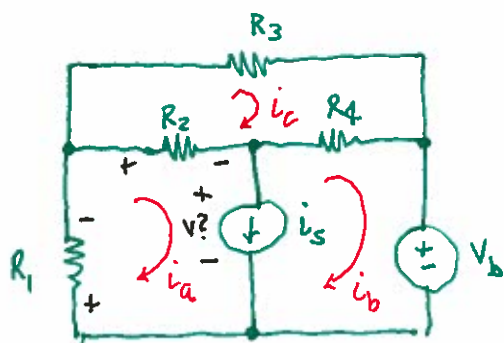

- $i_s$  shared by meshes a and b.

In mesh a, we have an unknown voltage  $V$ .

$$i_a R_1 + (i_a - i_c) R_2 + \textcircled{V} = 0 \quad (1)$$

another unknown


From mesh (b), in terms of the same unknown voltage  $V$ .

$$-V + (i_b - i_c) R_4 + V_b = 0 \quad (2)$$

Adding (1) and (2) eliminates unknown  $V$ .

$$i_a R_1 + (i_a - i_c) R_2 + V - V + (i_b - i_c) R_4 + V_b = 0$$

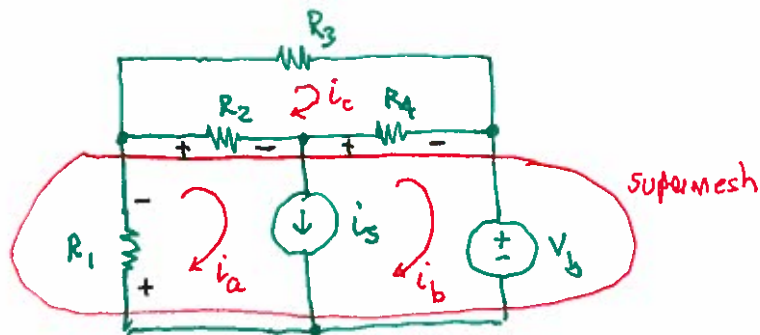We may obtain this equation directly by considering a and b as a supermesh.




We may write a supermesh equation in one step.

$$\underbrace{i_a R_1 + (i_a - i_c) R_2}_{\substack{\text{side of supermesh} \\ \text{in mesh a}}} + \underbrace{(i_b - i_c) R_4 + V_b}_{\substack{\text{side of supermesh} \\ \text{in mesh b}}} = 0$$

SUPERMESH EQUATION.

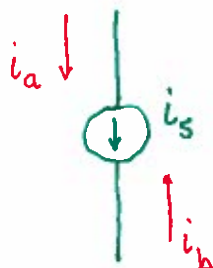
We also have a dependence equation for the two meshes within the supermesh.



$$i_a - i_b = i_s$$

DEPENDENCE EQUATION.

Example 1: Solve for mesh currents.

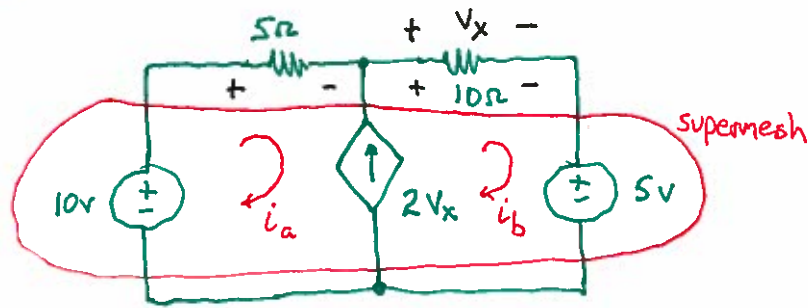

We'll need one supermesh equation and a dependence equation.

Supermesh: 
$$\underbrace{-10 + 5i_a}_{\text{from mesh a}} + \underbrace{10i_b + 5}_{\text{from mesh b}} = 0$$

$$5i_a + 10i_b = 5 \quad (1)$$

Dependence:  $i_b - i_a = 2V_x \quad (2)$

And the dependent current source,

$$V_x = 10i_b \quad (3)$$

Combining (2) and (3)

$$i_b - i_a = 20i_b$$

$$\text{so } i_a = -19i_b$$

Solving (1) and (4)

$$i_b = -0.0588 \text{ A}$$

$$i_a = 1.118 \text{ A}$$