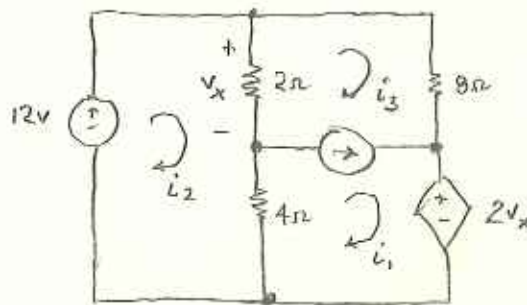


Question 1



$$\text{Mesh } i_2: -12 + 2(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$6i_2 - 4i_1 - 2i_3 = 12 \quad (1)$$

$$\text{Supermesh } i_1, i_3: 4(i_1 - i_2) + 2(i_3 - i_2) + 8i_3 + 2V_x = 0$$

$$4i_1 - 4i_2 + 2i_3 - 2i_2 + 8i_3 + 2V_x = 0$$

$$4i_1 - 6i_2 + 10i_3 + 2V_x = 0 \quad (2)$$

$$\text{The controlling voltage } V_x = 2(i_2 - i_3)$$

$$\text{Substituting this into (2) gives: } 4i_1 - 6i_2 + 10i_3 + 4(i_2 - i_3) = 0$$

$$-2i_2 + 4i_1 + 6i_3 = 0 \quad (3)$$

$$\text{Supermesh dependence: } i_1 - i_3 = 3$$

$$\text{so } i_3 = i_1 - 3 \quad (4)$$

$$\text{Substituting (4) into (3) gives: } -2i_2 + 4i_1 + 6(i_1 - 3) = 0$$

$$-2i_2 + 4i_1 + 6i_1 - 18 = 0$$

$$-2i_2 + 10i_1 = 18$$

$$\text{or, rearranging, } -2i_2 = 18 - 10i_1$$

$$i_2 = -9 + 5i_1 \quad (5)$$

Now substitute (5) and (4) into (1)

$$6(-9 + 5i_1) - 4i_1 - 2(i_1 - 3) = 12$$

$$-54 + 30i_1 - 4i_1 - 2i_1 + 6 = 12$$


$$24i_1 = 60$$

$$\text{Therefore, } \boxed{i_1 = 2.5 \text{ A}}$$

$$\text{Also, } i_2 = 3.5 \text{ A}$$

$$i_3 = -0.5 \text{ A}$$

Question 2

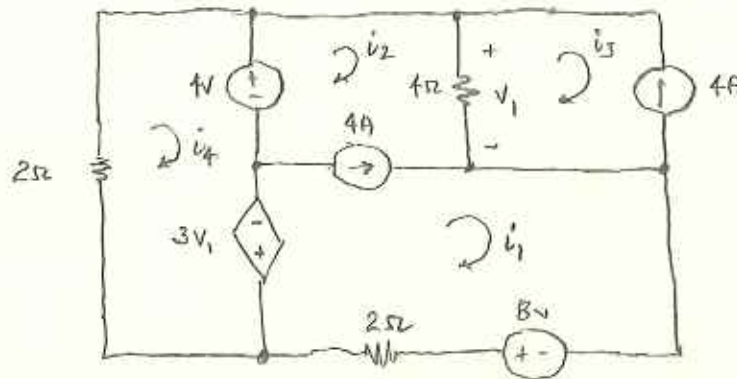

Here we note that $i_3 = -4A$ and i_1 and i_2 form a supermesh.

$$\text{Supermesh } i_1, i_2: \underbrace{-4 + 4(i_2 - i_3)}_{\text{mesh } i_2} - \underbrace{8 + 2i_1 + 3V_1}_{\text{mesh } i_1} = 0 \quad (1)$$

where we have the controlling voltage $V_1 = 4(i_2 - i_3)$. Substitute this into (1):

$$\begin{aligned} -4 + 4i_2 - 4i_3 - 8 + 2i_1 + 12i_2 - 12i_3 &= 0 \\ 2i_1 + 16i_2 - 16i_3 &= 12 \end{aligned}$$


$$\text{With } i_3 = -4, \quad \begin{aligned} -4 + 16i_2 + 64 &= 12 \\ 2i_1 + 16i_2 &= -52 \end{aligned} \quad (2)$$

$$\text{Supermesh dependence: } i_1 - i_2 = 4, \text{ so } i_2 = i_1 - 4$$

$$\begin{aligned} \text{Substitute into (2): } 2i_1 + 16(i_1 - 4) &= -52 \\ 18i_1 - 64 &= -52 \\ 18i_1 &= 12 \end{aligned}$$

$$\text{giving } \boxed{i_1 = 0.6667 A} \quad \text{and} \quad i_2 = -3.333 A$$

Note: Notice that i_4 was never needed in this calculation! The other mesh currents are independent of i_4 thanks to the voltage sources (4V, 3V₁).

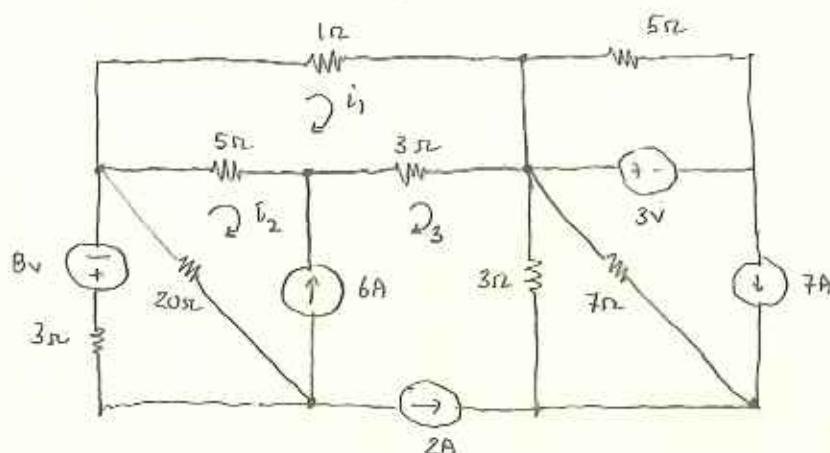Question 3

As the hint mentions, not all meshes are needed to find i_1 . Looking at mesh i_1 , it shares mesh currents i_2 and i_3 , and no other mesh.

Furthermore, by inspection, $i_3 = -2A$.

Mesches i_2 and i_3 form a supermesh where the currents are related by the dependence equation

$$i_3 - i_2 = 6$$

so $i_2 = i_3 - 6$

Since $i_3 = -2A$, $i_2 = -8A$

Then, mesh i_1 :

$$5(i_1 - i_2) + i_1 + 3(i_1 - i_3) = 0$$

$$5i_1 - 5i_2 + i_1 + 3i_1 - 3i_3 = 0$$

$$9i_1 - 5i_2 - 3i_3 = 0$$

giving:

$$9i_1 - 5(-8) - 3(-2) = 0$$


$$9i_1 = -46$$

$$i_1 = -5.111A$$

Question 4

We don't have any dependent sources, so we may use the short-cut method to find the Thevenin resistance.

First, find V_t .

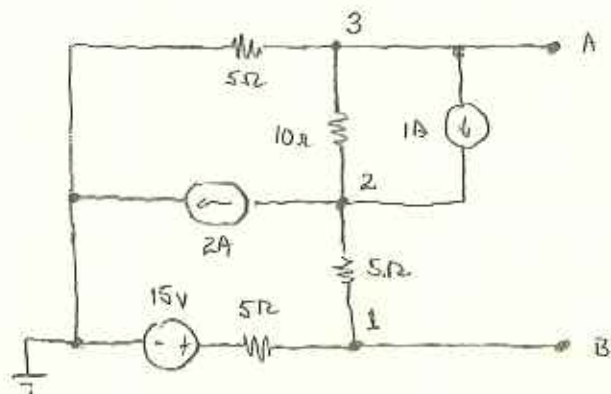

With the reference node chosen as shown, there are three unknown node voltages. When we're done,

$$V_A = V_3 \text{ and } V_B = V_1, \text{ so } V_t = V_A - V_B$$

$$\text{Node 1: } \frac{V_1 - 15}{5} + \frac{V_1 - V_2}{5} = 0$$

$$(\times 5) \quad V_1 - 15 + V_1 - V_2 = 0$$

$$2V_1 - V_2 = 15 \quad (1)$$

$$\text{Node 2: } \frac{V_2 - V_1}{5} + 2 + \frac{V_2 - V_3}{10} - 1 = 0$$

$$(\times 10) \quad 2V_2 - 2V_1 + 20 + V_2 - V_3 - 10 = 0$$

$$3V_2 - 2V_1 - V_3 = -10 \quad (2)$$

$$\text{Node 3: } \frac{V_3}{5} + \frac{V_3 - V_2}{10} + 1 = 0$$

$$(\times 10) \quad 2V_3 + V_3 - V_2 = -10$$

$$3V_3 - V_2 = -10 \quad (3)$$

From (1), $V_2 = 2V_1 - 15$. Substitute into (2)

$$3(2V_1 - 15) - 2V_1 - V_3 = -10$$

$$6V_1 - 45 - 2V_1 - V_3 = -10$$

$$4V_1 - V_3 = 35 \quad (4)$$

$$\text{From (3), } 3V_3 - (2V_1 - 15) = -10$$

$$-2V_1 + 3V_3 = -25 \quad (5)$$

$$\text{From (3) and (5), } -2V_1 + 3(4V_1 - 35) = -25$$

$$10V_1 - 105 = -25$$


$$10V_1 = 80$$

so $V_1 = 8V$, and also $V_3 = -3V$ and $V_2 = 1V$.

Finally $V_t = V_3 - V_1 = \boxed{-11\text{V}}$

Question 5


Zeroing the sources gives

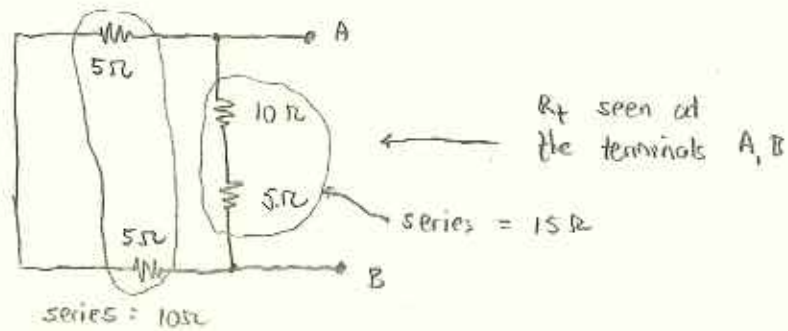

Finally, 10Ω is in parallel with 15Ω

$$R_t = 10 \parallel 15 = \boxed{6\Omega}$$

Question 6

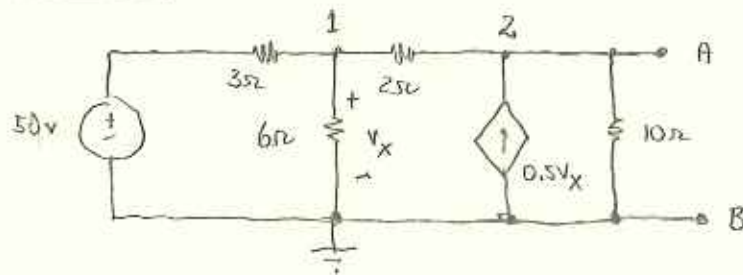

$$\text{Node 1: } \frac{V_1 - 50}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0$$

$$\begin{aligned} (\times 6) \quad 2V_1 - 100 + V_1 + 3V_1 - 3V_2 &= 0 \\ 6V_1 - 3V_2 &= 100 \end{aligned} \quad (1)$$

$$\text{Node 2: } -0.5V_x + \frac{V_2 - V_1}{2} + \frac{V_2}{10} = 0$$

where we observe that $V_x = V_1$.

$$-0.5V_1 + \frac{V_2 - V_1}{2} + \frac{V_2}{10} = 0$$

$$(\times 10) \quad -5V_1 + 5V_2 - 5V_1 + V_2 = 0$$

$$-10V_1 + 6V_2 = 0, \quad \text{so } V_1 = 0.6V_2 \quad (2)$$

Substitute this into (1) giving:

$$6(0.6V_2) - 3V_2 = 100$$

$$3.6V_2 - 3V_2 = 100$$

$$0.6V_2 = 100$$


and $V_2 = 166.67 \text{ V}$

Since $V_E = 0$ and $V_A = V_2$, the Thevenin voltage is

$$V_t = 166.67 \text{ V}$$

Question 7

The circuit has a dependent source, so we must calculate i_{sc}

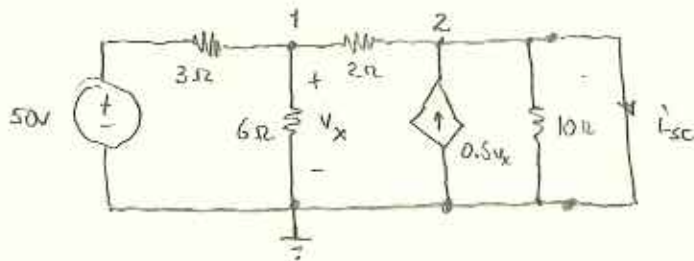

Node 1: $\frac{V_1 - 50}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0$

$$6V_1 - 3V_2 = 100 \quad [\text{same equation}]$$

However, $V_2 = 0$, so $6V_1 - 0 = 100$

$$V_1 = 16.67 \text{ V}$$


Node 2: $\frac{V_2 - V_1}{2} - 0.5V_1 + i_{sc} = 0$

$$0 - \frac{V_1}{2} - 0.5V_1 + i_{sc} = 0$$

$$i_{sc} = V_1$$

so $i_{sc} = 16.67 \text{ A}$

Question 8

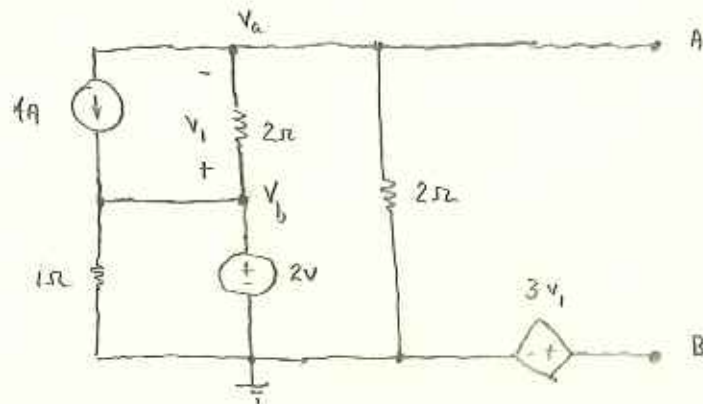

We see that $V_b = 2\text{V}$, and that $V_A = V_a$, and $V_B = 3V_1$.
When we're ready, $V_k = V_A - V_B$.

$$\text{At } V_a: 4 + \frac{V_a - 2}{2} + \frac{V_a}{2} = 0$$

$$(\times 2) \quad 8 + V_a - 2 + V_a = 0$$

$$2V_a = -6$$


$$\text{Therefore, } V_A = V_a = -3\text{V}$$

The dependent voltage source uses $V_1 = V_b - V_a = 2 - (-3)$
 $V_1 = 5\text{V}$

$$\text{so } V_B = 3V_1 = 3(5) = 15\text{V}$$

$$\text{Finally, } V_k = V_A - V_B = -3 - 15 = \boxed{-18\text{V}}$$

Question 9

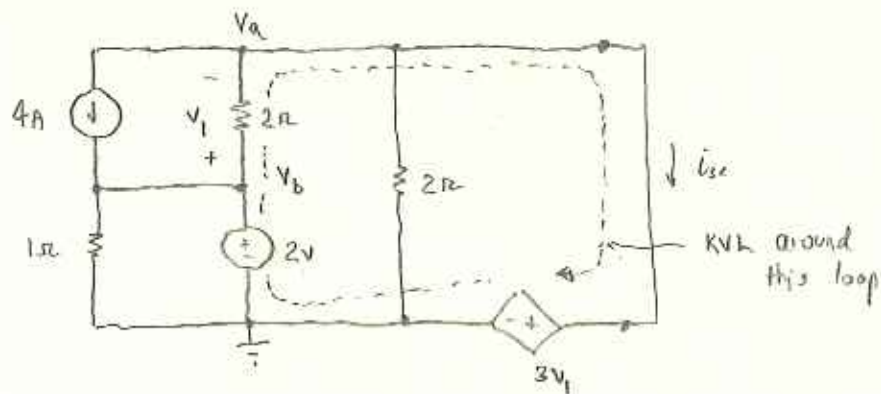

Following the hint given, KVL around the loop shown gives

$$-2 + V_1 + 3V_1 = 0$$

$$4V_1 = 2$$

$$\text{so } V_1 = \frac{1}{2} \text{ V}$$

With the short circuit applied,

$$V_a = 3V_1 = 1.5 \text{ V}$$

$$\text{At node a: } \frac{V_a - 2}{2} + 4 + \frac{V_a}{2} + i_{sc} = 0$$

$$(\times 2) \quad V_a - 2 + 8 + V_a + 2i_{sc} = 0$$

$$2V_a + 6 + 2i_{sc} = 0$$

$$\text{With } V_a = 1.5, \quad 2(1.5) + 6 + 2i_{sc} = 0$$

$$2i_{sc} = -9$$

$$i_{sc} = \boxed{-4.5 \text{ A}}$$

Alternatively, one may use the mesh-current method using two mesh equations. One of the mesh currents is i_{sc} !