
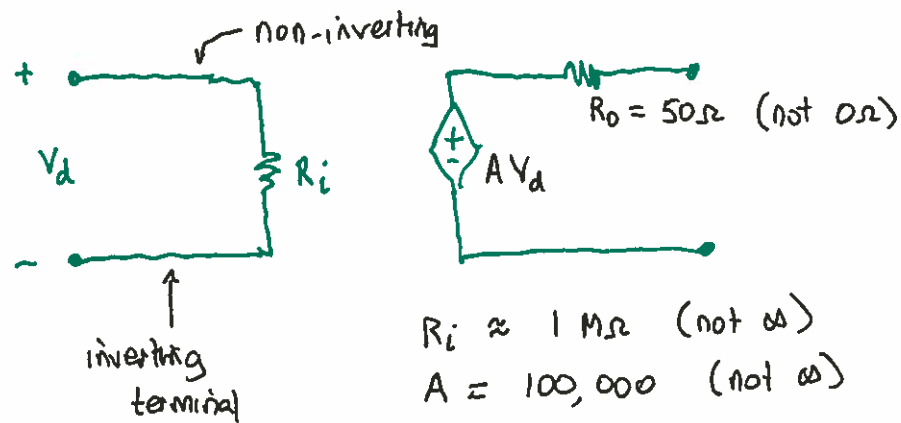


Monday,
February 29,
2016

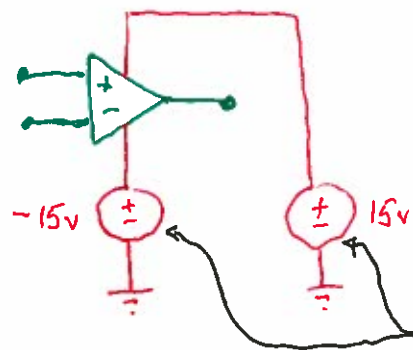

Since the op-amp is an electronic circuit, it requires an external power source to operate.



When we draw op-amp circuits, we seldom draw the external power sources - we always assume they're there!

Key properties — the summing-point constraints

1. The virtual short circuit

For any practical circuit, V_o must be finite-valued $|V_o| < \infty$.

For an ideal op-amp, $A = \infty$, and

$$V_o = A V_d$$

$$\text{So, } \frac{V_o}{A} = V_d = \frac{V_o}{\infty} = 0$$


$$V_d = 0$$

NO VOLTAGE
ACROSS INPUT
TERMINALS.

2. The virtual open circuit

For an ideal op-amp, $R_i = \infty$, so

Circuit symbol:

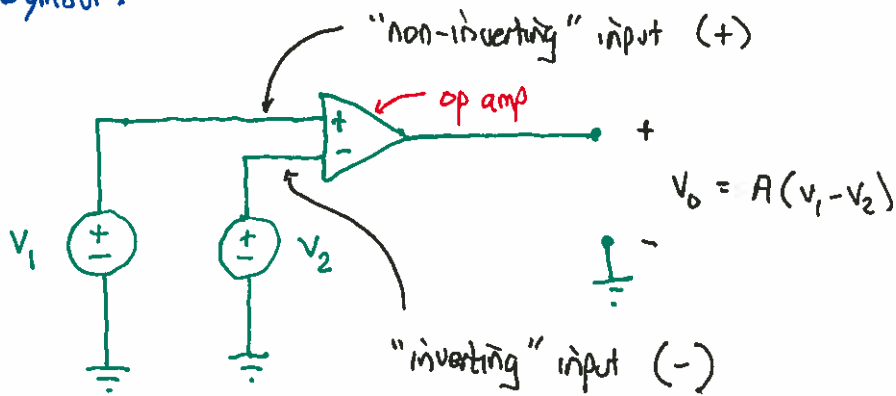


The op-amp amplifies the differential input voltage V_d , where

$$V_d = V_1 - V_2 \rightarrow V_o = A V_d$$

big number!

The model of ideal op-amp:

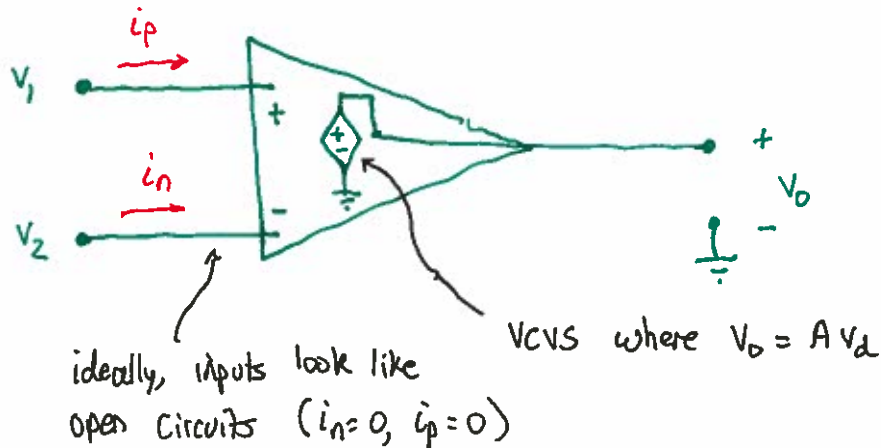

The main characteristics of an ideal op-amp:

- infinite input resistance, so $i_n = i_p = 0$
- $A = \infty$ ("A" is called the "open-loop gain")
- zero output resistance (the effective resistance of a voltage source is 0 Ω).

A real-world op-amp

$i_n = i_p = 0$ NO CURRENT FLOWS INTO INPUT TERMINALS.

In summary,

$V_d = 0$
 $i_n = i_p = 0$ SUMMING-POINT CONSTRAINTS.

Circuit analysis is then by all of your favorite methods while observing these constraints.

Op-amps not very useful by themselves; instead we use them in circuits designed to use these constraints.

- always designed to operate with "negative feedback" (useless otherwise)
- In ENGG 225, we'll always assume this is so.

→ It is these ~~an~~ summing-point constraints that give op-amp circuits a wide diversity of important applications.

Applying the summing-point constraints

Example 1: Find V_o in the following circuit

