

rms voltage : $V_{rms} = \frac{V_m}{\sqrt{2}} = 7.071 \text{ V}$

Wednesday,
March 16, 2016

and average power


$$P_{avg} = \frac{V_{rms}^2}{R} = \frac{(7.071)^2}{10} = 5 \text{ W}$$

Let's also sketch the instantaneous power $p(t)$

$$p(t) = \frac{v^2(t)}{R} = \frac{100}{10} \cos^2(1000\pi t - 60^\circ)$$

Use the trig identity $\cos^2(x) = \frac{1}{2} [1 + \cos(2x)]$

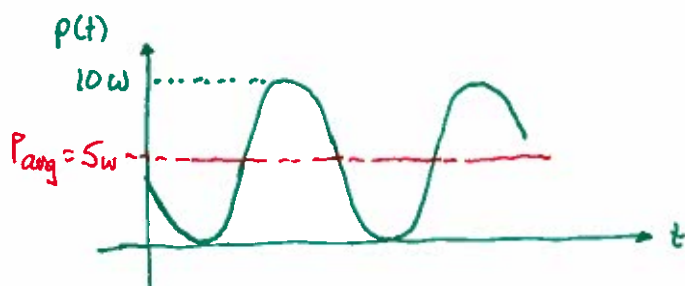
$$p(t) = 5 + 5 \cos(2000\pi t - 120^\circ)$$



Phasors

When dealing with sinusoidal voltages and currents, we need a convenient way to add them to satisfy KVL, KCL.

Consider :

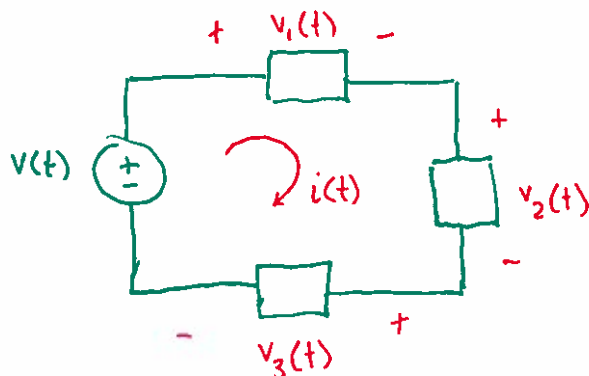

Let $v_1(t) = 10 \cos(\omega t)$

$$v_2(t) = 5 \cos(\omega t - 30^\circ)$$

$$v_3(t) = 5 \cos(\omega t + 90^\circ)$$

Find $v(t) = V_m \cos(\omega t + \theta)$

KVL must be satisfied by this circuit over all time

$$-v(t) + v_1(t) + v_2(t) + v_3(t) = 0$$

$$\text{So } v(t) = 10 \cos(\omega t) + 5 \cos(\omega t - 30^\circ) + 5 \cos(\omega t + 90^\circ)$$

How do we manipulate this to get the desired form

$$v(t) = V_m \cos(\omega t + \theta)? \quad \text{What are } V_m \text{ and } \theta? \quad \text{Help!}$$

For this, we instead express voltages and currents in terms of phasors.

$$\text{Let } v_1(t) = V_1 \cos(\omega t + \theta_1)$$

usually fixed in value throughout the circuit for an analysis problem.

We have a pair of independent parameters describing the voltage:

V_1 - magnitude (amplitude)

θ_1 - phase angle

BASIC IDEA: Represent as a vector on a plane: then add the vector lengths.

Examples of phasor representation:

Voltage

$$v_a(t) = V_a \cos(\omega t + \theta_a)$$

$$\begin{aligned} v_b(t) &= V_b \sin(\omega t + \theta_b) \\ &= V_b \cos(\omega t + \theta_b - 90^\circ) \end{aligned}$$

Phasor representation

$$\bar{V}_a = V_a \angle \theta_a$$

$$\bar{V}_b = V_b \angle \theta_b - 90^\circ$$

magnitude

phase angle.

Similarly, for currents

$$i_c(t) = I_c \cos(\omega t + \theta_c) \longleftrightarrow \bar{I}_c = I_c \angle \theta_c$$

To manipulate phasors, we need to use complex numbers.


Complex numbers - review

We express and manipulate phasors as complex numbers.
Complex numbers involve "imaginary" numbers.

Mathematicians: $i = \sqrt{-1}$

Engineers: j is current, so $j = \sqrt{-1}$
or $j^2 = -1$

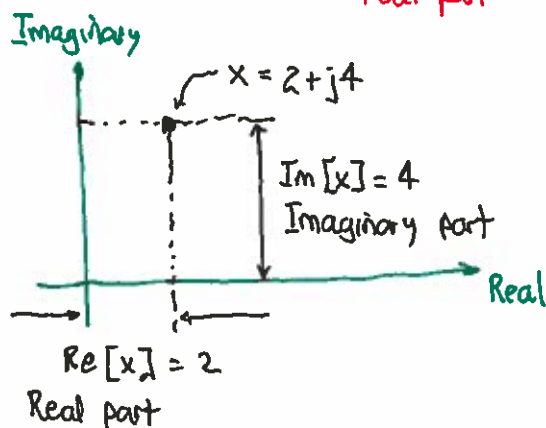E.g., complex number $x = 2 + j4$
real part imaginary part



x is a point on the complex plane.

The complex conjugate of x :

denotes complex conjugate
 $x^* = 2 - j4$
flip sign of $\text{Im}[x]$

Rectangular and polar forms of complex numbers

$$x = a + jb \quad (\text{rectangular})$$

$$x = M \angle \theta \quad (\text{polar})$$

