

Question 1

From the current waveform, we first must determine the voltage waveform. We have

$$v_c(t) = \frac{1}{C} \int_{t_1}^{t_2} i_c(t) dt + v_c(t_1)$$


- Interval $0 < t \leq 1 \text{ ms}$

$$i_c(t) = 0, \quad \text{so } v_c(t) = 10 \text{ V (unchanged from initial value)}$$

- Interval $1 < t \leq 3 \text{ ms}$

$$\begin{aligned} v_c(t) &= \frac{1}{10^{-6}} \int_{1 \text{ ms}}^t (-10 \times 10^{-3}) dt + v_c(1 \text{ ms}) \\ &= -10^6 \times 10 \times 10^{-3} t \Big|_{1 \text{ ms}}^t + 10 \\ &= -10^4 [t - 0.001] + 10 \\ &= -10^4 t + 10 + 10 \\ &= -10^4 t + 20 \end{aligned}$$

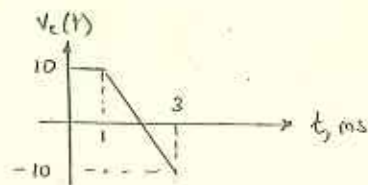
$$\text{At time } t = 0.003, \quad v_c(t) = -30 + 20 = -10$$




- Interval $3 < t \leq 5 \text{ ms}$

$$\begin{aligned} v_c(t) &= \frac{1}{C} \int_{3 \text{ ms}}^t i_c(t) dt + v_c(3 \text{ ms}) \\ &= +10^4 [t - 0.003] - 10 \\ &= 10^4 t - 30 - 10 \\ &= 10^4 t - 40 \end{aligned}$$
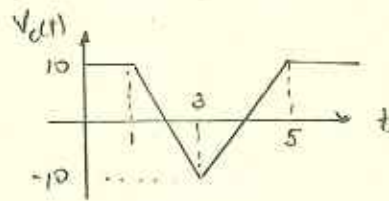
$$\begin{aligned} \text{At } t = 0.005, \quad v_c(t) &= 50 - 40 \\ &= 10 \text{ V} \end{aligned}$$



Multiplying this curve with $i_c(t)$ gives the power curve

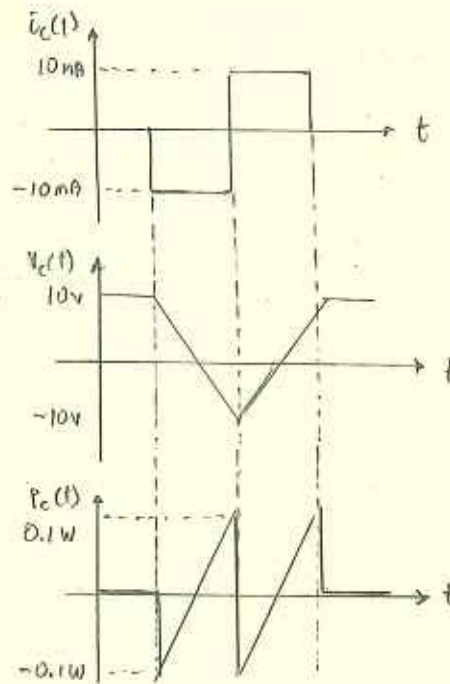

Question 2

There is no initial current in the inductor, since the switch is open

$$\begin{aligned}
 i_L(t) &= \frac{1}{L} \int_0^t v_L(t) dt + 0 \\
 &= \frac{1}{4} \int_0^t (8t+6) dt \\
 &= \frac{1}{4} [4t^2 + 6t] \Big|_0^t = t^2 + 1.5t
 \end{aligned}$$

$$\text{At } t = 2s, \quad i_L(2) = 4 + 3 = 7 \text{ A}$$

$$\begin{aligned}
 \text{And power} &= v_L(2) i_L(2) = (8 \times 2 + 6) \times 7 \\
 &= 22 \text{ V} \times 7 \text{ A}
 \end{aligned}$$

$$P_L(2) = 154 \text{ W}$$

Question 3

In question 2, we determined $i_L(2) = 7 \text{ A}$. The energy is therefore

$$\begin{aligned} w_L(2) &= \frac{1}{2} L i_L^2(2) \\ &= \frac{1}{4} \times 4 \times 7^2 \end{aligned}$$

$$\boxed{w_L(2) = 98 \text{ J}}$$

Question 4

We have $v_c(t) = 10 \sin(10^4 t) + 5 \cos(10^4 t)$, and

$$\begin{aligned} i_c(t) &= C \frac{dv_c(t)}{dt} \\ &= 20 \times 10^{-6} \left[10^5 \cos(10^4 t) - 5 \times 10^4 \sin(10^4 t) \right] \Big|_{t=0.5 \text{ ms}} \\ &= 20 \times 10^{-1} [\cos(5) - 0.5 \sin(5)] \\ &= 2 \cos(5) - \sin(5) \\ &= 1.5262 \text{ A} \end{aligned}$$

And the voltage at $t = 0.5 \text{ ms}$ $v_c(t) = 10 \sin(5) + 5 \cos(5)$
 $= -8.1709$

The power, therefore, is $p_c(t) = v_c(t) i_c(t)$
 $= -8.1709 \times 1.5262$

$$\boxed{p_c(t) = -12.471 \text{ W}}$$

Question 5

For the time between $t = 0$ and 0.5 s , we have

$$v_c(t) = 40t$$

$$\begin{aligned} \text{and } i_c(t) &= C \frac{dv_c(t)}{dt} = 40 \times 10^{-6} \times 40 \\ &= 1.6 \times 10^{-3} \text{ A} \end{aligned}$$

And $v_c(t) = 40 \times (0.4) = 16 \text{ V}$

Power: $p_c(t) = v_c(t) i_c(t) = 16 \times 1.6 \times 10^{-3} = \boxed{25.6 \text{ mW}}$

Question 6

To calculate $w_L(t)$, we must first obtain the current waveform $i_L(t)$

$$i_L(t) = \frac{1}{L} \int_{t_1}^{t_2} v_L(t) dt + i_L(t_1)$$

- Interval $0 \leq t \leq 3$ s

$$\begin{aligned} i_L(t) &= \frac{1}{2} \int_0^t 10 dt + i_L(0) \\ &= \frac{1}{2} [10t]_0^t + 2 \\ &= 5t + 2 \end{aligned}$$


When $t = 3$, $i_L(3) = 15 + 2 = 17$ A

- Interval $3 < t \leq 6$ s

$$\begin{aligned} i_L(t) &= \frac{1}{2} [-10t]_3^t + 17 \\ &= -5(t-3) + 17 \\ &= -5t + 32 \end{aligned}$$

When $t = 6$, $i_L(6) = -5 \times 6 + 32 = 2$ A

The energy waveform is determined from $w_L(t) = \frac{1}{2} L i_L^2(t)$

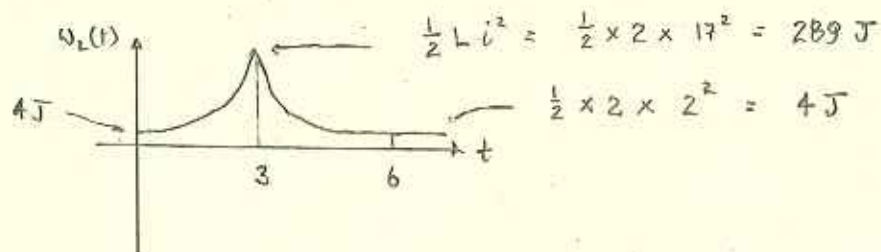Question 7

The voltage on the inductor is $v_L(t) = L \frac{di_L(t)}{dt}$

- Interval $0 \leq t \leq 1$, slope of $i_L(t) = 0$, so

$$v_L(t) = 0$$

• Interval $1 < t \leq 3$


$$\text{slope} = -\frac{4}{2} = -2$$

$$\text{so } v_L(t) = 1 \times -2 = -2\text{V}$$

• Interval $t > 3$, slope = 0, so

$$v_L(t) = 0$$

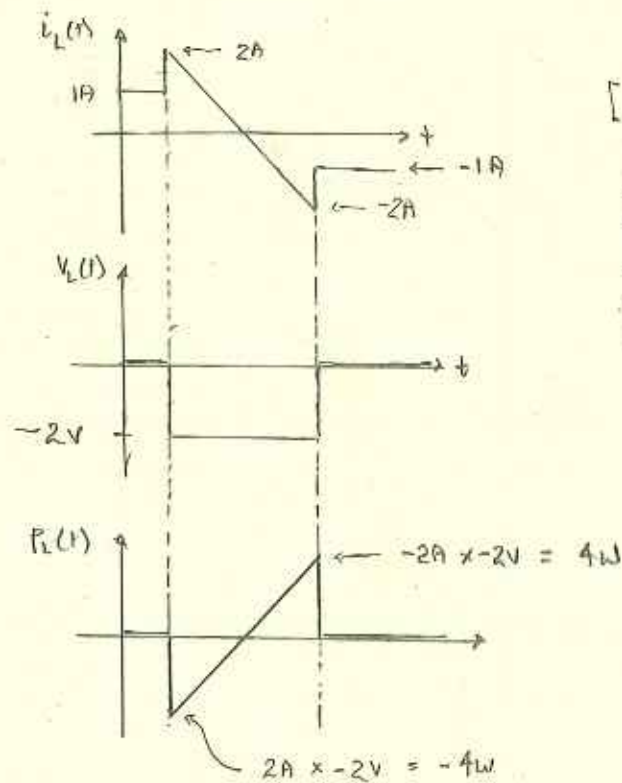The power waveform $p_L(t) = v_L(t) i_L(t)$



[Note that current changes instantaneously in this question, which should cause an infinite voltage; acceptable answers here are the one shown, and "none of the above"]