

## Apparent power (continued)

Friday, April 1, 2016.

$$P_{app} = V_{rms} I_{rms}$$

Units of apparent power



VOLT-AMPS: VAs

Sample specifications:

<u>units</u>	<u>meaning</u>
5 kW load	$P = 5000 \text{ W}$
10 KVA load	$V_{rms} I_{rms} = 10,000 \text{ VAs}$
15 KVAR load	$Q = 15,000 \text{ VARs}$
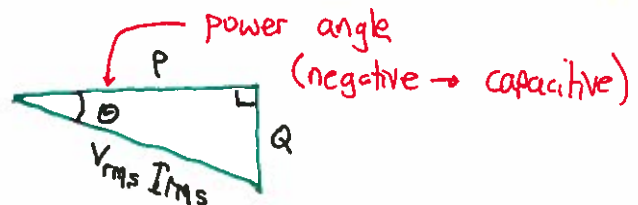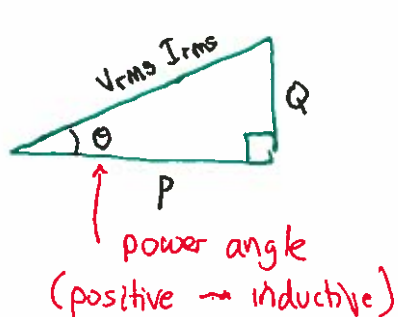
## The power triangle

Each of  $P$ ,  $Q$ , and apparent power can be represented in a triangle.



## Additional power relationships

It is easy to calculate  $P$ ,  $Q$ , and apparent power directly for an impedance.

$$\text{We have } Z = |Z| \angle \theta = R + jX$$

$$\text{and } \cos(\theta) = \frac{R}{|Z|}, \quad \sin(\theta) = \frac{X}{|Z|}$$

We also have

$$P = \frac{V_m I_m}{2} \cos(\theta) = \frac{V_m I_m}{2} \times \frac{R}{|Z|}$$

$$\text{and } I_m = \frac{V_m}{|Z|}$$

$$\text{so } P = \frac{I_m^2 R}{2}$$

$$\text{and } \boxed{P = I_{rms}^2 R} \quad \text{AVERAGE POWER IN } Z.$$

Similarly,

$$\boxed{Q = I_{rms}^2 X} \quad \text{REACTIVE POWER IN } Z.$$

$$\text{and } \boxed{P_{app} = \sqrt{P^2 + Q^2}} \quad \text{APPARENT POWER IN } Z.$$

Finally, complex power is defined as

$$\bar{S} = \frac{1}{2} \bar{V} \bar{I}^*$$

We have

$$\begin{aligned} \bar{S} &= \frac{1}{2} (V_m \angle \theta_v) \times (I_m \angle -\theta_i) \\ &= \frac{V_m I_m}{2} \angle \theta_v - \theta_i \end{aligned}$$

where  $\theta = \theta_v - \theta_i$  (power angle)

Expanding  $\bar{S}$  in rectangular form

$$\bar{S} = \frac{V_m I_m}{2} \cos(\theta) + j \frac{V_m I_m}{2} \sin(\theta)$$

which we may write


$$\bar{S} = P + jQ$$

The apparent power  $P_{app}$

$$P_{app} = |\bar{S}| = \sqrt{P^2 + Q^2}$$

Example : using power triangles


Find  $\bar{I}$  in the circuit below

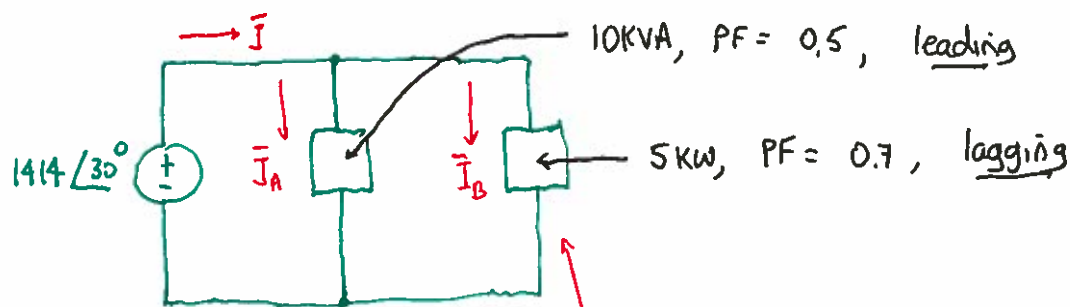

Note this load is specified in terms of apparent power ( $P_{app}$ , in KVA)

this load specified in terms of average power  $P$  ( $P$ , in Watts)

For branch A, we have

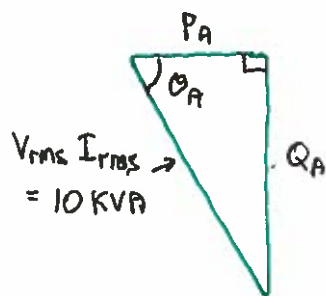

Power factor  $\cos(\theta_A) = 0.5$   
leading

Remember a leading PF means current leads the voltage.

$\theta_I > \theta_V$ , so  $\theta_A = \theta_V - \theta_I$   
(negative angle)

Tip:

PF	$\theta_V, \theta_I$	power angle $\theta$
leading	$\theta_I > \theta_V$	$\theta = \theta_V - \theta_I$ NEGATIVE
lagging	$\theta_I < \theta_V$	$\theta = \theta_V - \theta_I$ POSITIVE

The power angle is therefore  $\theta_A = -[\cos^{-1}(0.5)]$   
 $= -60^\circ$


For branch A,

$$\begin{aligned}
 P_A &= V_{rms} I_{rms} \cos(\theta_A) \\
 &= 10,000 \times 0.5 \\
 &= 5,000 \text{ W.}
 \end{aligned}$$

$$\begin{aligned}
 Q_A &= V_{rms} I_{rms} \sin(\theta_A) \\
 &= -10,000 \times 0.866 \\
 &= -8.660 \text{ KVAR}
 \end{aligned}$$

For branch B,
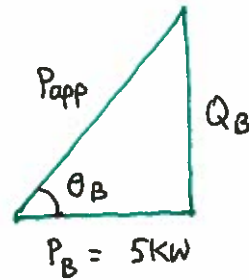
$$\text{We know } \theta_B = \cos^{-1}(0.7) \\ = 45.57^\circ$$



We have  $P_B$ , and need  $Q_B$ , where

$$\tan(\theta_B) = \frac{Q_B}{P_B}, \text{ so } Q_B = P_B \tan(\theta_B)$$

$$Q_B = 5000 \times \tan(45.57^\circ) \\ = 5.101 \text{ KVAR}$$

The total amount of power in both loads

$$P = P_A + P_B = 5\text{KW} + 5\text{KW} = 10\text{KW}$$

$$Q = Q_A + Q_B = -8.660 \text{ KVAR} + 5.101 \text{ KVAR} = -3.559 \text{ KVAR}$$

$$\bar{S} = P + jQ = 10,000 - j 3559 \text{ VA.}$$