

3. Purely capacitive load ($R=0, X<0$)

We have $Z = 1/j\omega C = \frac{1}{\omega C} \angle -90^\circ$, so $\theta = -90^\circ$

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t + 90^\circ) = -I_m \sin(\omega t)$$

Therefore,

$$p(t) = -V_m I_m \cos(\omega t) \sin(\omega t)$$

$$= -\frac{V_m I_m}{2} \sin(2\omega t)$$

This is also reactive power. For the capacitor and inductor, no average power is consumed or generated.

4. For a general load ($R \neq 0, X \neq 0$)

Here, we allow for both resistance and capacitance or inductance. We allow θ in the range.

$$-90^\circ \leq \theta \leq 90^\circ$$

purely capacitive \nearrow \nwarrow purely inductive.

We have

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$\text{and } p(t) = V_m \cos(\omega t) I_m \cos(\omega t - \theta)$$

This can be manipulated to get

$$p(t) = \frac{V_m I_m}{2} \cos(\theta) \underbrace{[1 + \cos(2\omega t)]}_{\text{average} = 0} + \frac{V_m I_m}{2} \sin(\theta) \underbrace{\sin(2\omega t)}_{\text{average} = 0}$$

The average power is

$$P = P_{\text{avg}} = \frac{V_m I_m}{2} \cos(\theta)$$

POWER, IN WATTS,
ABSORBED BY THE
RESISTIVE COMPONENT OF
TOTAL IMPEDANCE

Recall that $V_{rms} = \frac{V_m}{\sqrt{2}}$, $I_{rms} = \frac{I_m}{\sqrt{2}}$

so

$$P = V_{rms} I_{rms} \cos(\theta)$$

AVERAGE, OR
REAL, POWER

For a resistor, $\theta = 0^\circ$, so $P = V_{rms} I_{rms}$. The $\cos(\theta)$ term is very important, and is called

$$PF = \cos(\theta)$$

POWER
FACTOR

where, in the more general case,

$$\theta = \theta_V - \theta_I$$

POWER
ANGLE

We often state the PF and specify whether current leads or lags voltage.

Example: A load has a leading power factor of 0.707.

Is this capacitive or inductive, and what's the power angle?

→ A leading PF means current is leading (has a higher phase than) the voltage.

Reviewing what we know:

$$\text{We have } Z = R + jX = |Z| \angle \theta$$

$$\text{Let } \bar{V} = V_m \angle \theta_V$$

$$\text{and } \bar{I} = I_m \angle \theta_I$$

where we are given that $\theta_I > \theta_V$ (current leads voltage)

$$\text{We know } \bar{I} = \frac{\bar{V}}{Z}, \text{ so } Z = \frac{\bar{V}}{\bar{I}} = \frac{V_m \angle \theta_V}{I_m \angle \theta_I}$$

$$\text{so } Z = |Z| \angle \theta_V - \theta_I$$

↖ power angle negative,
because $\theta_I > \theta_V$

And what we have ...

We are given that $PF = \cos(\theta) = \cos(\theta_v - \theta_i) = 0.707$

and $\theta < 0$, so $\theta = -45^\circ$

This suggests that $Z = R + jX$, where $X < 0$.

The load has a capacitance ($Z_c = -j/\omega C$)

Reactive power

Average reactive power is always zero. However, its instantaneous value is sinusoidal with peak value Q .

$$Q = V_{rms} I_{rms} \sin(\theta)$$

REACTIVE POWER.

This is flowing back and forth between inductors/capacitors and the source.

- might be a problem in large-scale systems
- power companies might penalize you for reactive power.

Units of reactive power

VOLT-AMPERES-REACTIVE: VARs

Apparent power

This is a measure of the total power (average and reactive)

$$\text{apparent power} = V_{rms} I_{rms}$$