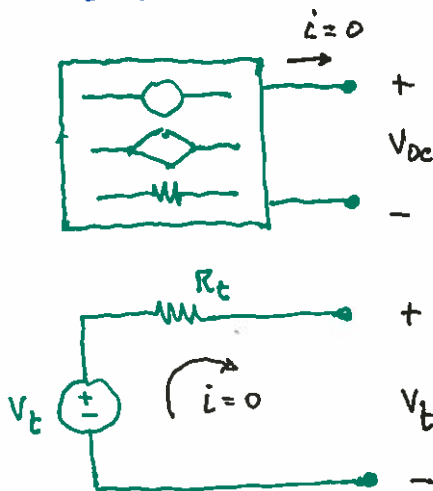


The voltage-current characteristics are identical at the two terminals.
 V_t and R_t are found by considering two operating extremes.


Thursday,
 February 11
 2016

Open-circuit



giving $V_t = V_{oc}$

Short-circuit

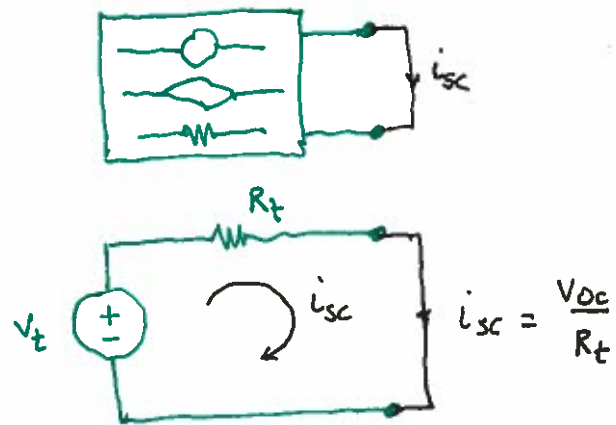


giving $i_{sc} = \frac{V_t}{R_t} = \frac{V_{oc}}{R_t}$

and $R_t = V_{oc} / i_{sc}$

Determining a Thevenin equivalent is two separate analysis problems:
 Find V_t , find R_t .

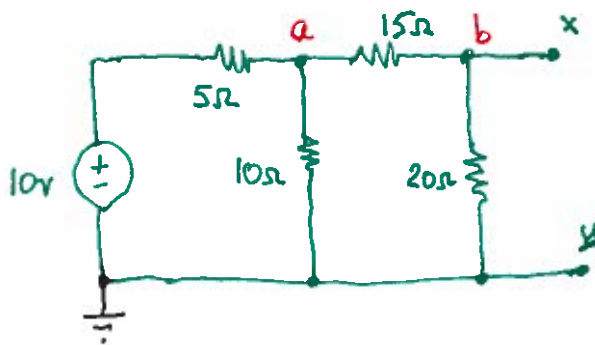Example: Find the Thevenin equivalent at terminals x, y.



Find V_t , where $V_t = V_{oc}$. Using node-voltage method, open-circuit voltage will be V_b .

$$\text{Node } a: \frac{V_a - 10}{5} + \frac{V_a}{10} + \frac{V_a - V_b}{15} = 0$$

$$(\times 30) \quad 6V_a - 60 + 3V_a + 2V_a - 2V_b = 0$$

$$\text{or } 11V_a - 2V_b = 60$$

(1)

$$\text{Node } b: \frac{V_b - V_a}{15} + \frac{V_b}{20} = 0$$

$$(\times 60) \quad 4V_b - 4V_a + 3V_b = 0$$

$$\text{or } -4V_a + 7V_b = 0$$

(2)


$$\text{Solving (1) and (2),} \quad V_a = 6.087\text{V}$$

$$V_b = 3.478\text{V}$$

Thus,

$$V_t = V_b = V_{oc} = 3.478\text{V}$$

Now find i_{sc}

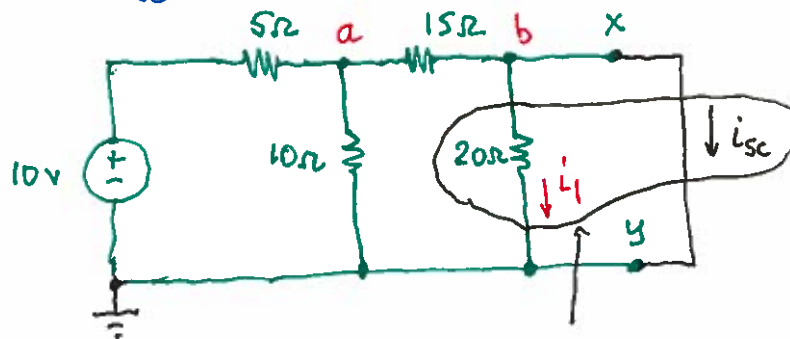


Notes: • parallel combination of 20Ω and a short circuit! (Equivalent resistance short circuit = 0Ω)

• What's happened to V_b ? Now connected directly to reference node. $V_b = 0$.

• $i_1 = 0$, since $V_b/20 = 0$. All current is in i_{sc} , none in 20Ω resistor.

Redraw

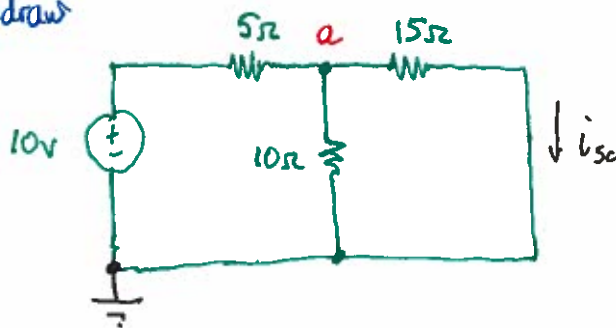

Node a: $\frac{V_a - 10}{5} + \frac{V_a}{10} + \frac{V_a}{15} = 0$ note this is i_{sc}


(x30) $6V_a - 60 + 3V_a + 2V_a = 0$

so $V_a = 60/11 = 5.455 \text{ v.}$


Therefore, $i_{sc} = \frac{V_a}{15} = 0.364 \text{ A}$

and $R_t = \frac{V_{oc}}{i_{sc}} = \frac{3.478}{0.364} = 9.56 \Omega$

The Thevenin equivalent circuit

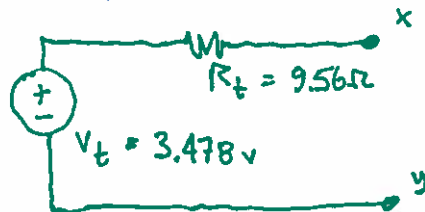

Example 2: Find the Thevenin equivalent

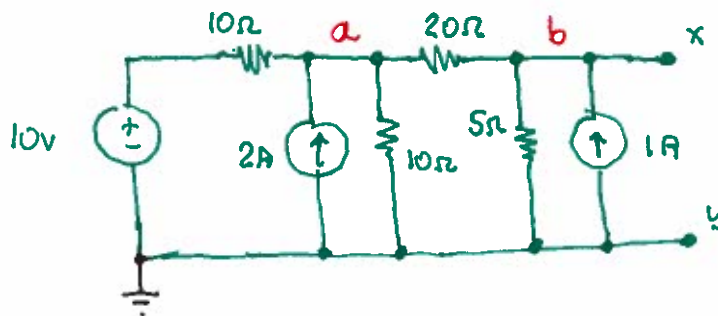

Find V_t . Using node-voltage method, $V_t = V_b$

Node a: $\frac{V_a - 10}{10} - 2 + \frac{V_a}{10} + \frac{V_a - V_b}{20} = 0$

(x20) $2V_a - 20 - 40 + 2V_a + V_a - V_b = 0$

$5V_a - V_b = 60$

(1)