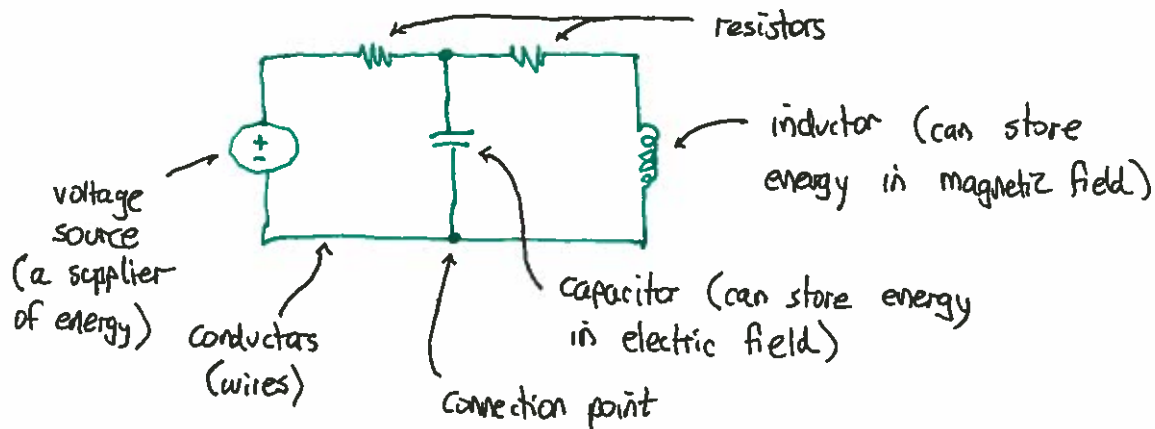


Circuits, currents, voltages

Electric circuit - an interconnection of circuit elements connected in closed paths by conductors



The concept of electrical charge is the basis for describing all electrical phenomena.

- charge exists in discrete quantities at integer multiples of

$$1.6022 \times 10^{-19} \text{ Coulombs} \quad \text{charge on one electron.}$$

Two fundamentally important electrical quantities: current and voltage.

Electrical current

Current - rate of flow of electrical charge

$$i(t) = \frac{dq(t)}{dt}$$

$i(t)$ = current in Amperes (A)

$q(t)$ = charge in Coulombs (C)

t = time in seconds (s)


$$1 \text{ A} = 1 \text{ C/s}$$

Given $i(t)$, one can also find total charge $q(t)$

$$q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$


↑ some initial constant value

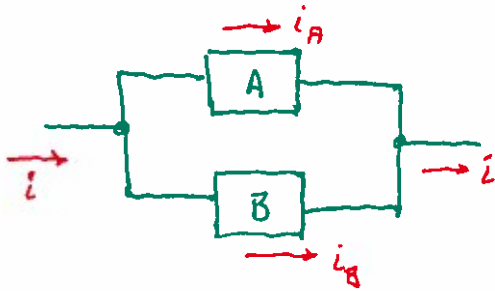We normally assign reference directions for current.




- can choose reference directions arbitrarily — if current flow is actually in the opposite direction, the value of i is opposite in sign.

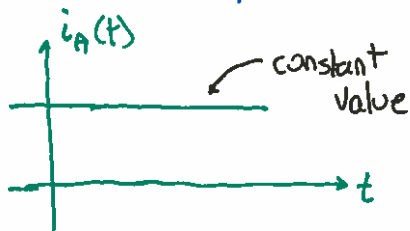We can have direct current (DC) and alternating current (AC)




DC
(e.g., battery power)

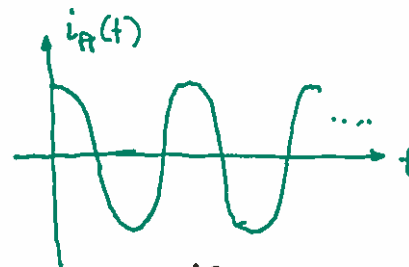

AC
(e.g., house current)

Some common notation:

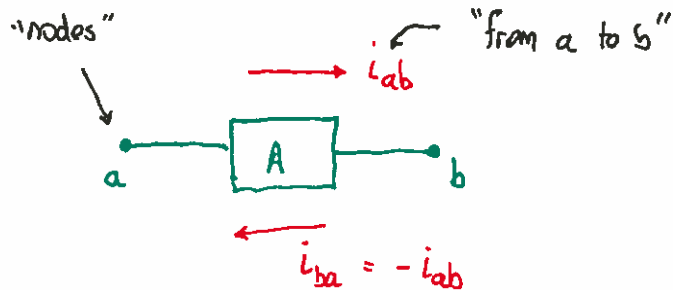

Voltages

Voltage — energy transferred to a circuit element per unit of charge flow through it.

$$v(t) = \frac{dw(t)}{dq(t)}$$


$v(t)$ = voltage in Volts (V)

$w(t)$ = energy in Joules (J)

$q(t)$ = charge in C.

$$1 \text{ V} = 1 \text{ J/C}$$

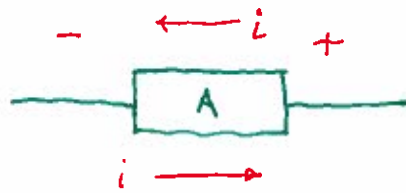
Voltages are assigned polarities to indicate direction of energy flow.



(energy absorbed by A)


(energy supplied by A)

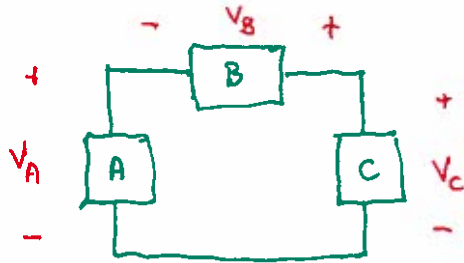For analysis purposes, we assign reference polarities



- can choose reference polarities arbitrarily — if polarity is opposite, the value of V is opposite in sign.

Some common notation:

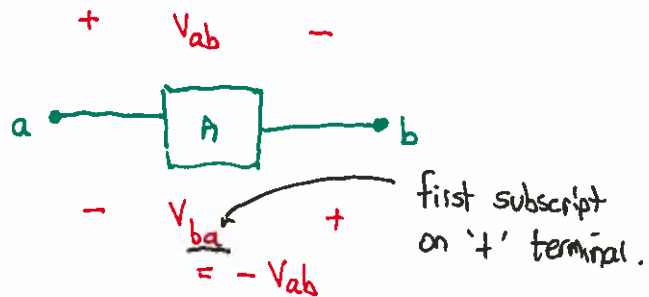

Ideal Basic Circuit Elements

Here, we will talk about conductors, sources, resistors. Later, will bring in inductors and capacitors.