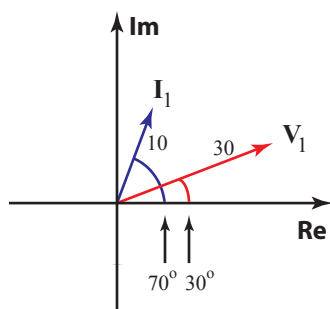



University of Calgary
Department of Electrical and Computer Engineering
ENGG 225 - Fundamentals of Electrical Circuits and Machines
Winter, 2017

Problem Assignment #7


1. [1 mark.] The current $i(t) = 2 \sin(120\pi t)$ flows through a 4Ω resistor. What is the average power delivered to the resistor? Express your answer in *Watts (W)*.
2. [2 marks.] A current of $i_C(t) = 2 \cos(120\pi t)$ is applied to a $400 \mu\text{F}$ capacitor. Give the *peak amplitude* of $v_C(t)$ in *Volts (V)*.
3. [2 marks.] Consider two sinusoidal current waveforms $i_1(t)$ and $i_2(t)$. $i_1(t)$ has angle phase of $\theta_1 = -45^\circ$, and reaches its positive peak 0.1875 ms *later* than the corresponding peak in $i_2(t)$. Both currents have a frequency of 1000 Hz. Give the phase angle θ_2 for $i_2(t)$ in degrees such that $-180^\circ \leq \theta_2 < 180^\circ$.
4. [2 marks.] The voltage across an element is $v_1(t) = 30 \cos(\omega t + 30^\circ)$. The current through that element, $i_1(t)$, has an rms value of 10 A, and it *leads* $v_1(t)$ by 40° . Choose the phasor diagram from the choices below that correctly depicts \mathbf{V}_1 and \mathbf{I}_1 .




(a)

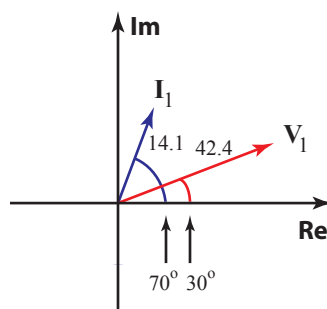

(b)

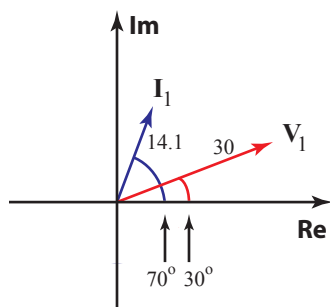


(c)

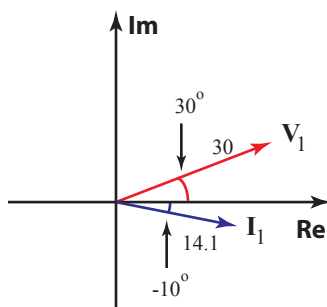

(d)

(e) None of the above.

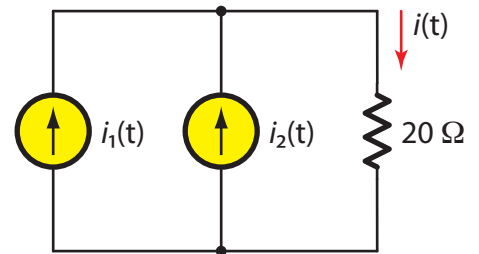5. **[2 marks.]** Let $i_1(t) = 10 \cos(120\pi t + 45^\circ)$ in the circuit at right. Suppose that the current through the resistor, as indicated, is measured to be $i(t) = 8 \cos(120\pi t + 30^\circ)$. Determine the phase angle θ_2 of $i_2(t)$ in degrees such that $-180^\circ \leq \theta_2 < 180^\circ$.



6. **[1 mark.]** For Question #5 above, give the *rms* amplitude of $i_2(t)$. Give your answer in *Amperes (A)*.
7. **[2 marks.]** A circuit element has a phasor voltage of $\mathbf{V} = 400 \angle 120^\circ$ and a current of $\mathbf{I} = 5 \angle 30^\circ$. The angular frequency is 100 rad/s. Decide on whether the circuit element is a capacitor or an inductor. If it is a capacitor, give its capacitance in *microFarads* (μF); if it is an inductor, give its inductance in *Henrys* (H).