
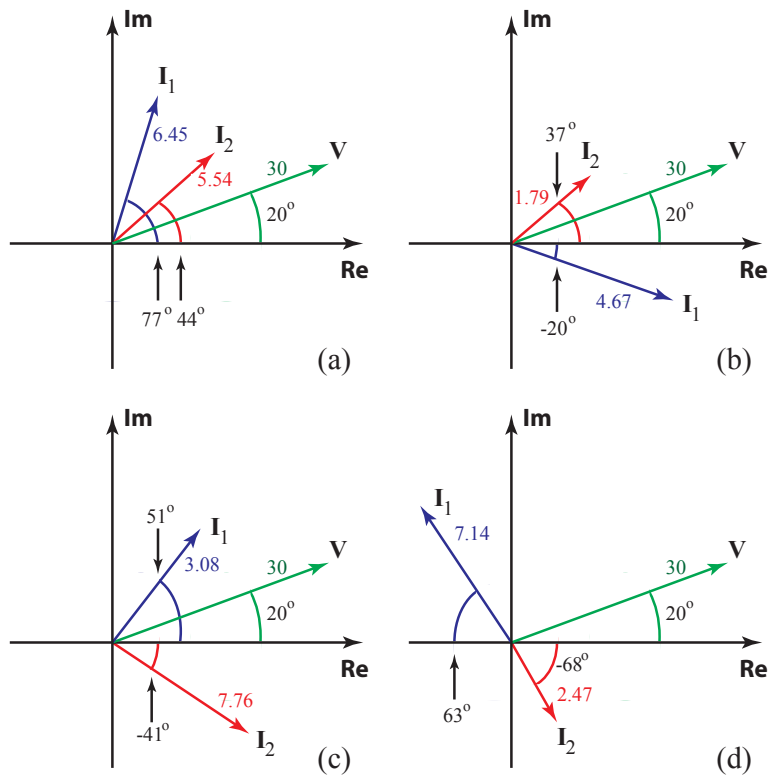


University of Calgary
Department of Electrical and Computer Engineering
ENGG 225 - Fundamentals of Electrical Circuits and Machines
Winter, 2018


Problem Assignment #8

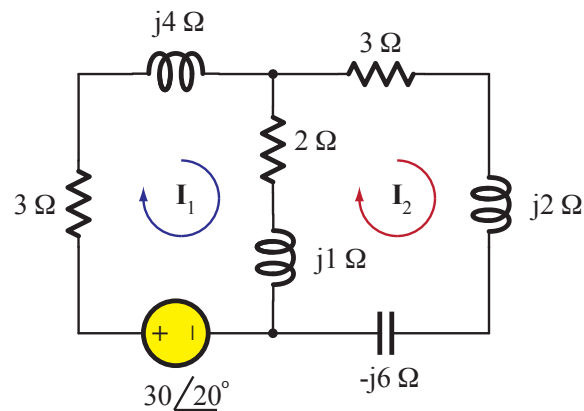1. [2 marks.] Use the mesh-current method to determine \mathbf{I}_1 and \mathbf{I}_2 in the following circuit, then choose the phasor diagram that correctly displays their values.




(e) None of the above.

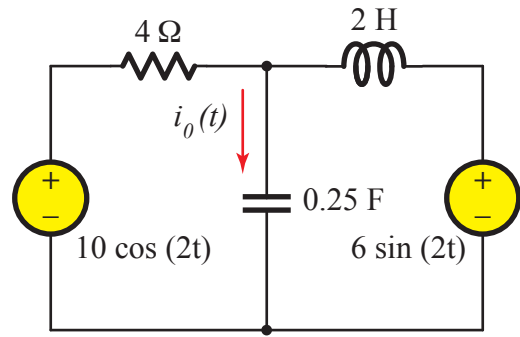
2. [2 marks.] Use the mesh-current method to find the current $i_0(t)$ in the circuit shown at right. Give just the peak current in *Ampères*.
3. [1 mark.] For Question #2 above, give the phase angle θ of $i_0(t)$ in degrees such that $-180^\circ \leq \theta < 180^\circ$.



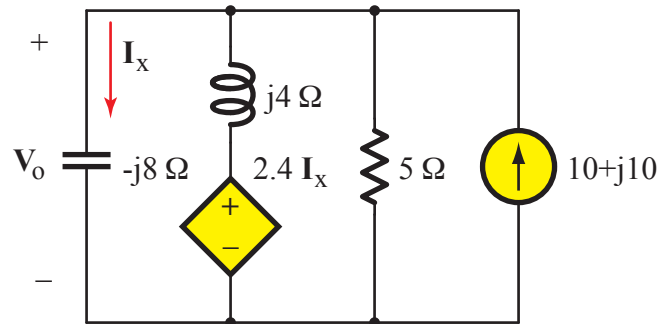4. [2 marks.] Use the node-voltage method to find the phasor voltage \mathbf{V}_O in the circuit at right. Give just the peak voltage of \mathbf{V}_O in *Volts*.
5. [1 mark.] For Question #4 above, give the phase angle θ of \mathbf{V}_O in degrees such that $-180^\circ \leq \theta < 180^\circ$.



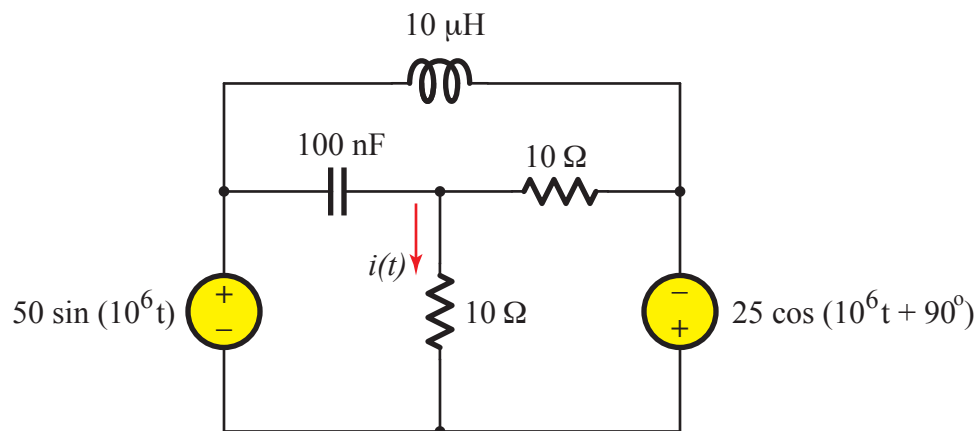6. [2 marks.] Use the node-voltage method to find the current $i(t)$ in the following circuit. Give just the peak amplitude of $i(t)$ in *Ampères*.



7. [2 marks.] Determine the Thévenin equivalent circuit at terminals **a** and **b**. Give just the peak voltage $V_t = V_{ab}$ in *Volts*.
8. [1 mark.] For Question #7 above, give the magnitude of the Thévenin impedance Z_t in *Ohms*.

