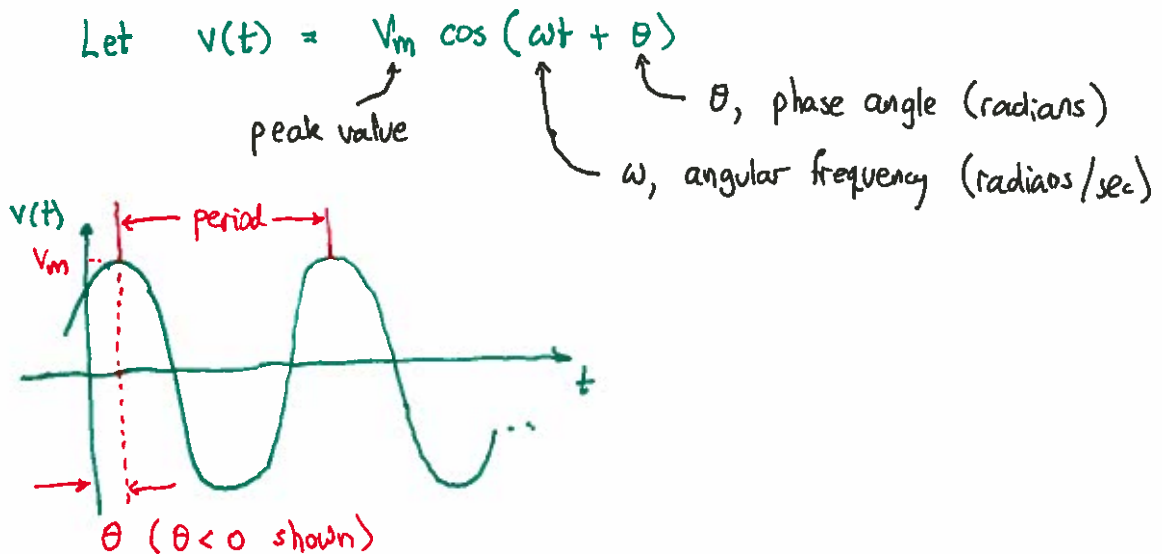


STEADY-STATE SINUSOIDAL ANALYSIS

So far, we have considered circuits in which sources are DC. We now investigate circuits where sources deliver sinusoidal (AC) currents and voltages

- methods of analysis are identical
- arithmetic changes from real to complex

Sinusoidal currents and voltages

The sinusoid is periodic with period T . We have one complete period when the angle increases by 2π .

$$\omega t \Big|_{t=T} = 2\pi, \quad \text{so } \omega T = 2\pi$$

$$\text{and } T = \frac{2\pi}{\omega}$$

Frequency is defined as the number of complete periods (cycles) per second

$$f = \frac{1}{T}, \quad f = \text{frequency in Hertz (Hz)}$$

We also have

$$\omega = \frac{2\pi}{T}, \quad \text{so } \omega = 2\pi f \text{ rads/sec.}$$

By convention, we use cosine and not sine. They are related by

$$\begin{aligned}\sin(\omega t) &= \cos(\omega t - \pi/2) \\ &= \cos(\omega t - 90^\circ)\end{aligned}$$

We say $\sin(\omega t)$ has a phase angle of -90° .

Root-mean-square values

We often express voltages and currents in terms of their peak values, V_m, I_m , but also in terms of their root-mean-square (rms) values).

Consider power in a resistor over one period of the waveforms. Instantaneous power is

$$p(t) = v(t)i(t) = v(t)\frac{v(t)}{R} = \frac{v^2(t)}{R}$$

The energy over one period is $E_T = \int_0^T p(t) dt$

An important measure is average power over one period.

$$\begin{aligned}P_{\text{avg}} &= \frac{E_T}{T} = \frac{1}{T} \int_0^T p(t) dt \\ \text{or } P_{\text{avg}} &= \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt\end{aligned}$$

which can be expressed as

$$P_{\text{avg}} = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R} = \frac{V_{\text{rms}}^2}{R}$$

Thus, we define rms voltage

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

(The integral is labeled "mean" with a bracket underneath, and the square root is labeled "root" with an arrow pointing to it. A red arrow labeled "square" points to the $v^2(t)$ term.)

Rms values are sometimes called effective values. In the real world,

- AC voltages are specified in rms, not peak (e.g., household voltages are 120V)
- Power is average power, not instantaneous power (e.g., a 100 W light bulb uses 100 W of average power)

Relating to DC circuits

$$v(t) = V_m \cos(\omega t + \theta), \text{ where } \omega = \omega, \theta = 0$$

$$\text{so } v(t) = V_m$$

$$\text{and also } v(t) = V_{rms} = V_m$$

$$i(t) = I_{rms} = I_m$$

$$p(t) = P_{avg}$$

For sinusoidal voltages and currents, peak and rms values are not equal.

It can be shown that

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad \begin{array}{l} \text{SINUSOIDAL} \\ \text{RMS VALUE} \end{array}$$

The voltage in your home is $V_{rms} = 120\text{V}$, so

$$v(t) = 120\sqrt{2} \cos(\omega t + \theta), \text{ where } \omega = 2\pi f$$

$$= 2\pi \times 60 \text{ Hz}$$

$$v(t) = 169.7 \cos(120\pi t + \theta)$$

Example: Let $v(t) = 10 \sin(1000\pi t + 30^\circ)$

Express as a cosine, give angular frequency, frequency in Hz, the rms voltage, and average power in a 10Ω resistor.

We have

$$v(t) = 10 \sin(1000\pi t + 30^\circ)$$

$$= 10 \cos(\underbrace{1000\pi t + 30^\circ - 90^\circ}_{\text{angular frequency}})$$

$$\omega = 1000\pi \text{ rad/sec}$$

$$f = \omega/2\pi = 500 \text{ Hz.}$$