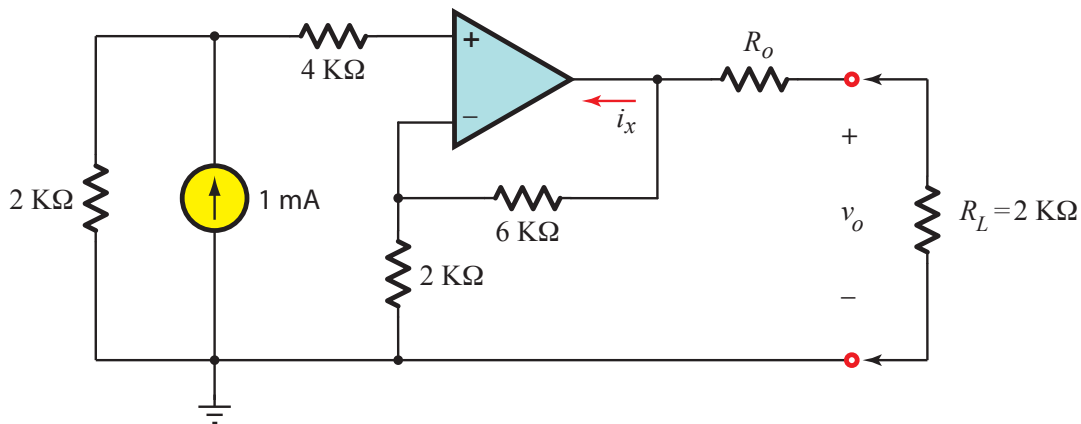


University of Calgary  
Department of Electrical and Computer Engineering  
ENGG 225 - Fundamentals of Electrical Circuits and Machines  
Winter, 2017


Problem Assignment #5

Please solve the operational amplifier problems below. Unless otherwise stated, express all your currents in Amperes, and voltages in Volts.


1. [1 mark.] In the circuit below, let  $R_o = 500\ \Omega$ . Determine the output voltage  $v_o$  with the  $2\ \text{K}\Omega$  load resistance attached as shown.



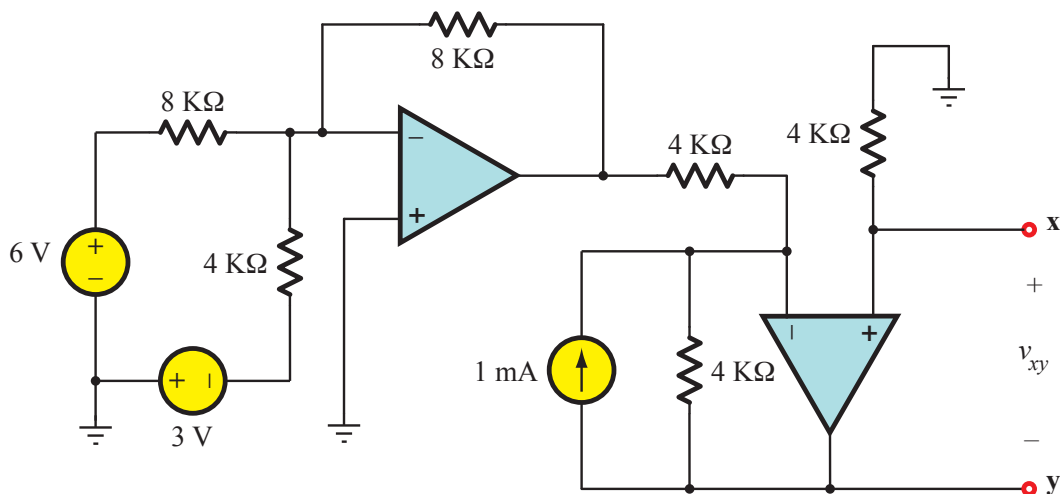
2. [1 mark.] In Problem 1 above, using the same values of  $R_o$  and  $R_L$ , calculate the current  $i_x$ . Express your answer in *milliAmperes (mA)*.
3. [2 marks.] Use superposition to analyze the following circuit, and find the output voltage  $v'_{xy}$  due to the  $3\text{-V}$  source acting alone.



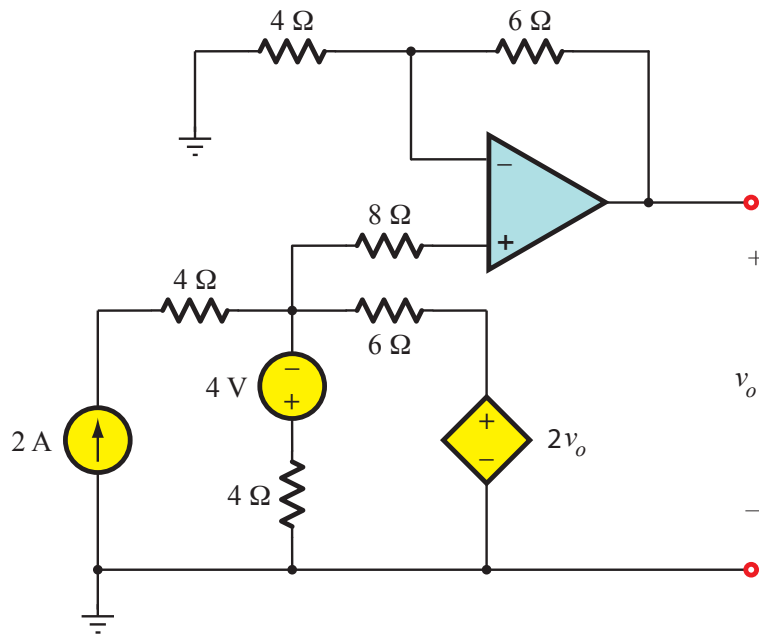
4. [2 marks.] Determine the output voltage  $v_o$  in the following circuit.



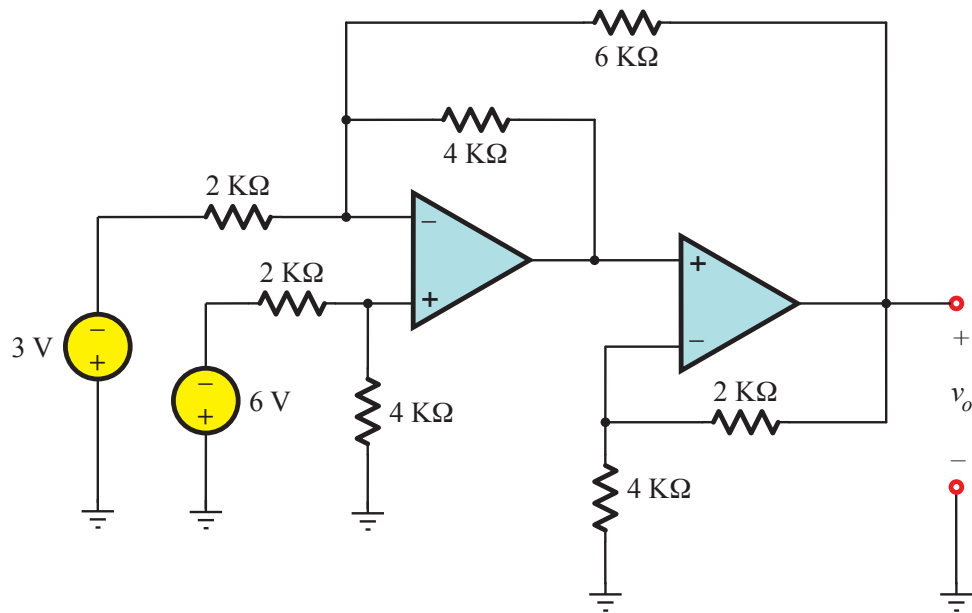5. [2 marks.] Determine the output voltage  $v_o$  in the following circuit.



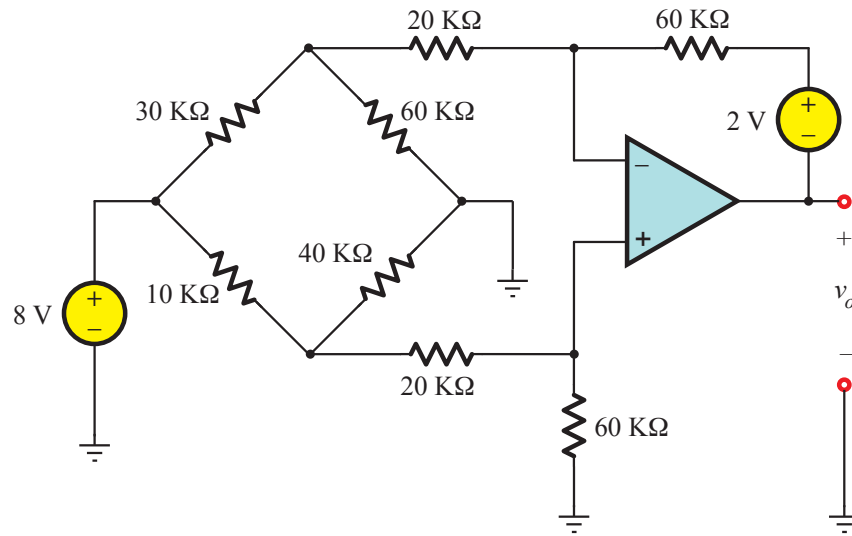6. [2 marks.] Determine the output voltage  $v_o$  in the following circuit.



7. [2 marks.] Determine the output voltage  $v_o$  in the following circuit.

