

University of Calgary  
Department of Electrical and Computer Engineering


ENGG 225 - Fundamentals of Electrical Circuits and Machines  
Winter, 2017

*Problem Assignment #1*


**Comments on D2L Data Entry:**

Calculate the numerical answers to the problems below, and enter them into Quiz #1 on D2L using four significant figures. For example, if an answer is 4.3957734, enter 4.396 when prompted by D2L. If an answer is a whole number, say -2, you may enter -2, -2.0, 2.00, or -2.000. For very large numbers or very small numbers, you may use scientific notation, such as 1.609e-19.

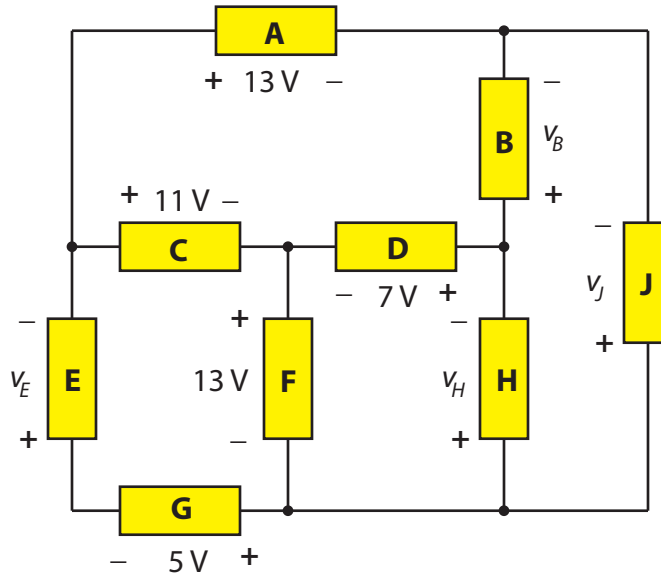
1. [1 mark.] A constant current of 4A for 20 hours is required to charge an automotive battery having a voltage at its terminals of  $v(t) = 12(1 + e^{-t/20})$  V, where  $t$  is in hours. Assuming an electricity cost \$0.19 per KWh, what is the cost to charge the battery? Give your answer in dollars.
2. [1 mark.] The current flowing through a device is  $i(t) = 120(1 + \cos(100\pi t))$  A. Calculate the total charge flow through the device over one period from  $t = 0$  to  $t = 10$  ms. Express your answer in Coulombs.
3. [1 mark.] Find  $v_E + v_H + v_J$  in the following circuit. Express your answer in Volts.



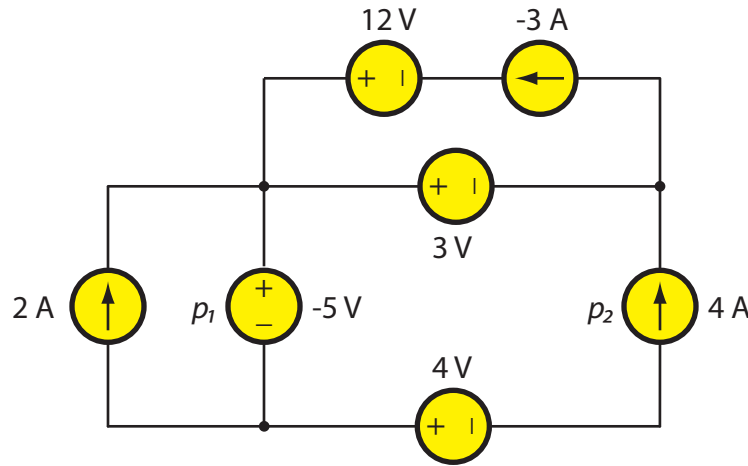4. [2 mark.] In the circuit below, use KVL and KCL to determine the power  $p_1 + p_2$ . Express your answer in Watts using the correct sign.



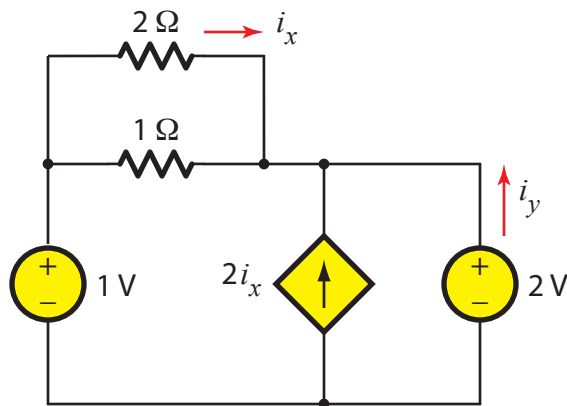5. [2 marks.] In the circuit below, use KCL, KVL, and Ohm's Law to determine the current  $i_y$  in the 2 V source. Express your answer in Amperes.



6. [2 mark.] Use KCL, KVL, and Ohm's Law to determine the power in the voltage source below. Express your answer in Watts using the correct sign.

