

Thursday, February 4,
2016

$$\begin{aligned} (\times 6000) \quad 5V_a - 75 + 20V_a + 24V_a - 24V_b &= 0 \\ 49V_a - 24V_b &= 75 \end{aligned} \quad (1)$$

$$\text{Node b: } \frac{V_b - 15}{1000} + \frac{V_b}{200} + \frac{V_b - V_a}{250} = 0$$

$$\begin{aligned} (\times 1000) \quad V_b - 15 + 5V_b + 4V_b - 4V_a &= 0 \\ -4V_a + 10V_b &= 15 \end{aligned} \quad (2)$$

$$\text{So } V_b = \frac{15 + 4V_a}{10}$$

Substitute into (1)

$$49V_a - \frac{24}{10}(15 + 4V_a) = 75$$

$$39.4V_a = 111$$

$$\text{so } V_a = 2.817\text{V}$$

From (2),


$$V_b = 2.627\text{V}$$

Power in 250Ω resistor:

$$P_{250} = \frac{(V_a - V_b)^2}{250\Omega} = 0.144\text{ mW}$$

The mesh-current method

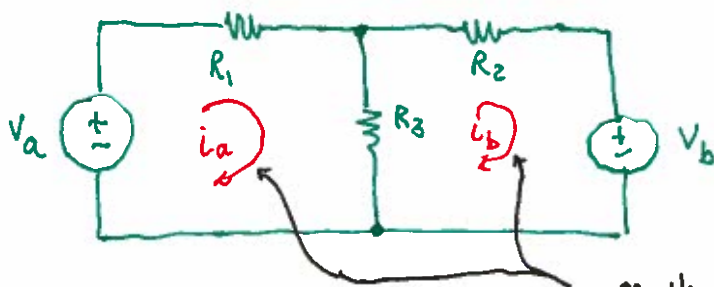Another useful systematic method of circuit analysis.




circuit must be planar
(i.e., no crossing conductors)

mesh currents


- imagined currents circulating in a closed, or mesh.

Mesh currents are different from branch currents

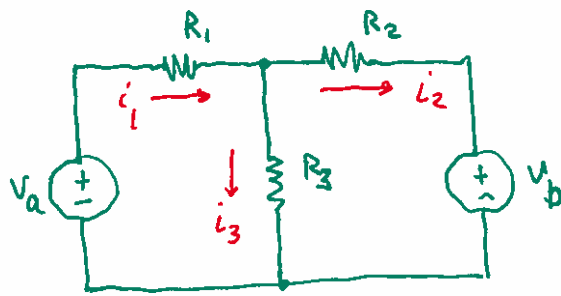- we use branch currents to write KCL equations.
- branch currents can be measured with an ammeter.



branch currents,
where $i_1 = i_2 + i_3$

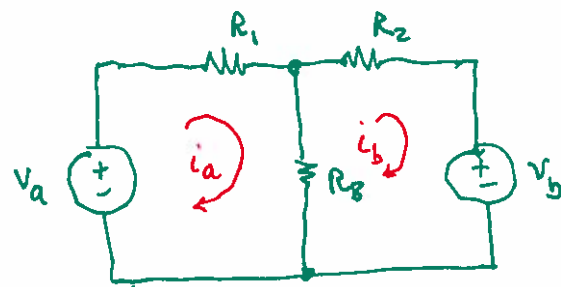


mesh currents, where
 $i_1 = i_a$
 $i_2 = i_b$
 $i_3 = i_a - i_b$

Three main steps in mesh-current analysis.


1. Identify meshes
2. Write mesh-current equation for each mesh; develop a system of equations.
3. Solve for mesh equations

Step 1: Identify meshes

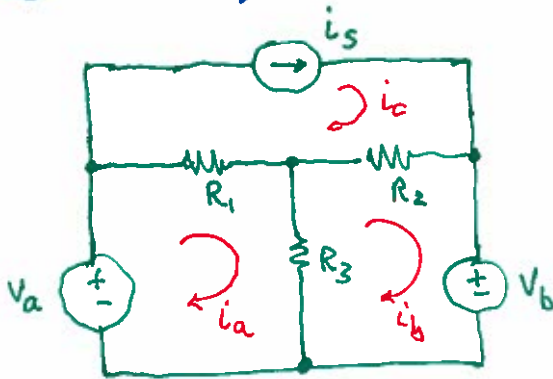


- Imagine circuit as a window with panes; assign a mesh current to each pane.

Note the upper current source in mesh c.

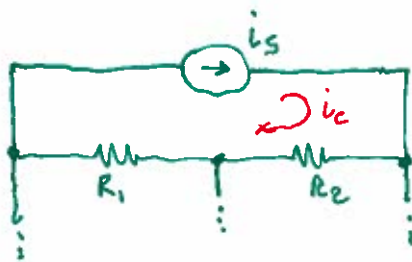

i_s forces the mesh current to be $i_c = i_s$
 (i_c known immediately).


Step 2: Form mesh equations in each mesh

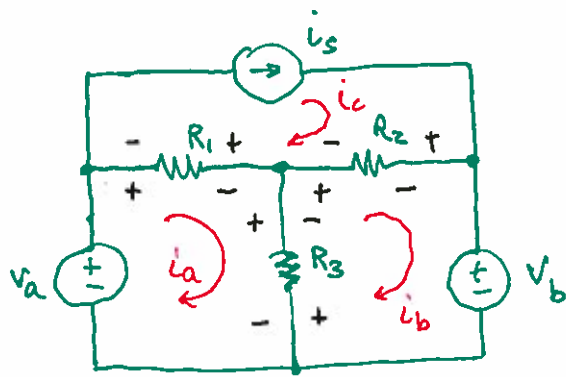

Labeling the circuit:

Indicate a polarity on each resistor inside each mesh in response to the mesh current in that mesh.

Consider R_1 :

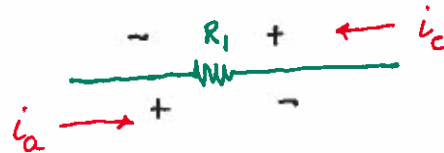

Now consider mesh a. Voltages around the mesh must sum to zero by KVL.

To find voltages across resistors, we need to determine the branch current in terms of mesh currents.

