

Node b: $\frac{V_b - V_a}{20} + \frac{V_b}{5} - 1 = 0$

Friday, February 12,
2016

$$\begin{aligned} (x20) \quad V_b - V_a + 4V_b - 20 &= 0 \\ -V_a + 5V_b &= 20 \end{aligned}$$


(2)

From (2), $V_a = 5V_b - 20$

Into (1) $5(5V_b - 20) - V_b = 60$
 $24V_b = 160$

$\therefore V_b = V_a = V_{oc} = 6.667 \text{ V}$

Now find i_{sc}

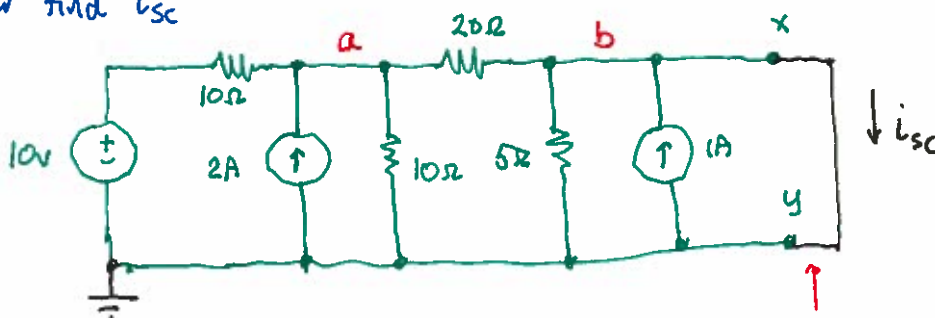

General observation:

Note this changes the circuit.
 Usually must treat circuit as
 a whole new analysis problem.

Node b is again attached
 to the reference node, $V_b = 0$

Node a: $\frac{V_a - 10}{10} + \frac{V_a}{10} - 2 + \frac{V_a - V_b}{20} = 0$ (Note: $V_b = 0$)

(x20) $2V_a - 20 + 2V_a - 40 + V_a = 0$

$5V_a = 60$, so $V_a = 12 \text{ V}$

For node b, we know $V_b = 0$, but we write a node equation
 with unknown current i_{sc} .

Node b: $\frac{V_b - V_a}{20} + \frac{V_b}{5} - 1 + i_{sc} = 0$
 (Note: $V_b = 0$)
 5Ω resistor shorted out
 (no current)


$-\frac{V_a}{20} - 1 + i_{sc} = 0$

$$i_{sc} = 1 + \frac{12}{20} = 1.6 \text{ A}$$

Therefore, $R_t = \frac{V_t}{i_{sc}} = \frac{6.667}{1.6}$

$$R_t = 4.1667 \Omega$$

Thevenin equivalent

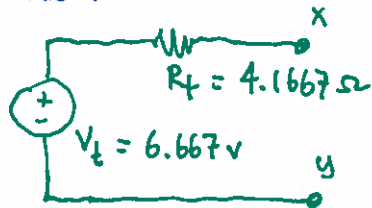


Shortcut method for finding Thevenin resistance


If a circuit has no dependent sources, then we may use an alternative method to find R_t by zeroing the sources.

We zero their values and use their "effective" resistance.

E.g.,

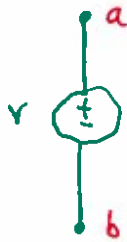

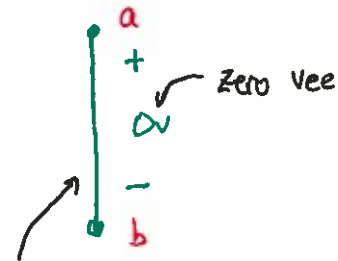
If we let $V=0$, the source becomes a short circuit.



Effective resistance = 0Ω



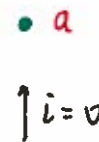
Let $i=0$, then the source becomes an open circuit.



Effective resistance = $\infty \Omega$

Repeat Example #2

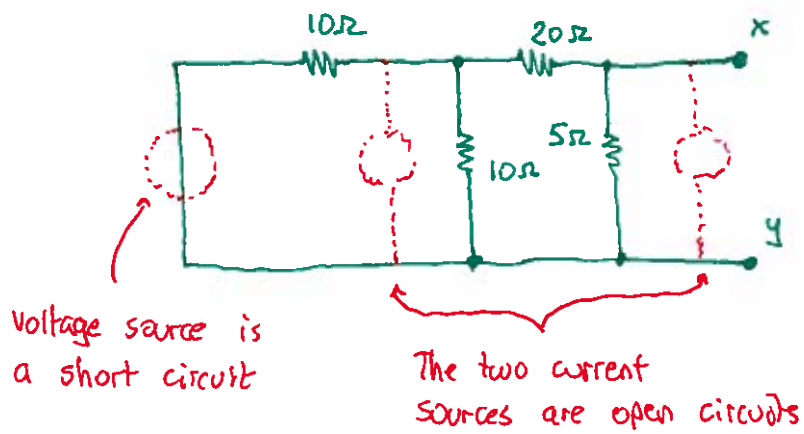Use $V_t = 6.667 \text{ V}$. Solve for R_t by zeroing the sources.



Series-parallel combination of resistors

$$R_t = [(10 \parallel 10) + 20] \parallel 5$$

↑
in parallel with

$$= (5 + 20) \parallel 5$$


$$= \frac{25 \times 5}{25 + 5} = 4.1667 \Omega$$

Thevenin equivalents with dependent sources

The above short-cut method cannot be used if a circuit has dependent sources.

Must determine i_{sc} , the $R_t = V_t / i_{sc}$

Example 1: Find Thevenin equivalent

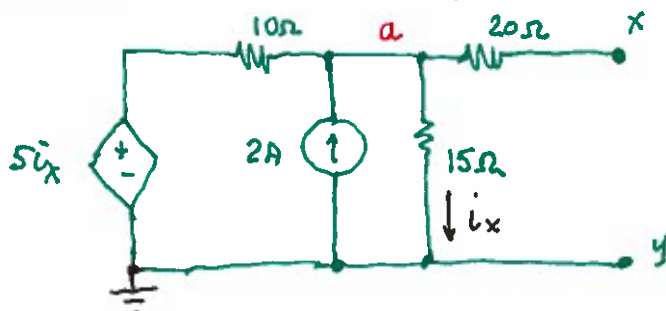

First, find V_t . With the terminals x, y open-circuited, no current flows in 20Ω resistor, so $V_t = V_{oc} = V_a$.