

Formulas needed for the final exam

A separate formula sheet is not allowed in ENGG 225.

Here's what you will be provided on the exam paper itself.

Machine equations and conversions:

$T_{dev} = K\phi I_a$	GIVEN
$E_A = K\phi \omega_m$	
$P = T\omega_m$	


Also given: $1 \text{ Ht} = 746 \text{ W}$

$$\omega_m (\text{rad/sec}) = n_m (\text{revs/min}) \times 2\pi (\text{rads/rev}) \times \frac{1}{60} (\text{mins/sec})$$

$$\omega_m = n_m \frac{2\pi}{60} \longleftrightarrow n_m = \frac{60}{2\pi} \omega_m$$

Important stuff to remember (which is not given)


L s and C s

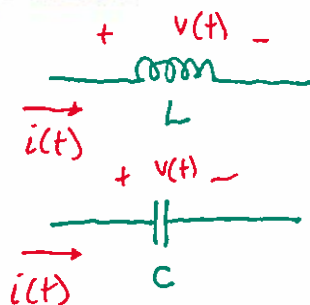

$$v(t) = L \frac{di(t)}{dt}, \quad Z_L = j\omega L$$

$$i(t) = C \frac{dv(t)}{dt}, \quad Z_C = \frac{1}{j\omega C}$$

DC Power

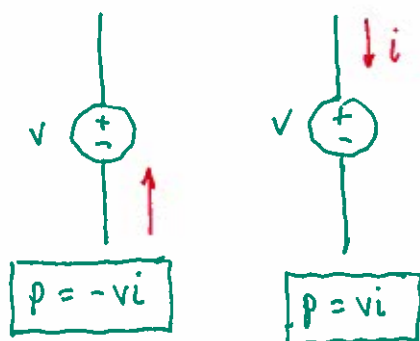

$p > 0$ absorbed
$p < 0$ delivered

Passive reference convention applies to AC circuits as well.

AC Power

P (power, or average power)

$$P = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

Q (reactive power)

$$Q = \frac{V_{rms}^2}{X} = I_{rms}^2 X$$

(X)

$$P = I_{rms} V_{rms} \cos(\theta)$$

$$Q = I_{rms} V_{rms} \sin(\theta)$$

↑ power angle
 $\theta = \theta_V - \theta_I$

where $X = |Z_L| = \omega L$

for an inductor

$$X = |Z_C| = 1/\omega C$$

for a capacitor


Complex power \bar{S}

$$\bar{S} = P + jQ = \frac{1}{2} \bar{V} \bar{I}^*$$

Power triangle

Apparent power

$$P_{app} = \sqrt{P^2 + Q^2} = |\bar{S}|$$

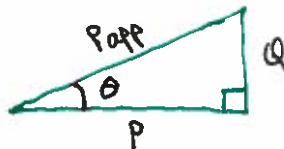

Past exams are very helpful!

Questions to ignore on past exams

- all questions with switches (i.e., transient analysis problems) - not covered any more in ENGG 225.
- all questions with ^{diodes} (never on ENGG 225 topic)

Tips on AC circuit analysis

1. Properly setting up and manipulating equations is the most important part
 - smaller weighting on correct answers
2. If you struggle through pages of complex number manipulation...

GIVE UP!

Tips on solving op-amp circuits


Casual observation:

- The difficulty of solving op-amp circuits is inversely proportional to size.


Tips:

1. Node-voltage equations at op-amp input terminals are often all that's needed.

2. Summing-point constraints

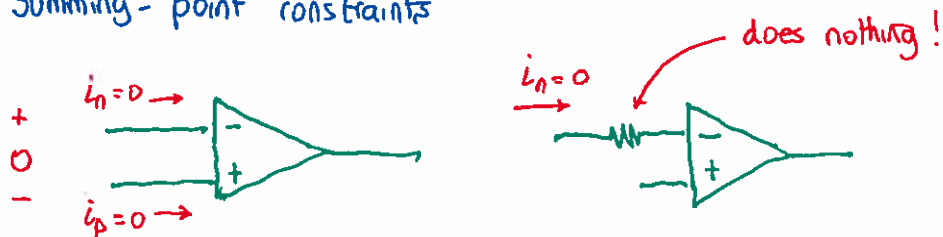

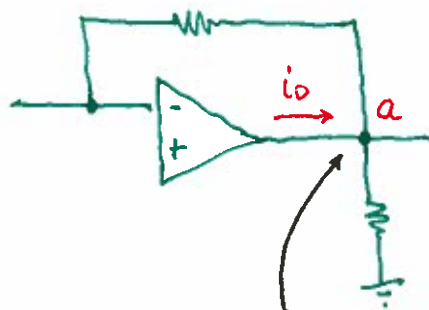3. Don't write an equation at the output unless you need to



write an equation at node a
only if you need to find i_o

- equation is wrong without it.