


Superposition in AC circuits

As with other methods of AC circuit analysis, the procedure is identical, except using complex algebra!

- Important: this method is the only way to analyze circuits with sources with different frequencies.

Power in AC circuits

Consider an arbitrary complex impedance

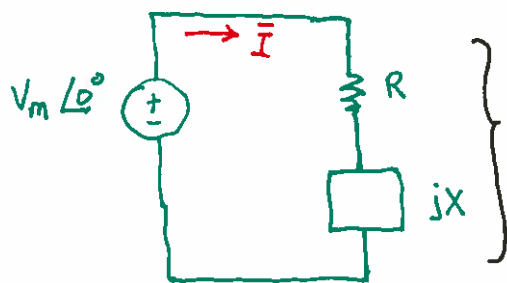

load impedance

$$Z = R + jX$$

$$= |Z| \angle \theta$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1}\left(\frac{X}{R}\right)$$

R - resistive part

X - "reactive" part

We have phasor current \bar{I}

$$\bar{I} = \frac{V_m \angle 0^\circ}{|Z| \angle \theta} = \frac{V_m}{|Z|} \angle -\theta$$

$$\text{and let } I_m = \frac{V_m}{|Z|}, \text{ so } \bar{I} = I_m \angle -\theta$$

We will investigate four cases:

1. A resistor
2. Inductor
3. Capacitor
4. General load.

1. Purely resistive load ($X=0$)


We have

$$\left. \begin{aligned} v(t) &= V_m \cos(\omega t) \\ i(t) &= I_m \cos(\omega t) \end{aligned} \right\} \text{in phase} \quad v(t) = R i(t)$$

And power is $p(t) = v(t)i(t) = V_m I_m \cos^2(\omega t)$

Using the identity $\cos^2(x) = \frac{1}{2} [1 + \cos(2x)]$
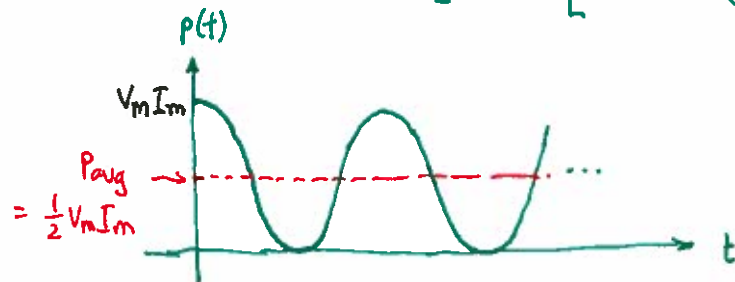
$$p(t) = \frac{1}{2} V_m I_m [1 + \cos(2\omega t)]$$



← always positive — resistor only absorbs power.

2. Purely inductive ($R=0, X > 0$)

For the inductor, $Z = j\omega L = \omega L \angle 90^\circ$, so $\theta = 90^\circ$

$$v(t) = V_m \cos(\omega t)$$


$$i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$

Power: $p(t) = v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t)$

Using the identity $\cos(x) \sin(x) = \frac{1}{2} \sin(2x)$

$$\text{so } p(t) = V_m I_m \cos(\omega t) \sin(\omega t)$$

$$= \frac{V_m I_m}{2} \sin(2\omega t)$$

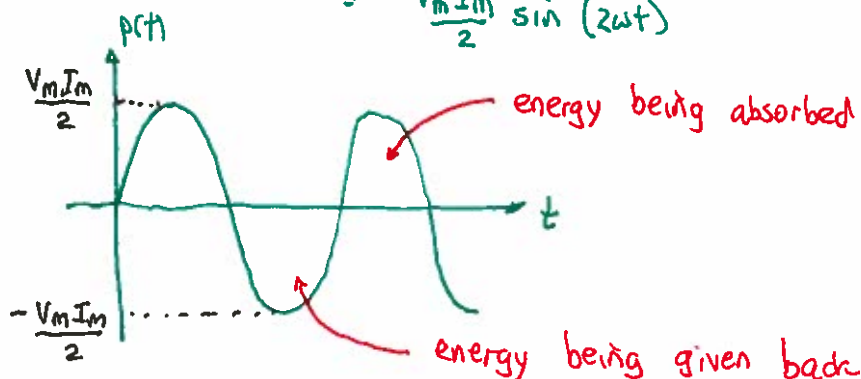

This is called reactive power — average is zero.