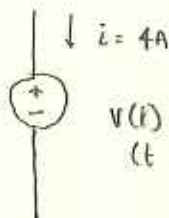


Question 1



$$v(t) = 12(1 + e^{-t/20}) \text{ V}$$

(t is in hours)

Note that battery is being charged, implying that it is absorbing power.

$$\text{We have } p(t) = i v(t) = 48(1 + e^{-t/20}) \text{ W}$$

Energy is defined as  $w = \underbrace{\int_{t_0}^{t_1} p(t) dt}_{\text{need this part of the energy calculation for } t=0 \text{ to } 20 \text{ hours}} + w(t_0)$

$$\begin{aligned} w &= 48 \int_0^{20} (1 + e^{-t/20}) dt = 48 \left[ t - 20e^{-t/20} \right] \Big|_0^{20} \\ &= 48 \left[ 20 - 20e^{-20/20} - 0 + 20 \right] \\ &= 48 \left[ 32.642 \right] = 1566.836 \text{ Wh} \end{aligned}$$

$$\text{so } w = 1.5668 \text{ kWh}$$

Given the cost of \$0.19 per kWh, the cost over 20 hours is

$$\begin{aligned} \text{cost} &= \$0.19 / \text{kWh} \times 1.5668 \text{ kWh} \\ &= \boxed{\$0.2977} \end{aligned}$$

Question 2

We have  $i(t) = 120(1 + \cos(100\pi t))$  A. Relating current and charge  $q$ , we also have

$$i(t) = \frac{dq(t)}{dt} \quad \text{and} \quad q(t) = \underbrace{\int_{t_0}^{t_1} i(t) dt}_{\text{need this part of the calculation for } t_0 = 0 \text{ and } t_1 = 0.01 \text{ s}} + q(t_0)$$

need this part of the calculation for  $t_0 = 0$  and  $t_1 = 0.01 \text{ s}$ .

$$q = 120 \int_0^{0.01} (1 + \cos(100\pi t)) dt$$

$$\text{so } q = 120 \left[ t + \frac{1}{100\pi} \sin(100\pi t) \right] \Big|_0^{0.01}$$

$$\text{giving } q = 120 \left[ 0.01 + \frac{1}{100\pi} \sin(\pi) - 0 - \frac{1}{100\pi} \sin(0) \right]$$

$$q = 120 (0.01) \text{ C} = \boxed{1.2 \text{ C}}$$

### Question 3

There are different ways to solve this. Below is one way

$$\text{In loop ECFG, KVL gives } 5 + V_E + 11 + 13 = 0$$

$$V_E = -29 \text{ V}$$

$$\text{In loop EAJG, KVL gives } 5 + V_E + 13 - V_J = 0$$

$$5 - 29 + 13 - V_J = 0$$

$$V_J = -11 \text{ V}$$


$$\text{In loop FDA, KVL gives } -13 - 7 - V_H = 0$$

$$V_H = -20 \text{ V}$$

$$\text{Finally, } V_E + V_H + V_J = -29 - 11 - 20$$

$$= \boxed{-60 \text{ V}}$$

### Question 4

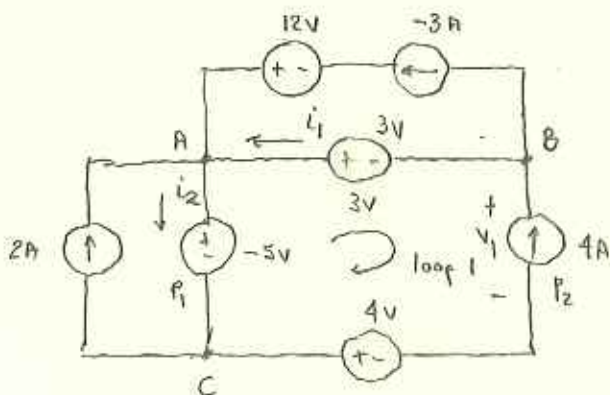

At node B, KCL gives

$$4 - i_1 - (-3) = 0$$

$$\text{so } i_1 = 7 \text{ A}$$

At node A, KCL gives

$$(-3) + i_1 + 2 - i_2 = 0$$

$$-3 + 7 + 2 = i_2$$

$$\text{so } i_2 = 6 \text{ A}$$

Observation: Performing KCL at node B was unnecessary; it would have been fine to recognize that the 4A splits at B, then recombines at A,  $4 + 2 - i_2 = 0$ , so  $i_2 = 6A$ .

Alternatively, KCL at node C!

Power  $P_1 = (-5)i_2 = -30W$


Now, KVL around loop 1 gives  $-(-5) + 3 + V_1 - 4 = 0$   
so  $V_1 = -4V$

Power  $P_2 = -V_1(4) = 4 \times 4 = 16W$

Therefore,  $P_1 + P_2 = -30 + 16 = \boxed{-14W}$


### Question 5

Combining the two resistors in parallel,

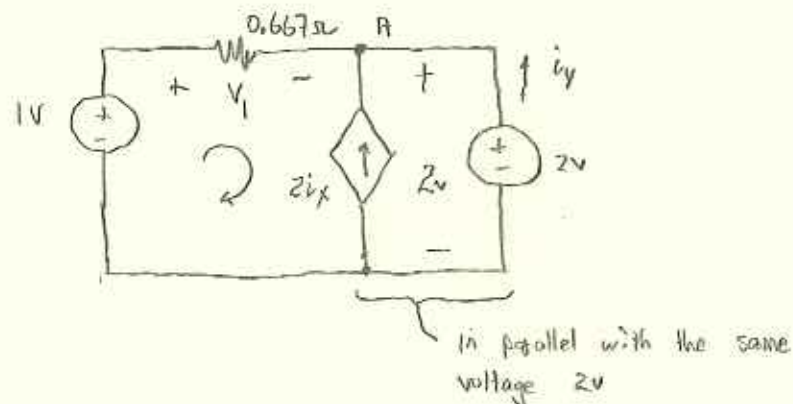

KVL around the loop gives  $-1 + V_1 + 2 = 0$   
 $V_1 = -1V$

Now consider the parallel resistors

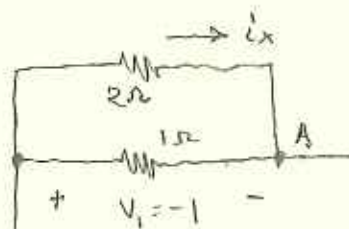

Ohm's law gives

$$i_x = \frac{V_1}{2\Omega} = -0.5A$$


At node A in the circuit, KCL gives

$$\frac{V_1}{1\Omega} + i_x + 2i_x + i_y = 0$$

$$\frac{-1}{1\Omega} - 0.5 + 2(-0.5) + i_y = 0$$

$$i_y = \boxed{2.5 \text{ A}}$$

### Question 6

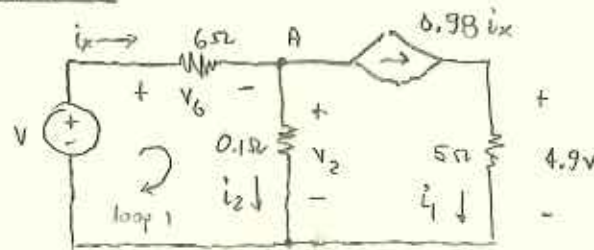

With 4.9V across the 5Ω resistor,  $i_1 = \frac{4.9}{5} = 0.98 \text{ A}$

This must also be the current in the dependent current source

$$0.98 i_x = i_1 = 0.98 \text{ A}$$

$$\text{so that } i_x = 1 \text{ A}$$

Then KCL at node A gives  $i_x - i_2 + 0.98 i_x = 0$   
 $1 - 0.98 = i_2$   
 so  $i_2 = 0.02 \text{ A}$

$$\text{This gives } V_2 = 0.02 \times 0.1\Omega = 0.002 \text{ V}$$

$$\text{KVL around loop 1: } -V + 6i_x + 0.002 = 0$$

$$V = 6.002 \text{ V}$$

Power in the voltage source:  $P = -V i_x = -6.002 \times 1$

$$P = \boxed{-6.002 \text{ W}}$$