

So for the dependent source,

$$V_2 = 2V_x = 2(V_3 - V_1)$$

(3)

Now solve for unknowns. Multiply (1) by 30

Monday, February 1,  
2016.

$$V_1(6+2+3) - V_2(2) - V_3(3) = 30$$

$$11V_1 - 2V_2 - 3V_3 = 30$$

From (3),  $11V_1 - 2[2(V_3 - V_1)] - 3V_3 = 30$

$$11V_1 - 4V_3 + 4V_1 - 3V_3 = 30$$

$$15V_1 - 7V_3 = 30$$

(4)

Multiply (2) by 10

$$-V_1 - V_2 + V_3(1+1+2) = 20$$

$$-V_1 - V_2 + 4V_3 = 20$$

From (3),  $-V_1 - 2(V_3 - V_1) + 4V_3 = 20$

$$V_1 + 2V_3 = 20$$

(5)

From equations (3), (4), (5),

$$V_1 = 5.405 \text{ V}$$


$$V_3 = 7.297 \text{ V}$$

$$V_2 = 2(V_3 - V_1) = 3.784 \text{ V}$$
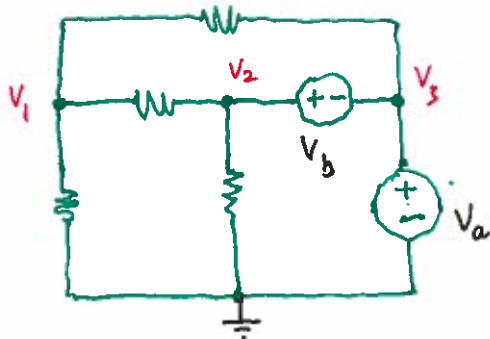
### Node-voltage method - special case

There is only one special case we need to handle, where we have voltage sources between nodes where neither node is a reference node

First, the easy case when voltage sources are connected directly to other voltage sources.



Notice that  $V_3 = V_a$


and also that  $V_2 - V_3 = V_b$

giving  $V_2 = V_3 + V_b$

$$V_2 = V_a + V_b$$

- $V_2$  and  $V_3$  are known! Don't need to write equations there.
- leaves one unknown (and one equation) at node 1.

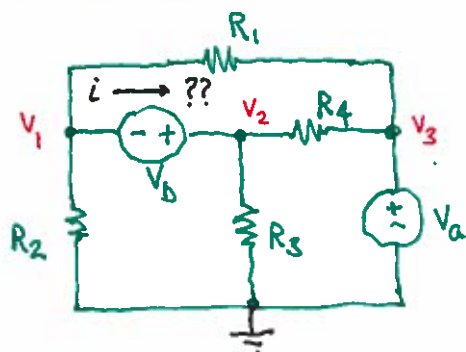Now the trickier case when sources not directly connected to each other.




Note  $V_3 = V_a$

Recall in writing node equations, we sum currents leaving nodes.  
But what's  $i$ ?

$$\text{node 1: } \frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1} + \textcircled{i} = 0 \quad (1)$$

another unknown, along with  $V_1, V_2$  (and we can't ignore it!)

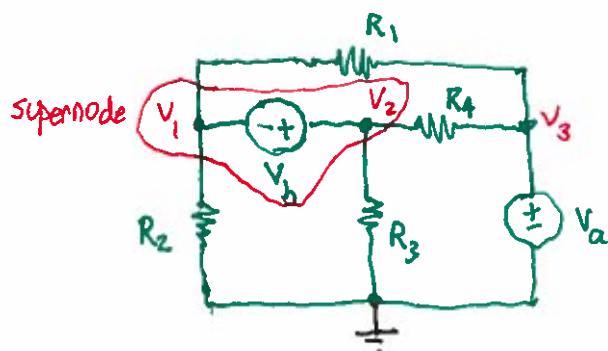The problem is handled by the concept of a supernode



Consider node 2 of the original circuit

$$\frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4} - i = 0 \quad (2)$$

Now, let's eliminate  $i$  by adding equations (1) and (2)

$$\frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1} + i + \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4} - i = 0$$

The result is a supernode equation, which we can write in one step.

$$\underbrace{\frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1}}_{\text{left side of supernode}} + \underbrace{\frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4}}_{\text{right side of supernode}} = 0$$

SUPERNODE EQUATION


We also have a dependence equation for the two nodes within the supernode.

$$\boxed{V_2 - V_1 = V_b}$$

DEPENDENCE EQUATION

The result is that we still have two equations to describe the nodes  $V_1$  and  $V_2$ : the supernode and dependence equations.

Example 1: Solve for node voltages

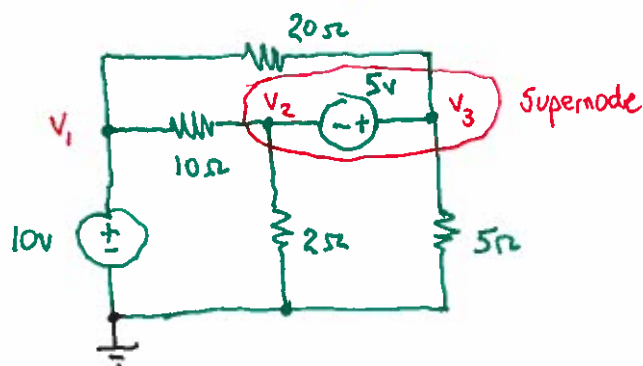

We know that  $V_1 = 10\text{V}$ .

Now write the supernode and dependence equation for  $V_2, V_3$ .

$$\underbrace{\frac{V_2 - V_1}{10} + \frac{V_2}{2}}_{V_2 \text{ side of supernode}} + \underbrace{\frac{V_3 - V_1}{20} + \frac{V_3}{5}}_{V_3 \text{ side of supernode}} = 0$$