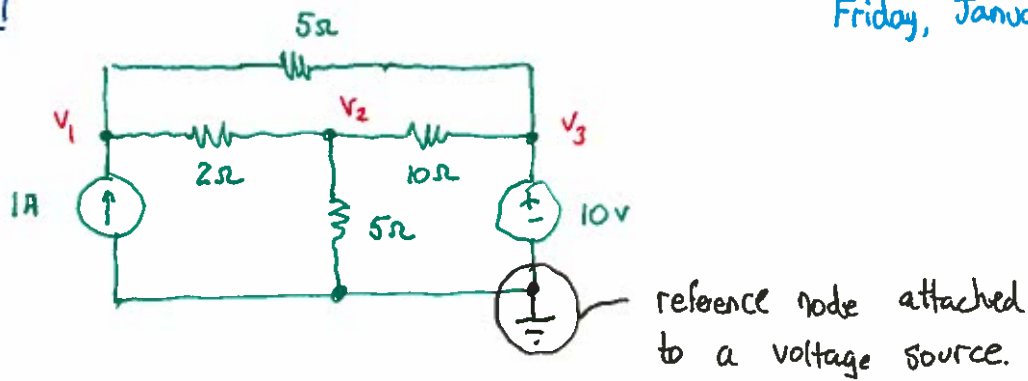


### Example 1

Friday, January 29, 2016



Looks like 3 nodes, with one ( $V_3$ ) fixed at 10V.

We may write

$$\text{Node } V_1: \frac{V_1 - V_2}{2} + \frac{V_1 - 10}{5} + (-1) = 0$$

1A forced into node 1.

$$\text{Node } V_2: \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{5} + \frac{V_2 - 10}{10} = 0$$

Can simplify to standard form:

$$\begin{aligned} \text{node 1 (x 10)} \quad 5V_1 - 5V_2 + 2V_1 - 20 + (-10) &= 0 \\ 7V_1 - 5V_2 &= 30 \end{aligned} \tag{1}$$

$$\begin{aligned} \text{node 2 (x 10)} \quad 5V_2 - 5V_1 + 2V_2 + V_2 - 10 &= 0 \\ -5V_1 + 8V_2 &= 10 \end{aligned} \tag{2}$$

Solving ...

$$\text{From (1), } V_1 = \frac{30 + 5V_2}{7} \tag{3}$$


$$\begin{aligned} \text{And from (2)} \quad -5 \left( \frac{30 + 5V_2}{7} \right) + 8V_2 &= 10 \\ -\frac{150}{7} - \frac{25}{7}V_2 + 8V_2 &= 10 \end{aligned}$$

$$4.429 V_2 = 31.429$$

$$\text{so } V_2 = 7.097 \text{ V}$$

$$\text{And from (3), } V_1 = 9.35$$

Example 2: Solve for node voltages

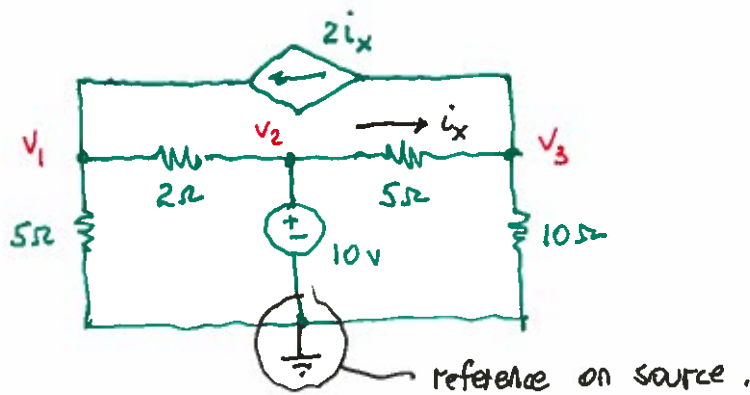

Three nodes again, one fixed by the voltage source  $V_2 = 10V$ .  
At nodes 1, 3:

$$\text{Node 1: } \frac{V_1 - 0}{5} + \frac{V_1 - V_2}{2} + (-2i_x) = 0$$

$$\text{Node 3: } \frac{V_3 - 0}{10} + \frac{V_3 - V_2}{5} + 2i_x = 0$$

this will be  $-i_x$

Simplifying with  $V_2 = 10$

$$\begin{aligned} 1 \text{ (x10)} \quad 2V_1 + 5(V_1 - 10) - 20i_x &= 0 \\ 7V_1 - 50 - 20i_x &= 0 \end{aligned} \quad (1)$$

$$\begin{aligned} 2 \text{ (x10)} \quad V_3 + 2(V_3 - 10) + 20i_x &= 0 \\ 3V_3 - 20 + 20i_x &= 0 \end{aligned} \quad (2)$$

We also have the dependent current source's controlling current  $i_x$ .  
Need to express this in terms of node voltages.

For the direction indicated,

$$i_x = \frac{V_x}{5} = \frac{V_2 - V_3}{5} \quad (3)$$

Substitute (3) into (1) and (2)


$$\begin{aligned} 7V_1 - 50 - 4(10 - V_3) &= 0 \\ 7V_1 + 4V_3 &= 90 \\ 3V_3 - 20 + 4(10 - V_3) &= 0 \\ -V_3 &= -20 \end{aligned}$$

equations fully  
in terms of  
node voltages.

$$\text{so } V_3 = 20 \text{ V}$$

$$\text{and } V_1 = 10/7 \text{ V.}$$

Example 3:

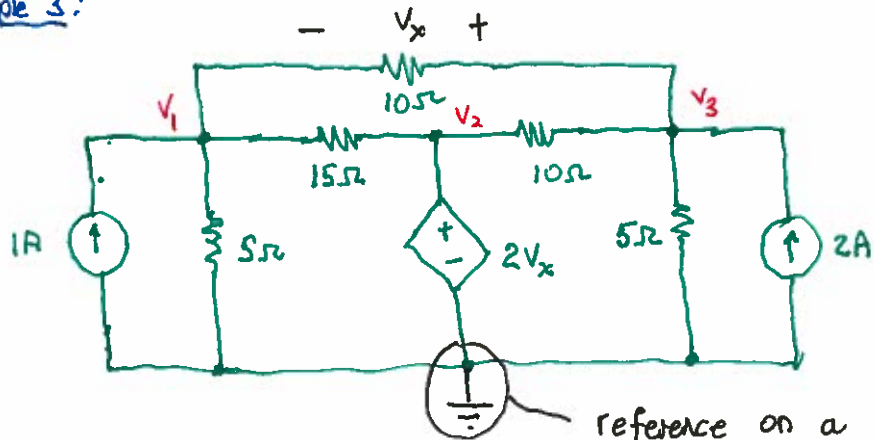

Three node voltages, where we know  $V_2 = 2V_x$ .

By rearranging, we see another important pattern in this equation:

$$\text{Node 1: } -1 + \frac{V_1}{5} + \frac{V_1 - V_2}{15} + \frac{V_1 - V_3}{10} = 0$$

$$V_1 \left( \frac{1}{5} + \frac{1}{15} + \frac{1}{10} \right) - V_2 \left( \frac{1}{15} \right) - V_3 \left( \frac{1}{10} \right) - 1 = 0$$

Sum of all conductances  
connected to node 1


conductance  
connecting nodes  
1 and 2

conductance  
connecting nodes  
1 and 3

current sources  
connected to  
node 1.

$$\text{Node 3: } \frac{V_3 - V_1}{10} + \frac{V_3 - V_2}{10} + \frac{V_3}{5} - 2 = 0$$

And we also have the dependence.

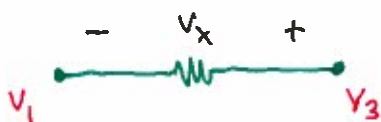

$$V_x = V_3 - V_1$$