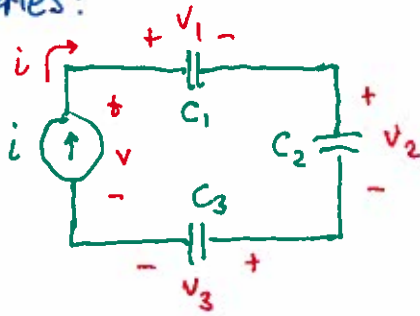


In series:



By KVL, we have

$$V = V_1 + V_2 + V_3$$

Assuming zero initial V_1, V_2, V_3

$$V = \frac{1}{C_1} \int_0^t i(x) dx + \frac{1}{C_2} \int_0^t i(x) dx + \frac{1}{C_3} \int_0^t i(x) dx$$

Or, equivalently,



$$V = \frac{1}{C_{eq}} \int_0^t i(x) dx$$

where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

SERIES CAPACITORS ARE
LIKE PARALLEL RESISTORS


Example: Given a capacitor, find voltage for a given current waveform. Assume no initial charge on the capacitor.

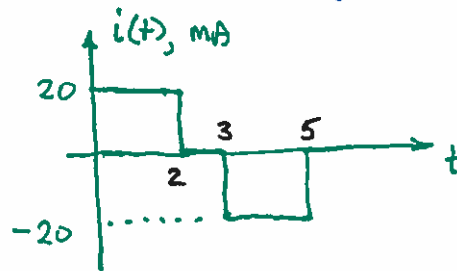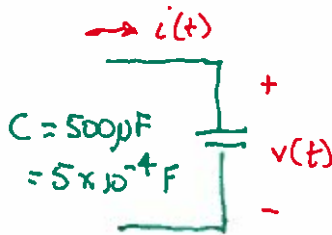For a capacitor, $i(t) = C \frac{dv(t)}{dt}$

$$\text{and } v(t) = \frac{1}{C} \int_0^t i(x) dx + v(0)$$

Time intervals:

$$0 < t \leq 2$$

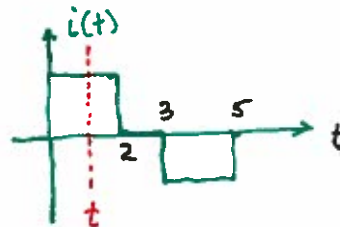

$$V(t) = \frac{1}{5 \times 10^{-4}} \int_0^t (20 \times 10^{-3}) dx = \left. \frac{(20 \times 10^{-3})x}{5 \times 10^{-4}} \right|_0^t$$

$$V(t) = 40t - 0 = 40t$$

$$2 < t \leq 3, \quad i(t) = 0$$

$$v(t) = \frac{1}{C} \int_2^t i(x) dx + v(2)$$

voltage on capacitor at end of the first interval.

$$\text{where } v(t) = v(2) = 40 \times 2 = 80\text{V}$$

$$3 < t \leq 5, \quad i(t) = -20\text{mA}$$

$$v(t) = \frac{1}{C} \int_3^t i(x) dx + v(3)$$


voltage on capacitor at end of the second interval = 80V

$$v(t) = \frac{(-20 \times 10^{-3})x}{5 \times 10^{-4}} \bigg|_3^t + 80$$

$$= -40(t-3) + 80$$

$$= -40t + 200$$

Sketch:

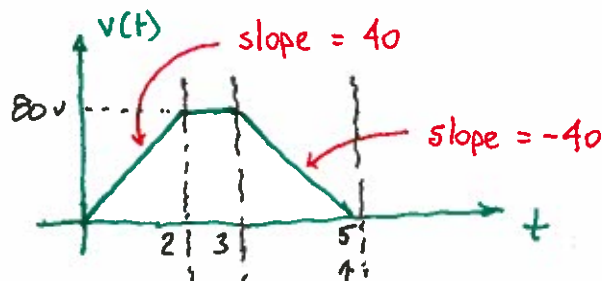


last interval $t > 5$, $i(t) = 0$, so

$$v(t) = v(5)$$

$$= -40 \times 5 + 200$$

$$= 0$$

What is the power?

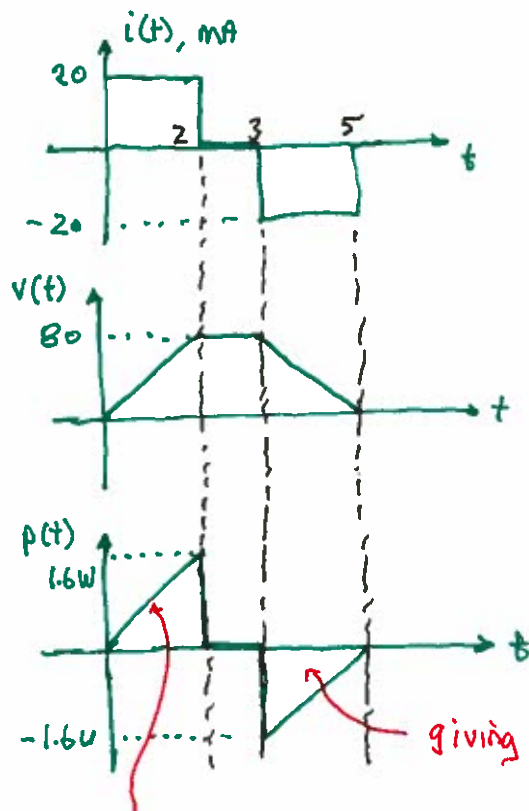

$$p = vi$$

capacitor is
absorbing energy

$$\text{Energy } W = \frac{1}{2} C v^2$$


The inductor

The circuit symbol



← circuit parameter for inductance.

Voltage-current relationship

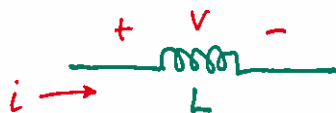

where

$$V = L \frac{di}{dt}$$

V = Voltage in Volts (V)

i = current in Amps (A)

t = time in secs (s)

L = inductance in Henrys (H)

Inductor properties:

- a constant value of current causes zero voltage drop,
So the inductor behaves like a short circuit