

$$v_L(t) = -\omega L I_m \sin(\omega t + \theta)$$

$$= -\omega L I_m \cos(\omega t + \theta - 90^\circ)$$

Monday, March 21,
2016

or $v_L(t) = \omega L I_m \cos(\omega t + \theta - 90^\circ + 180^\circ)$

$$= \omega L I_m \cos(\omega t + \theta + 90^\circ)$$

Now express in phasor form

$$i_L(t) = I_m \cos(\omega t + \theta) \longleftrightarrow \bar{I}_L = I_m \angle \theta$$

$$v_L(t) = \omega L I_m \cos(\omega t + \theta + 90^\circ) \longleftrightarrow \bar{V}_L = \omega L I_m \angle \theta + 90^\circ$$

We may write \bar{V}_L as

$$\bar{V}_L = \omega L \angle 90^\circ \times I_m \angle \theta = \omega L I_m \angle \theta + 90^\circ$$

$$= \underbrace{\omega L \angle 90^\circ}_{\omega L e^{j90^\circ}} \times \bar{I}_L$$

$$= \omega L \cos(90^\circ) + j\omega L \sin(90^\circ)$$

$$= j\omega L$$

Finally,

$$\bar{V}_L = j\omega L \times \bar{I}_L$$

The term $j\omega L$ is the inductor impedance Z_L


$$Z_L = j\omega L = \omega L \angle 90^\circ$$

IMPEDANCE OF AN
INDUCTOR, IN OHMS

and we have an equivalent expression for Ohm's Law

$$\bar{V}_L = Z_L \bar{I}_L$$


PHASOR EQUIVALENT
OF OHM'S LAW.

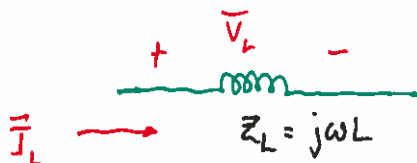

Note that the voltage leads the current by 90° (i.e., \bar{V}_L is 90° higher in phase than \bar{I}_L).

Capacitance

Recall for the capacitor,

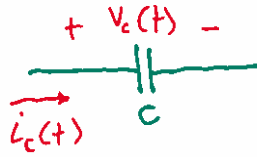

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

By the same analysis, we may write

$$\bar{V}_c = Z_c \bar{I}_c$$

where Z_c is the capacitor impedance given by

$$Z_c = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

IMPEDANCE OF A CAPACITOR, IN OHMS

Note that voltage lags current by 90° (i.e., \bar{V}_c is 90° less in phase than \bar{I}_c)

Resistance


Nothing new about the resistor!

$$\bar{V}_R = R \bar{I}_R$$

↖ real-valued constant (resistance)

\bar{V}_R and \bar{I}_R are exactly in phase.

Summary of impedances

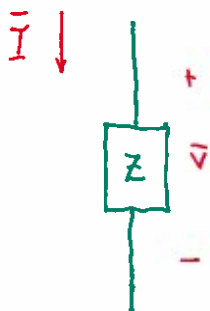

Inductor

$$\bar{V} = Z_L \bar{I}_L$$

$$Z_L = j\omega L$$

Capacitor

$$\bar{V} = Z_C \bar{I}_C$$

$$Z_C = \frac{1}{j\omega C}$$


Resistor

$$\bar{V} = R \bar{I}$$

$$Z_R = R.$$

Circuit analysis with phasors and complex impedances

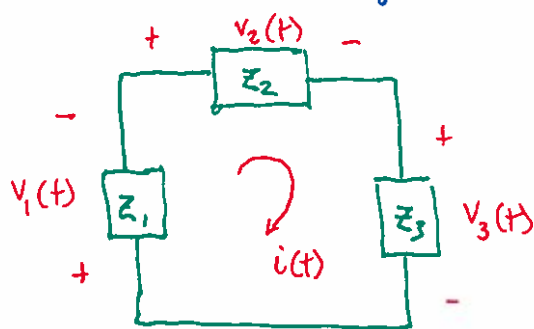KVL and KCL must always be satisfied, whether AC or DC



$$v_1(t) + v_2(t) + v_3(t) = 0$$



$$i_1(t) + i_2(t) + i_3(t) = 0$$

For sinusoidal AC circuits, we express KVL and KCL in terms of phasors.

$$\bar{V}_1 + \bar{V}_2 + \bar{V}_3 = 0$$

$$\bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 0$$

and we use phasor representation of voltage-current relationships


$$\bar{V} = Z \bar{I}$$

where Z is the complex impedance of an inductor, capacitor, or a resistor.

Analysis procedure:

- Use phasor for voltages and currents
- Use complex impedance Z
- then circuit analysis as usual!

Example 1: A complex voltage divider

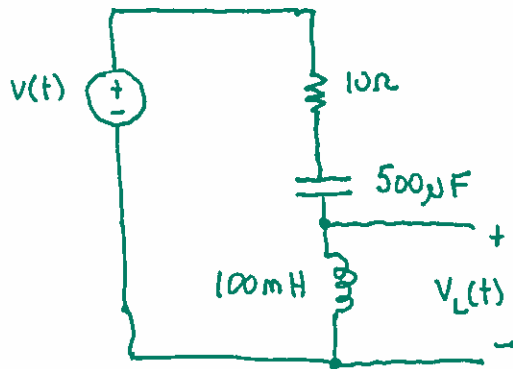


where

$$v(t) = 10 \cos(100t)$$

Find $v_L(t)$

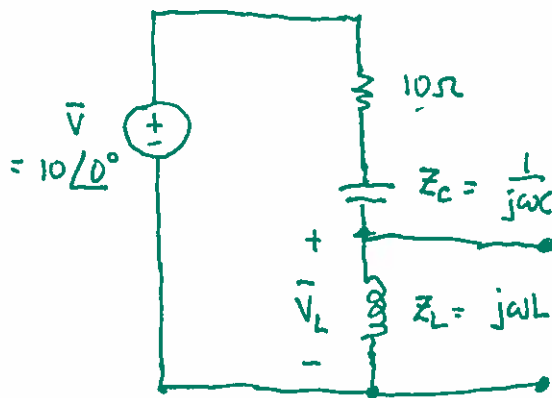Like resistors in series, impedances add. First, we need the impedances of everything using $\omega = 100$ rads/sec.



$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(100 \times 500 \times 10^{-6})} = -j20\Omega$$

$$Z_L = j\omega L = j(100 \times 0.1) = j10\Omega$$

Reminder: $\frac{1}{j} = -j$

$$\rightarrow \frac{1}{j} \cdot \frac{j}{j} = \frac{j}{j^2} = \frac{j}{-1} = -j$$