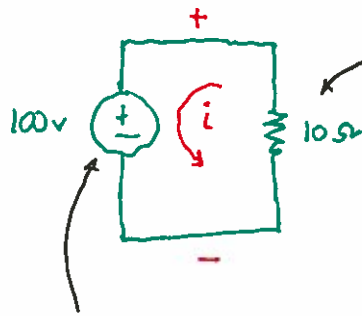


Monday, January 18, 2016
(both L02, L03)

Example revisited



For this current direction i
and voltage polarity v .

$$v = -iR, \text{ so } i = -\frac{v}{R}$$

$$i = \frac{-100\text{V}}{10\Omega} = -10\text{A}$$

Passive reference convention

$$p = +vi = 100 \times -10 \\ = -1000\text{W}$$

(power delivered)

In resistor,

$$p = -vi \\ = -100 \times -10$$

$$= +1000\text{W (absorbing)}$$

Example 2

Assume energy cost is \$0.12 per kilowatt-hour (kWh)

- electric bill for 30 days: \$60.00
- power is constant over this time.

(a) Give power in Watts.

(b) Voltage = 120V, find current

(c) How much energy is saved (in percent) by removing 60W.


Solution

(a) Total energy consumed in 30 days

$$W = \$60.00 / \$0.12 = 500\text{ kWh}$$


Constant power implies
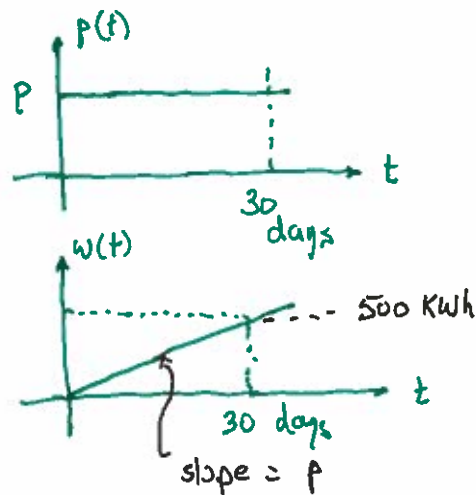
$$\text{and } w(t) = \int_0^t P dt \\ = Pt$$



$$P = \frac{500 \text{ KWh}}{30 \text{ days}} = \frac{500,000 \text{ Wh}}{30 \times 24 \text{ h}}$$

$$= 694.4 \text{ W}$$

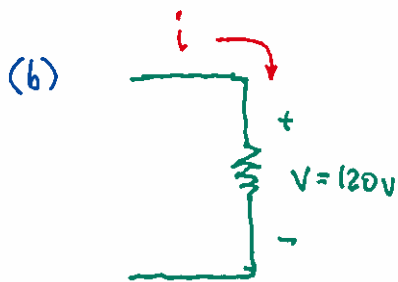

Assuming house is absorbing energy!

$$P = Vi, \text{ so } i = \frac{P}{V} = \frac{694.4}{120}$$

$$= 5.787 \text{ A}$$

(c) Reducing power consumption by 60 W.



$$\text{reduction} = \frac{60}{694.4} \times 100\% = 8.64\%$$

$$\text{or } 8.64\% \text{ of } \$60.00 = \$5.18$$

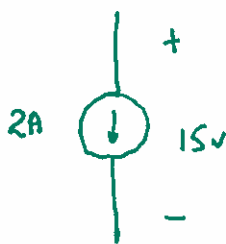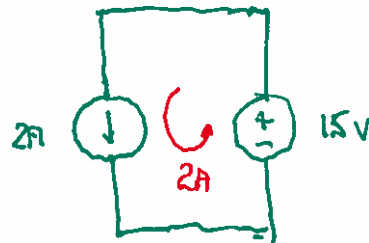Example 3:


Consider the simple circuit

Find the power in each source,
and determine if absorbing
or delivering.



Note that $P = Vi$
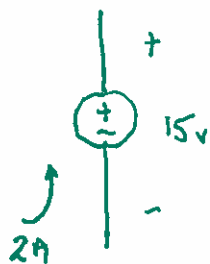
$$P_{2A} = 15 \times 2 = +30 \text{ W (absorbing)}$$



Here, $P_{15V} = -Vi$

$$= -15 \times 2 = -30 \text{ W (delivering)}$$

Note energy balance! $-30 \text{ W} + 30 \text{ W} = 0$

Kirchhoff's laws


So far, we have reviewed

- fundamental electrical quantities v, i (and p, w)
- basic circuit elements (R , sources, etc.)
 - each has its own important $v-i$ relationship.


Kirchhoff's laws now define how v, i distribute in a circuit.

Kirchhoff's Current Law (KCL)

KCL fluid-flow analogy

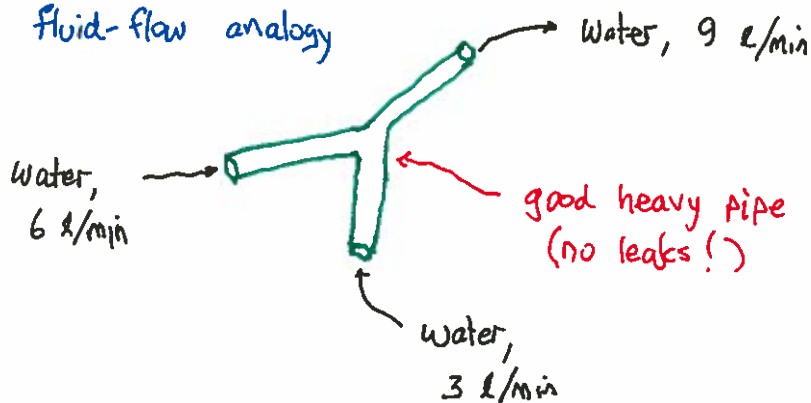

Consider a node in a circuit

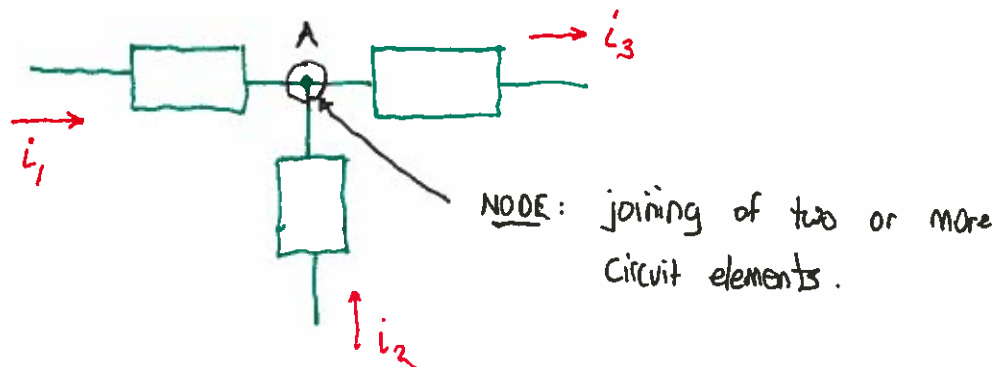


KCL states:

Algebraic sum of all currents
at a node must be zero

choose a consistent way to distinguish incoming and outgoing currents at a node.

E.g.,

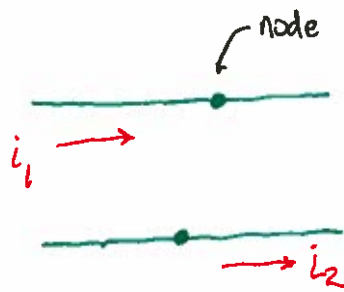

incoming current adds

outgoing current subtracts

Then, sum currents at node A

$$\underbrace{i_1 + i_2}_{\text{entering node A}} - \underbrace{i_3}_{\text{leaving node A}} = 0$$