

This is similar to the inverting amplifier, except V_{in} is moved to the non-inverting terminal (+)

Thursday, March 3, 2016

Summing-point constraints: $i_n = i_p = 0$
 $V_a = V_{in}$ (both '+' and '-' terminals at V_{in})

Node equation at a.

Node a: $\frac{V_a}{R_i} + \frac{V_a - V_o}{R_f} + \cancel{i_n} = 0$

and $V_a = V_{in}$, so

$$\frac{V_{in}}{R_i} + \frac{V_{in} - V_o}{R_f} = 0$$

$$\frac{R_f}{R_i} V_{in} + V_{in} - V_o = 0$$

$$\text{so } V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

which we may write as


$$A_v = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}$$

closed-loop gain

note positive (non-inverting amplifier)

The differential amplifier

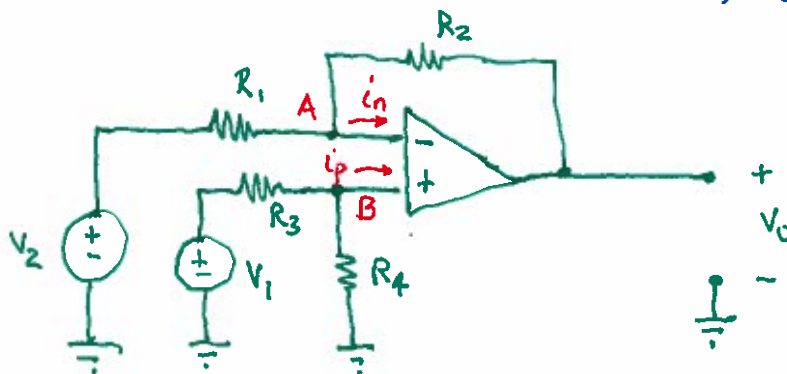This is another very important and very common configuration.



Combines both an inverting and non-inverting amplifier.


From node equations at A and B

$$\text{Node A: } \frac{V_A - V_2}{R_1} + \frac{V_A - V_O}{R_2} + i_n = 0 \quad (1)$$

$$\text{Node B: } \frac{V_B}{R_4} + \frac{V_B - V_1}{R_3} + i_p = 0 \quad (2)$$

From (2), $\frac{V_B}{R_4} + \frac{V_B}{R_3} = \frac{V_1}{R_3}$, so $V_B \left(\frac{1}{R_4} + \frac{1}{R_3} \right) = \frac{V_1}{R_3}$
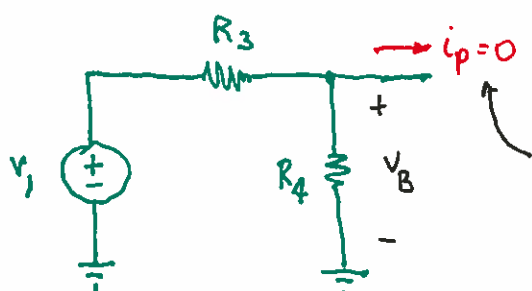
$$V_B = V_1 \left(\frac{R_4}{R_3 + R_4} \right) \quad (3)$$



note this is a voltage divider equation!

since no current can flow here (virtual open circuit), then R_3 and R_4 are in series!

$$V_B = \frac{R_4}{R_3 + R_4} V_1$$

Now, $V_A = V_B = V_1 \left(\frac{R_4}{R_3 + R_4} \right)$. Substitute into (1).

$$\frac{V_A - V_2}{R_1} + \frac{V_A - V_O}{R_2} = 0$$

$$\frac{V_A}{R_1} + \frac{V_A}{R_2} - \frac{V_2}{R_1} = \frac{V_O}{R_2}$$

$$V_O = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) R_2 - \frac{V_2 R_2}{R_1}$$

$$V_O = \left(\frac{R_2 + R_1}{R_1} \right) V_A - \frac{V_2 R_2}{R_1}$$


$$= \left(\frac{R_2 + R_1}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_1 - \left(\frac{R_2}{R_1} \right) V_2$$

If we let $\frac{R_2}{R_1} = \frac{R_4}{R_3}$, then it can be shown that

$$V_o = \frac{R_2}{R_1} (V_1 - V_2) \quad \left. \vphantom{\frac{R_2}{R_1}} \right\} \text{ amplified voltage difference.}$$

Examples of other op-amp circuits

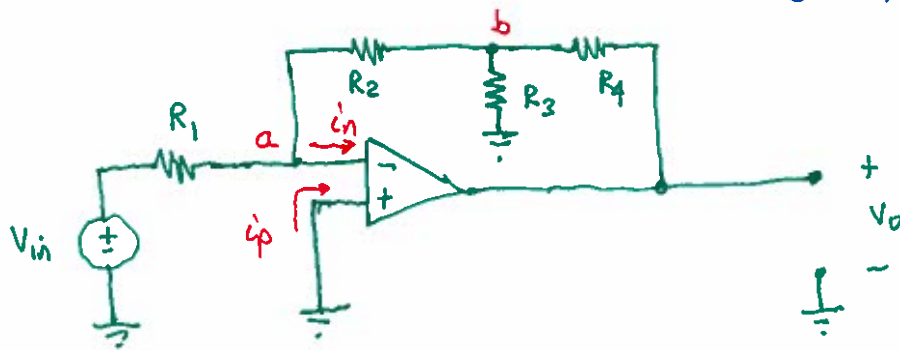Example 1: More practice — another inverting amplifier circuit



Node a: $\frac{V_a - V_{in}}{R_1} + \overset{0}{i_n} + \frac{V_a - V_b}{R_2} = 0$

With $V_a = 0$, $-\frac{V_{in}}{R_1} - \frac{V_b}{R_2} = 0$ (1)

Node b: $\frac{V_b - V_a}{R_2} + \frac{V_b}{R_3} + \frac{V_b - V_o}{R_4} = 0$

$$V_o = R_4 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) V_b$$
 (2)

From (1),

$$V_b = -\frac{R_2}{R_1} V_{in}, \quad \text{so}$$

$$V_o = -\frac{R_4 R_2}{R_1} \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) V_{in}$$