

Can find  $I_A$  from total developed power

Thursday, April 7 2016

$$P_{dev} = I_A E_A$$

$$I_A = \frac{7460 \text{ W}}{250} = 29.84$$

→ In this case, note that another way to calculate  $I_A$  is by

$$T_{dev} = K\phi I_A$$

$$\begin{aligned} \text{so } I_A &= \frac{T_{dev}}{K\phi} = \frac{47.49}{1.59} \\ &= 29.84 \text{ A.} \end{aligned}$$

The applied voltage  $V_T$  by KVL:

$$-V_T + I_A R_A + E_A = 0$$

$$\text{so } V_T = E_A + I_A R_A$$

$$\begin{aligned} V_T &= 250 + (29.84)(0.3) \\ &= 258.95 \end{aligned}$$

Total developed power in the armature (10 HP),  $P_{dev} = 7460 \text{ W}$


Total input power includes power supplied by  $V_T$  and field losses.

$$\begin{aligned} P_{in} &= V_T I_A + I_F^2 R_F \\ &= (258.95)(29.84) + (3)^2(50) \\ &= 8177.1 \text{ W.} \end{aligned}$$

$$\begin{aligned} \text{Efficiency: } \eta &= \frac{P_{dev}}{P_{in}} \times 100\% = \frac{7460}{8177.1} \times 100\% \\ &= 91.2\%. \end{aligned}$$

## Power and torque: "developed" vs. "output"

At the mechanical output of the motor

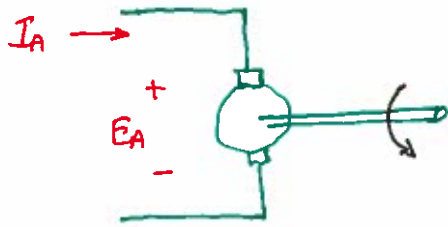

Electrical  
power  
 $P = I_A E_A$


Developed mechanical  
power  $P_{dev} = P = I_A E_A$

$$\text{and } T_{dev} = \frac{P_{dev}}{\omega_m} = K\phi I_A$$

Developed power and torque do not take into account rotational losses, such as

- friction (bearings)
- windage (wind resistance)

In a practical motor, we have

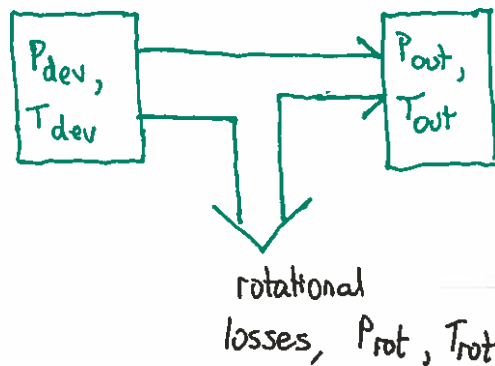


$$P_{out} = P_{dev} - P_{rot}$$
$$T_{out} = T_{dev} - T_{rot}$$

If there are no rotational losses, then  $P_{out} = P_{dev}$ ,  $T_{out} = T_{dev}$ .
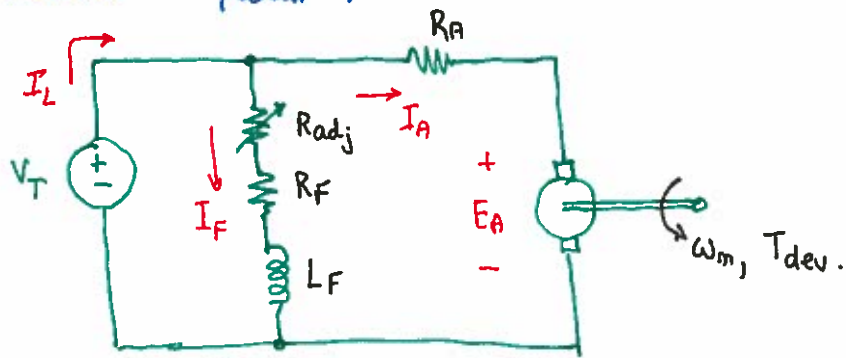
## Shunt - connected DC machines

In this machine configuration, the field and armature circuits are connected in parallel.



The variable resistor  $R_{adj}$  is available to adjust the torque-speed characteristic. The total input power is

$$P_{in} = V_T I_L \quad \text{total "line current"}$$

Some of this creates the field. Power absorbed by the field is dissipated as heat

$$\begin{aligned} P_F &= I_F^2 (R_{adj} + R_F) \\ &= \frac{V_T^2}{R_F + R_{adj}} \end{aligned}$$

Armature resistance similarly dissipates power as heat.

$$\begin{aligned} P_A &= I_A^2 R_A \\ &= \frac{(V_T - E_A)^2}{R_A} \end{aligned}$$

The remaining power is developed power  $P_{dev}$ .

$$P_{dev} = E_A I_A$$

$$\text{and } T_{dev} = \frac{P_{dev}}{\omega_m} = \frac{E_A I_A}{\omega_m}$$

Example: Consider a shunt-connected DC machine with

$$V_T = 300 \text{ V}$$

$$R_F = 10 \Omega$$

$$R_{adj} = 20 \Omega$$


$$R_A = 0.065 \Omega$$

$$\left. \begin{array}{l} R_F = 10 \Omega \\ R_{adj} = 20 \Omega \end{array} \right\} \text{combined } R_F = 30 \Omega$$

- The machine also has rotational losses (friction) represented by constant Torque :  $T_{rot} = 12 \text{ Nm}$  (rotational power loss proportional to speed  $P_{rot} = T_{rot} \omega_m$ )
- From prior tests on this machine, when  $I_F = 10 \text{ A}$  and  $n_m = 1200 \text{ rpm}$ ,  $E_A = 300 \text{ V}$ .
- Total required torque by the mechanical load is  $T_{out} = 200 \text{ Nm}$ .

Find motor speed and efficiency.

Solution: In the field, for DC,

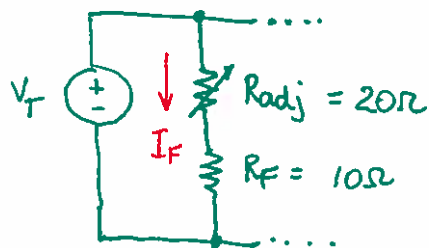

$$I_F = \frac{300}{20 + 10} = 10 \text{ A}$$

From information given at  $n_m = 1200 \text{ rpm}$  for  $I_F = 10 \text{ A}$ ,  $E_A = 300 \text{ V}$ .  
Basic machine equations again

$$T_{dev} = K \phi I_A, \quad E_A = K \phi \omega_m$$