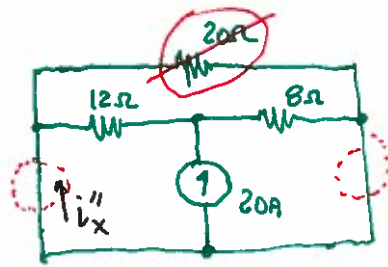


Friday, February 26, 2016




Current divider


$$i_1 = \frac{8}{8+12} \times 20 = 8A$$

and $i_x'' = -i_1$, so

$$i_x'' = -8$$

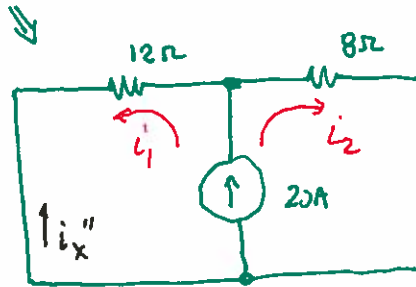

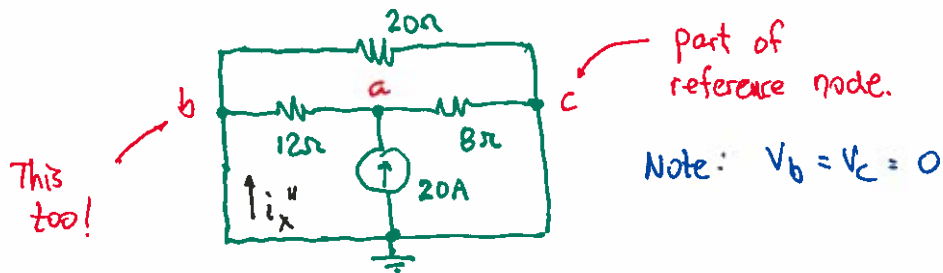Clearly, short-circuits can cause much confusion. Let's reattempt this without taking special notice.



$$\text{Node a: } -20 + \frac{V_a}{12} + \frac{V_a}{8} = 0$$

$$\text{so } V_a = 96V.$$


To solve for i_x'' , write node equation at b.

$$\text{Node b: } -i_x'' + \frac{V_b - V_a}{12} + \frac{V_b - V_c}{8} = 0$$

$$-i_x'' + \frac{0 - 96}{12} + \frac{0 - 0}{8} = 0$$

$$i_x'' = -8$$

(c) 30-volt source by itself

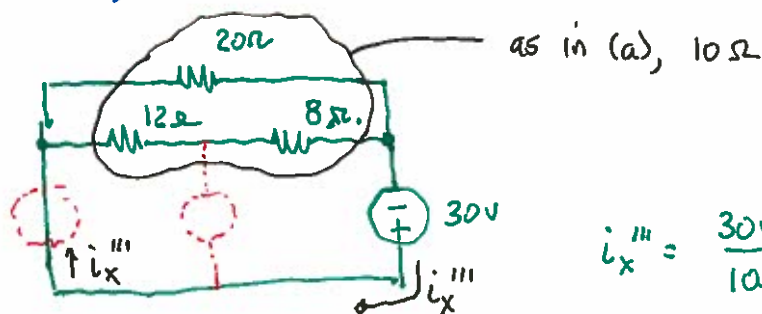

$$i_x''' = \frac{30V}{10\Omega} = 3A$$


By superposition,

$$i_x = i_x' + i_x'' + i_x''' \\ = 5 - 8 + 3 = 0$$

$$i_x = 0$$

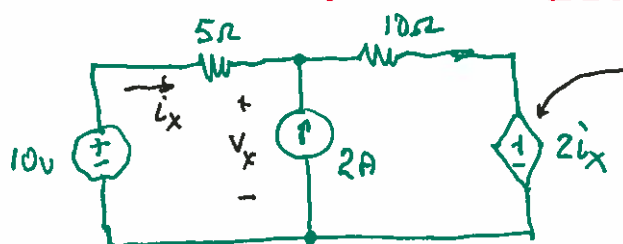
Example 2: With dependent source. Find V_x by superposition

IMPORTANT: only zero the independent sources



dependent sources: if we have them, we have to put up with them!

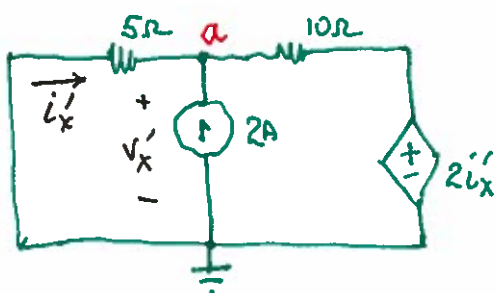(a) 2A current source acting alone; find V_x' .



Node a: $\left(\frac{V_a}{5}\right) - 2 + \frac{V_a - 2i_x'}{10} = 0$

this is $-i_x'$

$$(x10) \quad 2V_a - 20 + V_a - 2i_x' = 0$$


$$3V_a - 2i_x' = 20$$

We know $i'_x = -V_a/5$, so

$$3V_a + \frac{2V_a}{5} = 20 \quad \therefore V_a = 5.88\text{V}$$

so $V'_x = 5.88\text{V}$

(b) Now with the 10V source acting alone

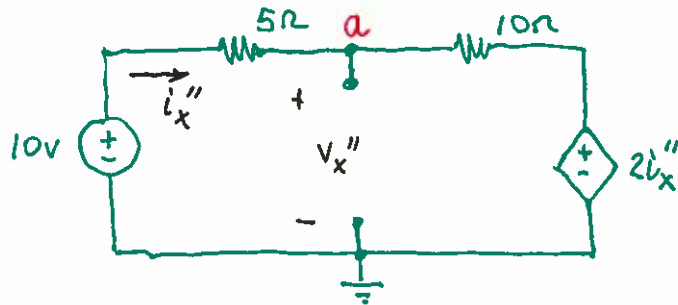

Node a: $\frac{V_a - 10}{5} + \frac{V_a - 2i_x''}{10} = 0$

Note this is $-i_x''$, so $i_x'' = \frac{10 - V_a}{5}$

$$(x10) \quad 2V_a - 20 + V_a - 2i_x'' = 0$$

$$3V_a - 2i_x'' = 20$$

$$\text{or} \quad 3V_a - 2\left(\frac{10 - V_a}{5}\right) = 20$$

$$3V_a - 4 + \frac{2}{5}V_a = 20$$

$$\therefore V_a = 7.06\text{V} \quad \text{so}$$

$$V''_x = 7.06\text{V}$$

Finally, by superposition

$$V_x = V'_x + V''_x = 5.88 + 7.06$$

$$V_x = 12.94\text{V}$$

OPERATIONAL AMPLIFIERS

An operational amplifier (op amp) is a complex electronic circuit that implements a voltage-controlled voltage source.

Many important practical engineering examples:

- high-speed video amplifiers
- microelectronic filters (telecommunications - huge industry)
- instrumentation (precision measuring devices)

Invented in 1968. Originally used to perform operations in "analog" computers to perform operations on voltages and currents

- addition
- integration
- multiplication